

WIN \$10,000 IN  
PRIZES!

# Electronics & Technology Today

\$3.50  
MM70924  
FEB/89

Canada's Magazine for High-Tech Discovery

# 12<sup>TH</sup> ANNIVERSARY!

PLUS

Power Controller  
Pioneer's Surround Sound  
Versatile Home Alarm  
Using Norton Amps

## Dell 386 Review



0 5743

513735\*JAN 90\* E103\*  
KEVIN JOURNEAU  
68 EASTON AVE  
MONTREAL WEST PQ H4X 1K8



# TAKE YOUR FIRST STEP TOWARD A CAREER IN THE MUSIC BUSINESS.



- ☐ Highly selective, two-year training program
- ☐ Campuses throughout North America
- ☐ Current theory mixed with practical hands-on training
- ☐ Modern state-of-the-art 24-track recording studios and digital audio labs
- ☐ All classes taught by qualified, working professionals
- ☐ Job placement assistance
- ☐ Financial assistance available
- ☐ Fully accredited by ACCET

 **TREBAS**  
INSTITUTE OF RECORDING ARTS

6602 Sunset Blvd., **Hollywood, CA**,  
U.S.A. 90028 (213) 467-6800

112 East 3rd Ave., Suite 305, **Vancouver, B.C.**,  
Canada V5T 1C8 (604) 872-2666

410 Dundas St. East, **Toronto, Ontario**,  
Canada M5A 2A8 (416) 966-3066

290 Nepean Street, **Ottawa, Ontario**,  
Canada K1R 5G3 (613) 232-7104

1435 Bleury, Suite 301, **Montreal, Quebec**,  
Canada H3A 2H7 (514) 845-4141

Circle No. 1 on Reader Service Card



# Electronics & Technology Today

Canada's Magazine for High-tech Discovery

Volume 13, Number 2

February 1989



## Our Cover

144 issues (plus our special editions) and the Dell 310 computer highlight our 12th year; design by Bill Markwick and Kevan Buss.

## FEATURES

<b>Guide to PC Interfacing, Part 2</b> .....	9
Continuing Steve Rimmer's series on PC ports.	
<b>The Scientists Tell Me</b> .....	12
David Dempster's monthly look at the world of science.	
<b>Index for 1988</b> .....	14
A year's worth of features, reviews and projects.	
<b>The Techie's Guide to C, Part 2</b> .....	16
Powerful programming for technical work.	
<b>Using the Norton Amplifier</b> .....	24
A review of this underused and novel op amp.	
<b>Looking Back</b> .....	38
Steve Rimmer recounts his beginning years with ET.	

## TECHNOLOGY

<b>How Stepping Motors Work</b> .....	49
A look at the various types and their controllers.	

## PRODUCT REVIEW

<b>Dell 310 Computer</b> .....	20
<b>Pioneer's Surround Sound</b> .....	35

## PROJECTS

<b>Simple Codelock</b> .....	22
<b>Versatile Home Alarm</b> .....	42
<b>Power Controller</b> .....	53
<b>Small-Fry Mini Amp</b> .....	60

## INFORMATION

<b>For Your Information</b> .....	4
<b>Software</b> .....	15, 19, 27, 53
<b>Books</b> .....	28
<b>Tech Tips</b> .....	30
<b>Toshiba Computer Contest</b> .....	32
<b>Marketplace</b> .....	41
<b>Next Month</b> .....	47
<b>Subscriptions</b> .....	47
<b>Order Form</b> .....	48
<b>Classifieds</b> .....	58
<b>Advertiser's Index</b> .....	3



## **Electronics & Technology Today**

**Electronics & Technology Today**  
is published 12 times a year by:  
Moorshead Publications Ltd.  
1300 Don Mills Road, North York, Ontario  
M3B 3M8 (416)445-5600 FAX: (416)445-8149

Editor: William Markwick  
Director of Production: Papu Leynes  
Art Direction: Kevan Buss  
Circulation Manager: Sharon Cernecca  
Advertising Representative: Garth Birt

President: H.W. Moorshead  
Publisher & V.K. Marskell  
Executive Vice-President:  
Vice-President - Sales: A. Wheeler  
Vice-President - Finance: B. Shankman  
Production Assistants: C. Dalziel  
N. Sunderji

Office Manager: P. Dunphy  
Reader Services: R. Cree  
J. Cardoni  
Advertising Services: M. Millett  
H. Brooks

**Newsstand Distribution:**  
Master Media, Oakville, Ontario

**Subscriptions:**  
\$22.95 (one year), \$37.95 (two years).  
Please specify if subscription is new or a  
renewal.

Outside Canada (US Dollars). U.S.A. add \$3.00  
per year. Other countries add \$5.00 per year.

**Postal Information:**  
Second Class Mail Registration No. 3955.  
Mailing address for subscription orders,  
undeliverable copies and change of address  
notice is:  
Electronics & Technology Today  
1300 Don Mills Road, North York, Ontario  
M3B 3M8.

**Printed by:**  
Heritage Press Ltd., Mississauga, Ontario  
ISSN 07038984

Moorshead Publications also publishes PETS  
Magazine, Computing Now!, Computers in  
Education, Business Computer News and  
Government Purchasing Guide.

Circulation independently audited by  
MURPHY & MURPHY Chartered  
Accountants.

Electronics & Technology Today  
is indexed in the Canadian Magazine Index  
by Micromedia Ltd.  
Back copies are available in microfilm form  
from Micromedia Ltd. 158 Pearl Street,  
Toronto, Ontario M5H 1L3 (416)593-5211.

# FOR YOUR INFORMATION

## **Correction**

Gulp. Those of you reading Steve Rimmer's guide to the C programming language last month may have thought that huge amounts of text were missing. In fact, the order of two of the pages was inadvertently switched during the printing. To read it in the correct order, the pages would go 16-17-19-18-20.

**COPYRIGHT:** All material is subject to worldwide copyright. PCB designs are copyright and may not be sold without permission.

**LIABILITY:** No responsibility whatever is accepted for failure of projects to perform for any reason, and no responsibility is accepted for any injury or damage caused by any fault in design.

**EDITORIAL QUERIES:** We cannot answer telephone queries.

Written queries must be accompanied by a stamped, self-addressed envelope, relate to recent articles and must not involve the staff in any research.

**PCB SUPPLIERS:** We do not supply printed circuits or kits, and we do not keep track of availability. However, PCBs for projects are available from the following mail order sources:  
**B-C-D Electronics**, PO Box 6326, Stn. F., Hamilton, Ontario L9C 6L9.

**K.S.K. Associates**, PO Box 266, Milton, Ontario L9T 4N9.

**Spectrum Electronics**, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.

## **Weather Satellite Sources**

In answer to the unusually heavy response to the weather satellite photo article in last month's issue, we would like to add the following information. The author can be contacted for further information: Hank Brandli, 3165 Sharon Drive, Melbourne, Florida 32904-9533, (407) 724-5599. The low-noise preamp mentioned, the Vanguard 102-W, is available from Vanguard Labs, 196-23 Jamica Avenue, Hollis, NY 11412, (718) 468-2720. PC hardware and software information is available from Jim MacLean, 2112 S. Parsons Avenue, Melbourne, Florida 32901, (407) 727-3646.

## **Undersea Fibre Optics**

AT&T has deployed TAT-8, the world's first undersea fibre optic cable. Stretching 3,148 miles from New Jersey to a branching repeater on Europe's continental shelf, the cable has the capacity to handle 40,000 simultaneous phone calls over its fur fibres (with two more fibres in reserve for reliability). 109 repeaters along the cable regenerate the digital audio, which is carried by a pulse train of infrared laser light at 295.6 megabits per second. The repeaters are powered from a 5,000 volt DC feed.

The first undersea cable was laid in 1856, though it failed after a few weeks service. Another telegraph cable was successfully laid between Ireland and Newfoundland in 1866. When it came to telephone service, though, the use of shortwave radio dominated until the 1950s. The development of the repeater made the analog long-distance cable possible, and in 1956 AT&T laid TAT-1, carrying 36 simultaneous calls between Scotland and Newfoundland.

TAT-9 will be in service in 1991, carrying 80,000 calls. A unique undersea branching multiplexer will allow the cable to come ashore at five different points in the US, Canada, the UK, France and Spain.

## **Soldering Equipment**

Antex of England has appointed Cobra Sales of Downsview as the exclusive importer of their precision soldering irons, soldering stations, stands, etc. Their TCS soldering pencil, for instance, has a built-in temperature control (200-450°C) and a 50W element. Various tips are available, including IC tips that melt up to 16 pins simultaneously. Especially interesting is a soldering gun with jaws like a large pair of crimping pliers, used to solder plumbing pipe where a flame is not possible.

Circle No. 2 on Reader Service Card



# IF YOU WANT TO LEARN PC SERVICING, YOU MUST GET INTO A MICROCOMPUTER!

"ALSO  
INCLUDES  
DOT MATRIX  
PRINTER!"

## Learn PC Servicing By Building Your Own (PC-XT Turbo) Desk-Top Computer!

NTS "Home-Study" training gets you right down into the heart of computer circuitry. Learn how microprocessors function, how they operate and are used to solve problems. Your programme includes a wide variety of tests and projects you perform as you build your own PC-XT-Turbo, circuit board by circuit board unit by unit.

## Hands-On Training With Your (100% IBM Compatible) PC-XT Turbo Puts You At The Leading Edge of Technology!

This remarkable desk-top Micro-computer is the most powerful and versatile ever offered in any home study course .... and it's yours to keep.

- IBM is a Registered Trademark of IBM Corporation.
- All Diploma Programmes 100% tax deductible.
- Monthly payment Plan available.

PHONE FOR FREE  
COLOUR CATALOGUE  
842-8383

### Advanced features of this PC-XT Turbo include:

- 8088 microprocessor for IBM compatibility • 640K Ram for high speed performance • 8 expansion slots • 135 watt power supply
- Dual 360K double density floppy disk drives • Colour graphics/printer adapter card
- Operating system included: MS-DOS with GW Basic • 4.77 MHz - 8MHz "Turbo".



**National Technical Schools**  
517 Bohemia Cres, Oakville, Ontario  
L6J 2K7 (416) 842-8383

School Head Office: 456 W. Martin Luther King Jr. Blvd., Los Angeles, CA 90037



# Computer Expo

April 20, 21, 22, 23, 1989  
Toronto International Centre


## \*Brands:

Amstrad  
NEC  
Epyx  
Atari  
Electronic Arts

IBM  
Hayes  
iNet  
Accolade  
Berkeley  
Novell  
AMA  
Execufold  
Panamax  
US Robotics  
Commodore  
Roland  
Datatrain  
Epson  
Miniscribe  
CUI  
Apco  
Educomp  
Amiga

Star Micronics  
Tron  
Xerox Ventura  
Zenith  
Canon  
Packard Bell  
Sharpe  
Nintendo  
Micropro  
AST Research  
Opcode  
JL Cooper  
Timeworks  
Xetec

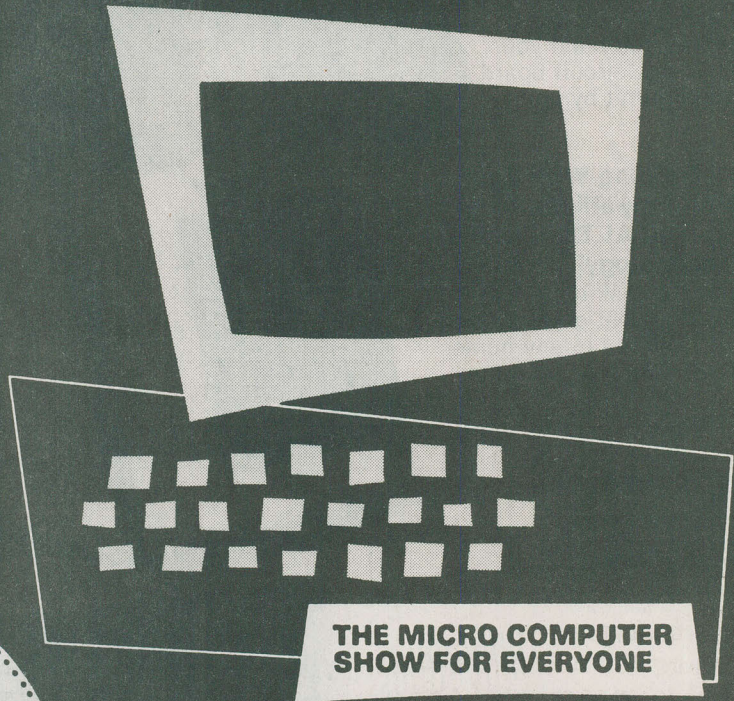Dysan  
Spencer  
Aldus  
Akai  
Mindscape  
Sierra On-Line  
Ultinet  
Microsoft  
Fuji  
Sony  
Hewlett-Packard  
Load 'N Go  
Infocom  
Apple  
WordPerfect  
Ashton-Tate



**THE MICRO COMPUTER  
SHOW FOR EVERYONE**

- SHOW AND SALE
- FREE SEMINARS
- HUNDREDS OF COMPUTERS
- FREE PARKING
- THOUSANDS OF SOFTWARE TITLES

\* 1988 Computer Expo brand names. List may vary for 1989.

**WIN A NEC LAPTOP COMPUTER**

For information contact:



**The Hunter Group Inc**

204 Richmond Street West, Suite 410  
Toronto, Ontario, Canada M5V 1V6  
(416) 595-5906 Fax: (416) 595-5093

Circle No. 3 on Reader Service Card

THE  
HOME  
OFFICE



SPONSORED BY

**NEC**



## Unix Study

The Unix operating system is rarely heard from in popular computing, which is dominated by Microsoft's MS-DOS. There's a general feeling that it's limited to scientific and engineering applications, but the Canadian Network of Unix Systems Users have commissioned a comprehensive study that shows that the highest use is for data processing and office automation. 31% of those surveyed use Unix for general computing, and 79% use it for specific limited functions (there was some overlap). Unix as a percentage of industry hardware revenue will increase from 6% in 1988 to 19% in 1992. For further information, you can contact the Unix user's group at (416) 259-8122.

## Another Fast One

Continuing our monthly reports on the world's fastest semiconductor: this month it's Bell Labs and their bipolar transistor that can switch at 140 billion times a second (140GHz). That's 12 times faster than the commercial bipolars used in today's superconductors. The new transistors are made from indium phosphide and gallium indium arsenide using a new method of crystal-growing that minimizes collisions of the electrons with atoms in the structure. Researchers are evaluating the product potential of the new device, which would have obvious applications in high-speed logic or gigabit lightwave communications.

## HP Workstation

Hewlett-Packard has introduced a new low-cost workstation using the Motorola 68030 CPU and 68882 math coprocessor, providing 4 MIPS (million instructions per second) for a price of \$5,495 US. Other models in the 9000 Workstation Family line can provide up to 8 MIPS.

## IBM Grant

IBM has granted \$1,000,000 to Georgia Tech in Atlanta to support research projects in the field of electronics manufacturing. This continues the trend in both the US and Canada for commercial companies to work closely with universities in research and development.

## AutoShade Upgrade

AutoShade, Autodesk's program that transforms AutoCAD drawings into full-color shaded renderings, now supports the 3D design capability offered by AutoCAD

Release 10. It also includes VGA drivers, and files for hardcopy of shaded renderings are now compatible with desktop publishing applications via the Encapsulated Postscript format.

## Arctic Ozone

NASA and the National Oceanic and Atmospheric Administration (NOAA) have announced an investigation in early 1989 to better understand the nature of potential ozone depletion of the stratosphere over the Arctic. Scientists from NASA, NOAA and other organizations will carry out an airborne study similar to that done last year over the Antarctic. That study directly implicated manmade chlorofluorocarbons (CFCs) as a cause of the ozone hole and raised the question whether the same thing could be occurring in the Arctic.

Flights will be stationed in Stavanger, Norway, with other similar tests based in

Alaska and the NWT. Coordinated balloon experiments will be carried out by the Soviets and Germany. Airborne instruments will sample the stratosphere for many different chemical compounds. One of the aircraft used is the ER-2, a highly modified U-2 high-altitude reconnaissance plane; it will fly at up to 65,000 feet.

A preliminary report on the findings should be ready by late August.

## An AT for the Amiga

Commodore Business Machines has announced the availability of the 2286D Bridgeboard, a plug-in for the Amiga 2000 and 2500 computers, giving them an 80286 processor for AT compatibility. The board is recognized at power-on and allows the user to run IBM-compatible applications concurrently with Amiga software because of the Amiga's multi-tasking operating system. ■

## MULTI-FUNCTION Counters

### GREAT FEATURES & PRICE!

#### HCF-100

Compact, lightweight 10 Hz to 100 MHz counter with four function performances. Features eight digit LED display, low power consumption circuit with functions for frequency, period, totalize and self check.

**\$259.**


Plus \$10 for shipping & handling.

#### HCF-1000

Range 10 Hz to 1 GHz with 8-digit LED display, frequency, period, totalize and self check functions.

**\$495.**

Plus \$10 for shipping & handling.

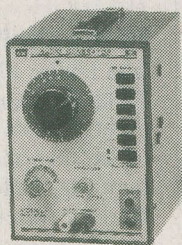


## AUDIO GENERATOR

Five frequency ranges 10 MHz - 1 MHz, low distortion factor and six range output attenuator: 0, 10, 20, 30, 40 and 50 dB. 110 VAC power supply.


#### MODEL GAG-808B

**\$259.**

Plus \$10 for shipping & handling.

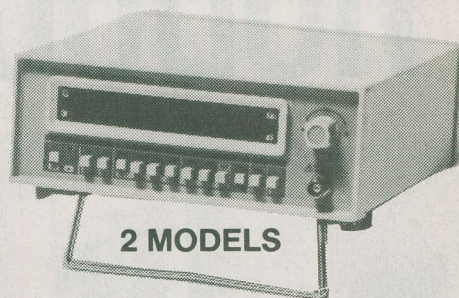

**2 MODELS**

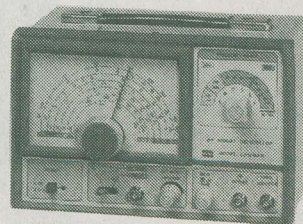

## RF GENERATOR SUPER VALUE!

Features frequency range from 100 KHz to 150 MHz and up to 450 MHz on harmonics, internal/external AM modulation, frequency monitor output, high/low switch and fine adjustable output control.

#### MODEL GRG-450

**\$259.**

Plus \$10 for shipping & handling.



Ask for our free catalogue.


# KB ELECTRONICS

355 Iroquois Shore Road, Oakville, Ontario L6H 1M3  
Tel: (416) 842-6888 • Telex: 06-982396 KBELOKVL

"ORDER BY PHONE OR MAIL. CREDIT CARD, MONEY ORDER, CERT. CHEQUE OR C.O.D. ONTARIO RESIDENTS ADD 8% P.S.T."



# NEW PRODUCTS

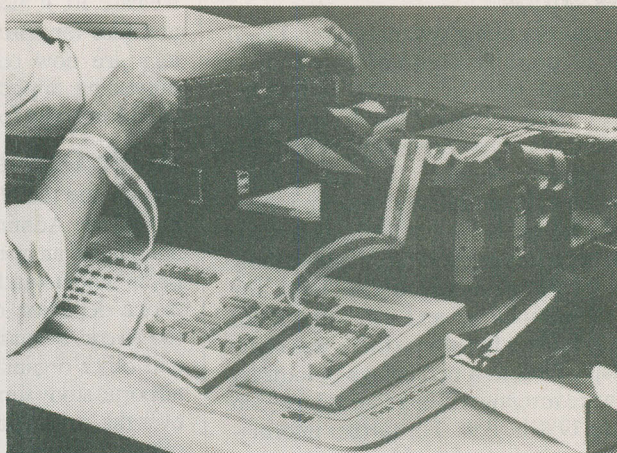

## ESD Strap

Low-cost static protection for electronic repair personnel and hobbyists is now available from 3M Canada Inc., Static and Electromagnetic Control Systems. A hypoallergenic conductive adhesive strip is attached to a porous, non-woven, insulative backing. A one-megohm resistor is part of the strap. When secured to a ground such as an equipment frame, using its self-sticking copper fopil, the strap allows movement within a four-foot radius.


Circle No. 5 on Reader Service Card



## New Multimeter

The Brunelle Model 4090 Digital Multimeter features computer compatibility via an RS232 buffer, plus all the standard multimeter functions. When used with the Model 270 Buffer and software, signal can be measured and output to a computer or printer. Various optional adapters allow measurement of temperature, humidity, light, RPM, etc. The software and hardware is compatible with the IBM PC/XT/AT.

Circle No. 6 on Reader Service Card

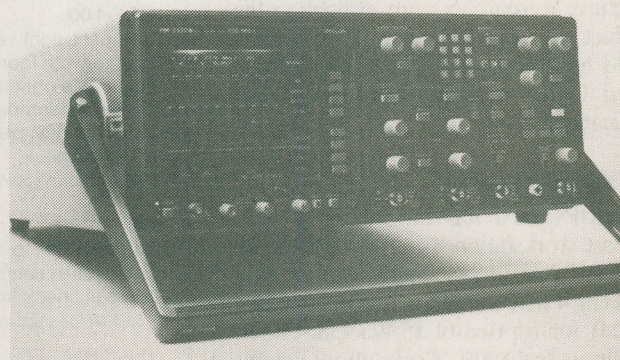

## Hi-res Digital Scope

The Philips PM 3320A Digital Storage Oscilloscope from Fluke Electronics Canada Inc. is suited for capturing single events with its 200MHz bandwidth, real-time sampling rate of 250MS/s and 10-bit resolution. Using random repetitive sampling, the full 200MHz of the dual-channel scope can be used for waveform digitizing and storage. Two acquisition modes are available to capture signal details that exceed preset limits. The incoming signal is compared to one stored in memory and the new waveform is stored as soon as a difference appears, useful for unattended monitoring of signal lines. Up to 250 front-panel setups can be stored and recalled. Available from stock for \$12,992 Canadian.

Circle No. 7 on Reader Service Card



# Interfacing the PC

## Part 2

**Plumbing the further mysteries of I/O address decoding, it turns out that the world is really controlled by jumper settings.**

STEVE RIMMER

In the first installment of this series, we had a look at the basic port addressing scheme of the 8088 microprocessor that drives the IBM PC and all its lineal — and oftentimes illegitimate — descendants. If you're still a bit dazed by it all, the contents of this article probably won't help you very much. We're going to dig a bit further into the whole writhing mess.

Regrettably, without a workable I/O decoding system fluttering about your head, all that comes later will be grass in the wind.

The basic I/O decoding circuitry that we checked out last month was workable, but only in the most rudimentary sense. In common with North American television and most Tory politicians, it ignored the real world to the best of its abilities. Plugged into just about any PC, it would probably have found itself instantly at odds with something.

This month, we're going to make it a bit more likeable — something that's relatively easy to do for a card, as it turns out. All it takes is a soldering iron. This is more that you can say for a Tory politician... although there are certainly those who would be willing to try the same approach on one just to see what happens.

### Rabbits and Other Jumpers

If you flip back to the last episode in this drama, you'll recall that we devised an I/O decoder which would raise a line if any port in the range of 300H through 31FH were to be addressed by the processor.

The only serious sweat about this is that it was fixed in this range, and no power in the known universe was likely to talk it out of its little hole in the wall.

In the original specification for the IBM PC, this range of port addresses was reserved for designing prototype cards. However, it should be realized that the people who designed this system were genuinely a bit short sighted. They figured that 64 kilobytes of memory, for example, would do for most souls, with 128 kilobytes for the greedy ones. As such, the original port address allocations of the system have become a bit blurred over time as designers realized that most of what they wanted to do with the system hadn't been allowed for.

Some of the original port addresses of the IBM PC *have* remained, of course. Things like disk drives exist in all machines, and, as such, their ports are invariably spoken for. Other devices, like hard drives, are sufficiently common that one would not want to design a card which infringed on their real estate. Of the remaining port ranges, it's largely impossible to realistically carve out any specific range of addresses for a custom peripheral card and blindly assume that it won't already be in use by some other card.

This all being the case, it's pretty well essential that in designing cards for the PC one make the port address range a bit flexible, such that the person using the card can find a free space in the port allocation of her or her particular system

and plug in our card. This, of course, is why there are so many jumpers and DIP switches on cards. Ours will be no exception, of course.

To get started with all this, let's have a look at the "official" port allocation strategy of the PC.

- 000-00FDMA chip
- 020-021Interrupt controller
- 040-043 Timer chip
- 060-063 Parallel port chip
- 080-083 DMA controller
- 0A0-0AFNMI mask
- 0C0-0CFReserved
- 0E0-0E7Reserved
- 100-1FF Not for rent
- 200-20FJoystick port
- 210-217 Expansion box
- 220-24F Reserved
- 278-27F Reserved
- 2F0-2F7Reserved
- 2F8-2FFCOM2 serial port
- 300-31FPrototype card
- 320-32FHard drive
- 378-37FPrinter
- 380-38CSDLC communications
- 3A0-3A9Binary synchronous communications
- 3B0-3BFMonochrome card
- 3C0-3CFReserved
- 3D0-3DFColour card
- 3E0-3F7Floppy controller
- 3F8-3FFCOM1 serial port

In the official IBM view of the universe, port addresses above 3FFH can't



## Interfacing the PC, Part 2

### New improved I/O decoder... now with the miracle ingredient PortSwitch

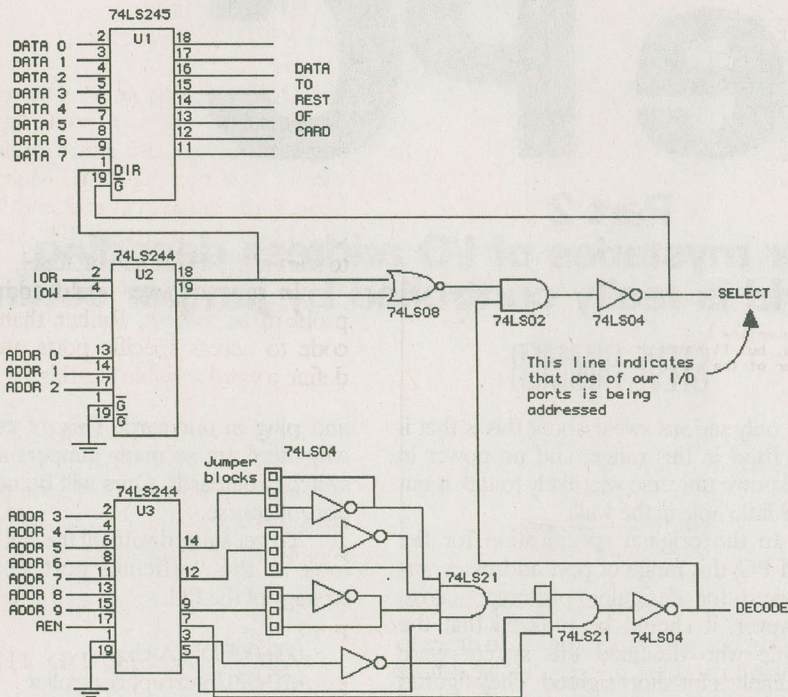


Figure one: The address decoder with modifications to allow for jumper selectable addresses.

be decoded because only address lines zero through nine are supposed to matter to the system when it's doing port I/O. In fact, as we've seen, one could build hardware to handle these extra addresses, although there are several good reasons why not to. The most notable of these is that most real IBM hardware... and clones thereof... do not look, for example, at address line ten. As such, if one attempts to address port 0400H, having designed a card which *can* decode this address, it will look like port 0200H to all the other cards in the system, that is, the ones which ignore line ten.

The low order port addresses, the ones below 200H, are better off left alone unless you specifically want to design a card that creates hardware interrupts. We will do this — but not just now. As such, the area we have to consider in creating

this card is the one which ranges from 200H through 3FFH.

There are a number of devices in this list which may seem a bit unusual. For example, you may not have encountered an SDLC communications card. That's okay — they were never a real driving force in the PC universe. Likewise, if you were designing a local area network card, for example, you could probably assume that the sorts of machines that it would come to reside in would not have joystick ports in them.

If this seems a little funky... ya, well, it is. This is why it's important to make the port addressing of any cards we design for general distribution user selectable to some extent. It's impossible to know which bits of the unspoken for real estate other card designers will have snaffled, so you have to let the heads who use your cards

decide for themselves.

You also have to find ways to explain to said heads how to ascertain what addresses *are* currently in use. Best of cosmic luck in this.

Even if you're just hacking copper for yourself, it's not a great deal of extra work to get this together, and it can save you some hassles later on, should you subsequently add more fiberglass to your system and find that some of it covets the address space you've set up for your home made interfaces.

### Joy Sticks

In order to decode the address space from 300H through 31FH, as we got into last month, we have to see that address lines eight and nine are high and that lines five through seven are low. The lines zero through four constitute the low order part of the address, and don't matter at this stage of the decoding.

You can see the circuitry which does this in the schematic we used last month, or the one for this month, as nothing has really changed in this respect. The 74LS04 at the bottom of the diagram takes care of the lines five through seven. Lines eight and nine go directly to the second 74LS21 and gate. Thus, if all of lines five through seven are low and line nine is high, all of the inputs to the first quad AND gate will be high because of the 74LS04 inverters, and the output of the gate will be high. If line eight is high as well, all the inputs to the second quad AND gate will be high and its output will be high, indicating that we have decoded an address in the range we're interested in.

Clear as a Toronto sky in smog season, I know.

Now, in order to shift the address range around a little bit, let's consider jumpering out one of the inverters that connects the address lines five through seven to the first quad AND gate. Let's lose the one that handles line seven. This line decides whether the address range in question starts at 300H or 380H. As things are, it must be low for the address to fall in the area we're up for decoding. However, with the inverter removed, it would have to go high. As such, with this inverter gone our decoded address range for this card is suddenly 380H through 39FH.

Ah hah!

This is a particularly handy little port address, as it's where the aforementioned and seethingly mythical SDLC communications adapter is supposed to go. It's prime hunting ground for custom cards.



This can be used to replace the 74LS04's and the jumper blocks so that DIP switches can select the port address.

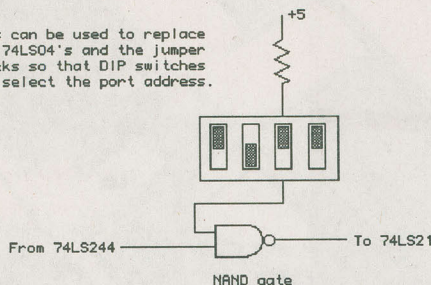


Figure two: using a NAND gate instead of inverters and jumpers. This takes a bit of extra hardware, but it makes the addresses easier to set for the end user of the card. The NAND gates replace the inverters

If we jumper the inverter in line six, we can switch the range up to 340H through 35FH, which the chart doesn't have anything much to tell us about.

How about jumpering both of them, you cry. Well, yes, this would give us address decoding in the range of 3C0H through 3DFH. The lower half of this range is marked as being reserved, whatever that means, and I'd certainly be willing to trample on it. The upper half, however, overlaps the port addresses for the 6845 CRTC chip that makes the colour card go. This is harmless if you have a Hercules card in your computer, but it could be a tad nasty otherwise.

Now, this range might be useful if we were designing a card which really only wanted to be able to use a maximum of sixteen ports. This is actually a fairly probable occurrence, in which case putting the base of the address range at 3C0H would be quite acceptable.

Jumpering out the three inverters on the card does, of course, only allow us to shift the addresses around in the range of 300H through 3E0H. It ignores the juicy looking space down at 0200H, where the aforementioned game controller and ex-

pansion box port ranges dwell. In order to be able to address these areas, we'd have to put a jumperable inverter between pin seven of the 74LS244 that buffers the high order address lines and the second quad AND gate. This would allow us to switch the base of the address range being decoded between 300H and 200H.

In designing actual hardware to allow for the selective jumpering of these inverters, we can set the whole ugly mess up with DIP switches and NAND gates, the preferable way, or we can use three pin header blocks, such that jumper caps fit over two of the three pins to decide how the connection is to be made. I've used jumper blocks in the schematic here to keep things reasonably easy to understand, but you can see how the NAND gate approach works, too.

It may seem that having a variable port address system like this would make writing the software that ultimately speaks to the ports in our card a bit of a nightmare. It doesn't. The 8088 allows for floating port ranges very nicely. It should be kept in mind that no matter where in the absolute address range of the machine the ports actually wind up, all the ports on our card will bear the same relationship to

each other. For example, the 8250 serial chip that drives the COM ports on a PC has the following register port addresses when it lives in the address range for the primary serial port.

3F8H Data buffer and LSB divisor  
3F9H Interrupt enable MSB divisor  
3FAH Interrupt identification  
3FBH Line control  
3FCH Modem control  
3FDH Line status  
3FEH Modem status

Don't worry about what these actually do. However, this is a pretty typical example of register use, and therefore port use, in a peripheral card. More to the point, if this serial port suddenly becomes COM2, all the addresses shift downwards to start at 2F8H instead of 3F8H.

In software, we would address this problem as follows. Rather than writing code to access specific ports, we would define a word variable like this

PORTBASEDW03F8H

and use it to deal with the ports. To read the line status port of this card, for example, we would

```
MOV DX, PORTBASE; GET THE
PORT BASE
ADDDX, 0005H; ADD THE OF-
FSET
IN AL, DX; GET THE BYTE
```

The number five that we add to the base port address is the difference between the port base and the line status register, that is, five locations. No matter where the card turns up, this will remain constant. As such, if we move the card we need only adjust the value of PORTBASE accordingly.

## Ports of Call

I think we've decoded the high order part of the port address question into groveling, helpless submission. It will not rise again. In the next part of this series, we'll look at those five lines that we keep saying don't actually matter. They do, in fact, just not all that much.

By the end of the next part of this engrossing narrative, you'll be able to narrow things down to a single port. It makes one stop and consider the incredible wonder of the universe in all its cosmic order, I know...

'Til then... ■



# THE SCIENTISTS TELL ME

DAVID P. DEMPSTER

## Solar Powered Pumps for the Prairies

Goodbye wind — hello sun. That's the message that Agriculture Canada engineers are giving to prairie farmers these days.

All during last summer the sun beat down on the prairies almost without let-up. It didn't take long for the earth to become parched, crops to shrivel, and livestock to become thirsty. It was bad enough to see crops burn out, it was even more frustrating to scramble for water supplies for cattle. But with all the trouble caused by the sun, that same sun was also the source of power to supply water to a couple of parched prairie farms.

In the past five years, the Prairie Farm Rehabilitation Administration (PFRA) of Agriculture Canada, has been operating two solar pumps in the Swift Current and Saskatoon areas of Saskatchewan. The units which stand about a metre off the ground, are simplicity plus — a battery of cells in a glazed panel on a single post. The post rotates to face the sun which activates the solar cells in the panel to produce electricity. The power generated then runs a pump in an adjoining well which pushes water up to a trough for livestock consumption.

PFRA wasn't happy with the existing system used throughout the prairies — windmills. They are costly to maintain, demanding annual expenditures to keep them operating. Initial costs of windmills are somewhat less than the solar units, \$5,000 vs \$6,000 to

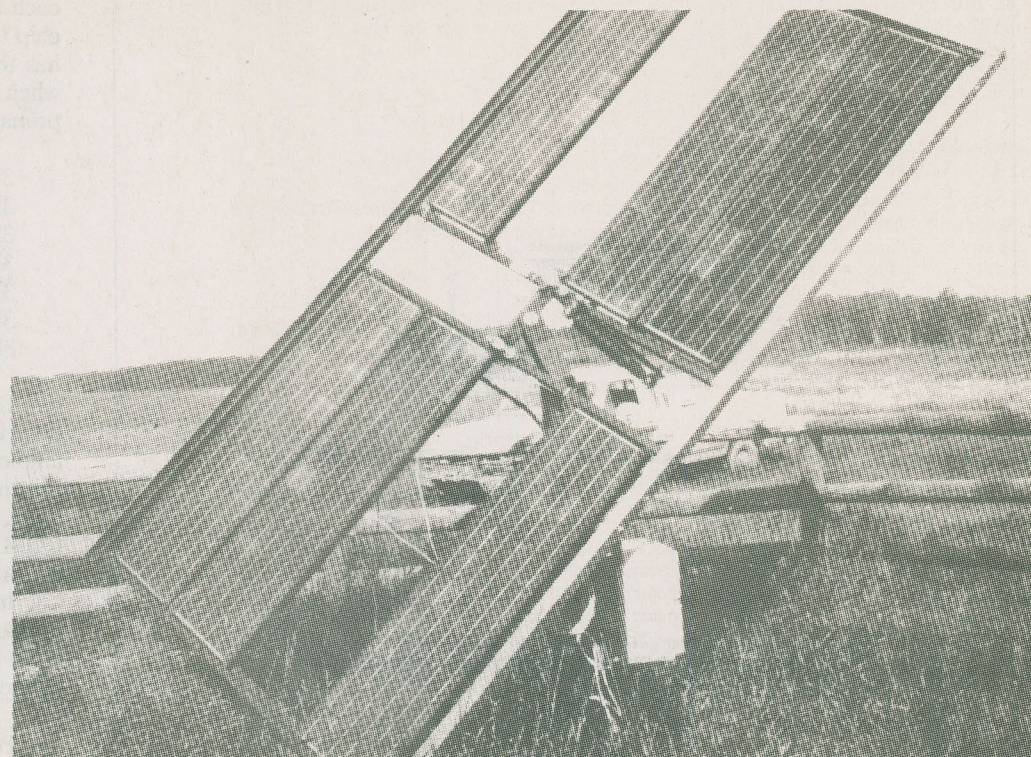


Fig. 1. Solar panels in Montrose Community Pasture near Saskatoon. The panels track the sun's progress through the day.

\$8,000 respectively.

"Quite a few farmers are using windmills in areas that are far from hydro lines," says Ron Lien, a technical standards engineer with the agency. PFRA started looking for various alternatives to conventional windmills when replacement parts started to be in short supply in the 1970s. And based on PFRA's experience over the last five years, he sees solar pumps as being a realistic alternative.

The solar pumps are easier to install and easier to maintain. So far, the two units in operation have needed no significant repair. If repairs are required, components are simple to fix and it is done at ground level, not up on the top of a tower, as it could be with windmills.

Windmills must be checked frequently because in periods of low wind and hot weather the troughs tend to run dry, just when farmers are having to deal with thirsty cattle.

Based on PFRA experience, it would appear solar pumps could have a good future on the prairies — minimizing maintenance problems and guaranteeing a source of water, because with them, the troughs seldom run dry.

What of the future? Says Lien, "The PFRA work with solar pumps is attracting the attention of private industry. Several firms have expressed interest in producing and marketing the pumps to farmers. And if they take off, no doubt the market for them could expand beyond the prairies.

## 3-D Image Data Files from National Research Council

The National Research Council of Canada has recently produced a series of three-dimensional image data files which are available on magnetic tape or disks. This bank of more than 200 3-D images have been designed for use by computer scientists for a variety of research activities — robot vision, graphics, animation, metrology, the medical field, anthropometry, image processing and understanding, 3-D portraiture, inspection vehicle guidance, automatic assembly, and automation.

Each image consists of 256 lines, with each line being made up of 256 points or picture elements. Range resolution is in the order of 0.04 mm and the dimensions of the picture element varies from 0.5 mm to 2.0 mm depending on the subject recorded. A variety of familiar objects are included — industrial objects, tools, utensils, blocks, fruits and vegetables, toys, human faces, plus many others. The three dimensional images can be the same object to form a model; creating a library of object models; and developing interactive procedures to measure, manipulate, and edit 3-D information.

What makes it all so interesting is the quality of the images, quality which has been achieved by a camera based on a laser scanner developed and patented by NRC. The system uses a unique method of high-speed data col-

lection and is capable of scanning 200,000 points in one second. NRC has been successful in transferring the technology to industry. Firms licensed to market the NRC development are Servo-Robot of Boucherville, Quebec, and Hymarc Engineering Ltd. Ottawa, Ontario.

Servo-Robot offers two systems, The Saturn System and the Jupiter System, the former a three-dimensional laser vision for high speed measurements and robot control in the factory, the latter a compact, high speed, high range, 3-D laser ranger finder designed for applications requiring a compact and light weight optical head with a large field of view.

Hymarc Engineering Ltd. has incorporated the technology in their HyScan-60, a 3-D machine vision system for digitizing rapidly and accurately, complex shapes. The resulting data can then be used as input to a CAD/CAM system. Their scanner is said to be suitable for use in many applications and on a variety of materials including metals, plastics, wood and cloth.

Data of the 214 images in the free NRC catalogue may be purchased for \$900 on tape and \$1500 on disk. Individual images on disk only, are \$35 each. Further information about this data bank may be obtained from Mr. N. Rioux, National Research Council of Canada, Division of Electrical Engineering, Laboratory for Intelligent Systems, Photonics and Sensors Section, Ottawa, ON K1A 0R6. (613) 993-



7902. The free catalogue is obtainable from The Editorial Officer, Room 301, Division of Electrical Engineering, National Research Council of Canada, Ottawa, ON K1A 0R6, (613) 993-1880.

### Controlling Computers with an Eye-Tracking Device

All eyes are focused on the future for a Texas A&M University project that uses an eye-tracking device to control machines including computers and robots.

The system's biggest advantage is speed, it is much faster than traditional control schemes because eyes move almost as fast as thoughts, says Dr. Charles Shea, a researcher in the university's Human Performance Laboratory. "The applications of eye tracking systems seem limitless," she said. "The Air Force is currently monitoring eye position in the newest experimental aircraft with hopes someday of incorporating the eyes into the controls scheme. Perhaps some day, not too far off in the future, pilots will be making rapid maneuvers based on the movement of their eyes, just like we saw in "Star Wars."

What are some of these future applications envisaged by Shea. He suggests that eye-tracking systems could benefit wheel-chair use by quadriplegics, microsurgery telephone dialing, reading and air traffic control situations, for a start.

Research on computers to use eye position information as a way to select control functions has been going on in the Human Performance Lab for the past two years, said Shea. Although other facilities across the country are

studying eye-tracking devices, few are looking at it from an applications standpoint, he said.

They have found that subjects can efficiently — and much more rapidly — give commands to a computer by using eye position.

The two major components of eye-tracking systems are a signal processing unit accompanied with spectacle frames and a computer graphics monitor.

The eyeglass frames are equipped with infrared emitting diodes and phototransistors and the basic theory of operation involves electro-optical sensing. The light intensity detected by the phototransistors is dependent on the positioning of the eye.

The system uses photoelectric sensing and processing techniques to determine both the magnitude and direction of eye movement.


Results of Shea's experiments show that after a decision is made, it takes only 20-30 milliseconds for the eyes to make command selections, while giving computer commands via a keyboard or computer "mouse" takes much longer.

"Eyes are an unexplored resource we can use to control our environment. Eye-tracking devices are simply a resource — a special device to enable us to do just that," he stated.

### Good News at last about Acid Rain

Scientists from Norway and Sweden have concluded that lakes and streams will recover at least in part from the chemical changes caused by acid rain.

The scientists wrote in the August 25 issue of *Nature* that their "acid-exclusion experiment shows that chemical

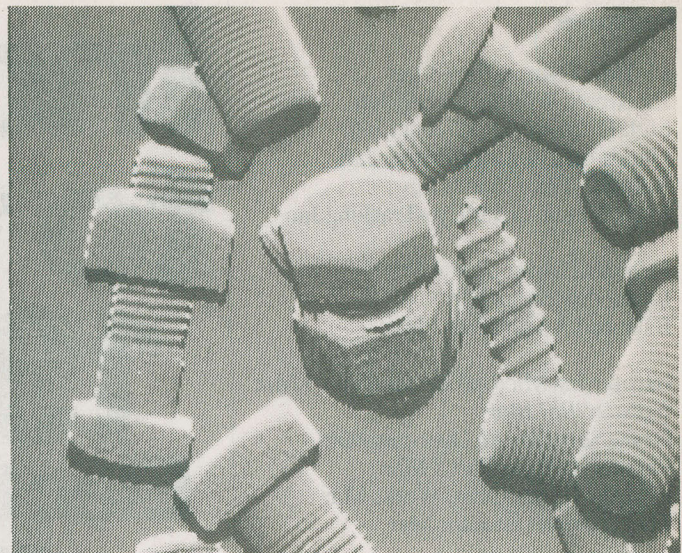

*Fig. 2. A three-dimensional image which was taken at the National Research Council of Canada laboratories employing a three-dimensional camera based on a synchronized laser scanner recently developed at the Division of Electrical Engineering.*


changes caused by acid deposition are largely reversible." The researchers based their conclusions on experiments conducted for the past four years under the Reducing Acidification in Norway (RAIN) project.

In the acid-exclusion experiment, the scientists studied a site in southern Norway that had been exposed to acid rain. They covered the site with a roof, shielding it from further acidic precipitation.

The scientists filtered the precipita-

tion that fell on the roof before distributing it to the water. They wrote in the *Nature* article that runoff has "begun to recover to preacidification chemical composition."

Can water and soil recover completely from the effects of acid rain? The scientists hope the Norwegian experiment — which agrees with previously conducted research in Canada, United States and Scotland — will provide the answer to that question in the future. ■

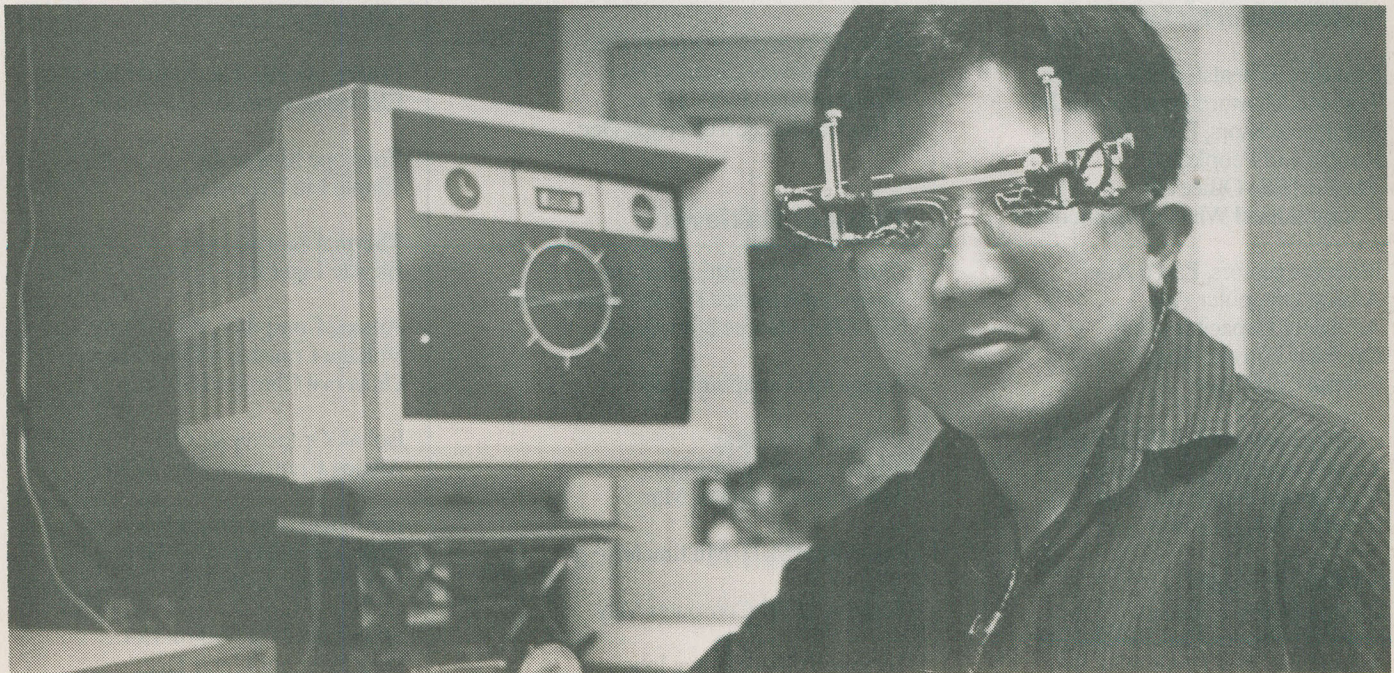

*Fig. 3. An eyeful — Bernard Zee, an electrical engineering graduate student at Texas A&M University from College Station, models the eyeglasses used in an eye-tracking device used to control machines including computer and robots.*



## Features

Physics of Music, Part 3 Jan  
Electronic Warfare and AI Jan  
SDI: Discovery and Debate Jan  
Hands-on Transistor Primer Jan  
Installing Fibre Optics Jan  
Flight Simulators & Eye-Tracking Jan

Physics of Music, Part 4 Feb  
Image Processing Feb  
Balanced Audio Lines Feb

Introducing Microprocessors, Part 1 Mar  
Index to 1987 Mar  
Home Security: An Overview Mar  
Physics of Music, Part 5 Mar  
How the RIAA Curve Works Mar  
The Slowpoke Reactor Mar

The Sine Wave Apr  
Physics of Music, Part 6 Apr  
Microprocessors, Part 2 Apr  
How VCRs Work Apr

Uninterruptible Power Supplies May  
A Visit to Trebas May  
Electrochemical Computers May  
Microprocessors, Part 3 May  
Unique Electronics Shockmount May

From Chaos to Order: AI Jun  
Microprocessors, Part 4  
Thermistor Applications Jun  
Guide to Cellular Phones Jun  
Audio Cassette Tape Test Jun  
Superconductor Kit Jun

Making a Wheatstone Bridge Jul  
Test and Measurement Special Jul  
Microprocessors, Part 5 Jul  
Robots and People Jul  
The Portable Office Jul  
Computerized Wheel Alignment Jul

Microprocessors, Part 6 Aug  
Analog Computer Aug  
All About Capacitors Aug  
Op Amp Tutorial Aug  
Coaxial Cable Aug

Controlling Pollution With AI Sep  
Troubleshooting Concepts Sep  
Microprocessing, Part 7 Sep  
Proximity Switches Sep

Satellite TV Update  
Electronic Solder Pastes  
Microprocessors, Part 8 (final) Sep  
Automotive Test Equipment Sep

# Index to the 1988 Electronics and Technology Today Issues

Basic Testbench Oct  
Canadian High Technology Show Oct  
Field Effect Transistors Oct  
Industrial Control with PCs Oct

Periodicity and Perception Dec  
Model Railway Circuits Dec  
Digital Storage in TVs Dec  
European Space Telescope Dec

## Product Reviews

Akai GX-8 Cassette Deck Jan  
American Reliance AR-140 Meter Jan  
NRI Micro Home Study Jan

Amiga 500 Computer Feb

Velleman Kits Mar  
Edukit Logic Tutor Mar  
Atari 1040 Computer Mar

Daetron MM100 Multimeter Apr

Toshiba T5100 Computer May

Tecmar VGA Adapter June

Amstrad PC1640 Computer Jul

ATI 2400etc Modem Aug  
CAT Image Scanner Aug  
Amiga Genlock Aug

Easyl Drawing Tablet Sep

Sony CDP707 CD Player Oct  
Stabilant 22 Oct  
Nissei FAX-305 Oct  
GW 543 Scope Oct

Fluke 80-series DMM Nov  
Amstrad PPC640 Computer Nov

Dell 220 Computer Dec

## Projects

Photoflash Trigger Jan  
Video Controller Jan

Accented Beat Metronome Feb  
Car Alarm Feb  
Audio Power Meter Feb

Logic Pulser Mar  
Hyper Fuzz Mar  
Easy Sine Generator Mar

Reaction Timer Apr  
Transistor Tester Apr

Pseudo Echo Unit May  
Capacitance Meter May

Programmable Thermostat Jun  
Electronic Combo Lock Jun

Envelope Shaper Jul  
Simple Lie Detector Jul

Thermal Alarm Aug  
Bicycle Light Backup Aug

Analog Computer, Part 1 Sep  
Voltage Controlled Filter Sep  
Universal Charger/PSU Sep

Isolink Optocoupler Oct  
Analog Computer, Part 2 Oct

Breaking Glass Alarm Nov  
Simple Metal Detector Nov  
Stereo Noise Gate Nov

Professional Car Alarm Dec  
Peak Program Meter Dec

**TO ORDER ANY OF THESE BACK ISSUES SEE PAGE 48**



NEW  
FROM THE  
CREATORS OF  
ALMOST FREE SOFTWARE

# ANNOUNCING THE EXECUTIVE SOFTWARE SERIES

If you own a PC, XT, or AT compatible microcomputer, you'll probably have heard about the power and economy of low cost public domain software and shareware. However, if you've ever tried to make sense of the thousands of cryptic programs available in the public domain, you might well have abandoned all hope of any of it ever being of much use to you.

We'd like to introduce you to our Executive Software Series... no fuss, no risk software. We'll make your computer dance... with no piper to pay. We sort through six to eight megabytes of public domain software to create one of these collections. We weed out the programs which don't work properly, the ones which just aren't suitable for business applications and the ones which contain computer viruses.

We're very, very good at spotting the latter. The result of our efforts is available on a disk for just \$19.95. Each volume of our Executive Software Series contains an assortment of utilities and applications which will make your computer work harder for you.

Executive Software Series disks provide you with programs that are up to date, virus free, business oriented, well debugged and well supported, and a complete volume... typically a one or two dozen separate business programs... costs less than a good lunch.

Finally, every Executive Software Series collection carries our promise of satisfaction. If you don't think it's fair value, we'll buy it back from you for every cent you paid for it.

## EXECUTIVE SOFTWARE SERIES VOLUME ONE

The first volume of our Executive Software Series is a collection of what we feel are essential utility programs for anyone using a PC in business. You probably won't need anything like all of these, but we're certain that there will be one or two that you won't be able to live without once you see what they can do.

All of these programs include detailed documentation files on the disk which will explain their operation to you. In addition, you'll have access to our telephone support service if you really get stuck.

**XWORD** is a program to translate text files created by one word processor into files compatible with any of several others. It supports WordStar, WordStar 2000, XYWRITE II Plus, WordPerfect, Multimate and SideKick.

**BANKER** will help you balance your checkbook... as much as anything short of divine intervention really can.

**APPBK** is a memory resident appointment book. It will remind you of things you have to do... just the program for users who get lost in their work.

**BROWSE** lets you scroll forwards and backwards through a text file just like you can in a word processor... without having to wait for one to boot up.

**CARDFILE** is a memory resident address book you can pop up from within any application. It'll even dial your phone for you.

**DCACHE** is a "disk cache". Install it in your machine and just about any program which uses your hard drive frequently will speed itself up noticeably.

**DELZ** is a very important security tool. The DOS DEL command doesn't completely destroy the contents of a file you delete, and potentially sensitive files can be brought back without your knowing it. This program quickly destroys all trace of a deleted file.

**DIRNOTES** allows you to affix notes and comments to any file on your hard drive... great for remembering what they are a few months later.

**DOSEDIT** is a must for every PC. If you type a command incorrectly under normal DOS you'll have to

retype it. With DOSEDIT installed, you can call back previous commands, edit them and use them again. Saves buckets of frustration.

**FREE** quickly tells you how much free space is available on any floppy or hard drive.

**FREEZE** locks up your PC while you're away from your desk, protecting your sensitive files from a quick disk copy while you're at lunch.

**KEY-FAKE** lets you bypass the start up screens of most applications by "stuffing" the appropriate keystrokes into your PC just before the application boots.

**LOCATE** will find any file on a complicated hard drive. Saves ages of directory changing and searching.

**LOCK and UNLOCK** allow you to encrypt sensitive files so that only you can get at them. Works with text files, spreadsheets, data bases... anything that can be illegally duplicated.

**NPAD** is a small, memory resident note pad you can pop up from within any application to jot things down on.

**POP-CAL** is a calendar which can be popped up from within any application. It will show you a correct calendar page from any month of any year from 1582 onwards.

**RENDIR** allows you to rename sub-directories as you currently rename files.

**RN** is a great little utility which will show you a map of the subdirectories of your hard drive and allow you change directories simply by pointing

Power users of PC, XT and AT compatible machines have known about these little programs for years. They're what transform a simple microcomputer into an extension of your fingers, without tying them in knots. If you don't buy another application in the next twelve months, make sure you own a copy of this collection.

You owe it to yourself to stop running up against the limitations of your equipment when our Executive Software can remove so many of them.

to the area you wish to log into.

**SETUP** sends control codes to your printer. It allows you to change fonts and effects with having to remember scores of obtuse escape sequences.

**SNIPPER** lets you copy the contents of any text screen into other applications. For example, you can extract part of a spreadsheet and pop it into a report being prepared on your word processor.

**SWEEP** lets you execute any command you like in every sub directory of your hard drive.

**TSR MANAGER** is a collection of utilities which will keep your pop up utilities, resident programs and other TSR's from rising up to consume you. Among other things, it lets you load in pop up programs and blow them away later on. It also includes several utilities which will help you identify TSR conflict problems.

**VTREE** is another of those essential little programs. It draws a map of the subdirectories of your hard drive.

**CONFIG** allows you to change the way your CONFIG.SYS behaves when your system boots up. For example, you can exclude specific drivers or commands to free up memory. This is extremely handy if you have a tape streamer, a LAN and a couple of other memory pigs in your system.

**READRITE** allows you to analyze how readable your writing is... as you write it. It pops up from within your favourite word processor and produces a readability index of the screen contents.

## EXECUTIVE SOFTWARE DISK OF THE MONTH CLUB

New Executive Software Series disks will be appearing roughly once a month. If your day is too full to allow you the time to order these disks, we offer you our disk of the month club service. Join the club, provide us with a credit card number and we'll automatically ship you each new disk, billing your account.

If you don't want to keep a disk, simply return it and we'll credit your card account.

This service places you under no obligation... you can cancel it whenever you no longer need it. However, it will save you valuable time and it will make sure you don't miss any of the powerful business utilities and applications which will be appearing on Executive Software Series disks over the next few months.

All club members will receive disks at the rate of \$19.95, or \$29.95 for two disk sets, for twelve calendar months, regardless of any price increases which may occur within this period.

To get on line with the Executive Software Series disk club, contact us by letter, phone, or FAX, or simply use the coupon below.

- ☐ Charge my Credit Card  
☐ Visa ☐ MasterCard ☐ AmEx

Account# \_\_\_\_\_

Expiry Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

Prov. \_\_\_\_\_ Postal Code \_\_\_\_\_

Signature \_\_\_\_\_

MOORSHEAD PUBLICATIONS

1300 Don Mills Road, North York,

Ontario M3B 3M8

(416)445-5600 FAX: 416-445-8149

FINE PRINT: This software has been collected from public access bulletin boards and/or has been placed directly in the public domain by its authors. It is all believed to be in the public domain, or offered as "shareware". As shareware, users of these programs are requested to pay registration fees to their authors, which may entitle you to additional updates, support and documentation. Note that the fee charged for this disk defers our cost in collecting and distributing the software only, it does not replace any requested shareware contributions. This will help to ensure a continuing supply of high quality shareware available at reasonable prices. If you try out this disk, and do not feel that it is fair value, you may return it for a refund or exchange it for a different disk with no questions asked. We do not sell software to people who cannot use it. If you have trouble with disk, you are welcome to call our free technical support service at (416) 445-5600 during normal business hours. Please be prepared to tell us the exact make and model of your computer and the disk and program you are having difficulty with. Please note that we cannot be responsible for any loss, damage or expense resulting from your use of this software, however caused. If you are unable to read your disk, it has probably been corrupted in the mail. You need not call us in this case. Simply return the disk to our software department with a note requesting a replacement. It will be shipped immediately. Please note that this disk does presuppose a reasonable familiarity with your computer. If you are very new to your system, we strongly recommend that you familiarize yourself with it before attempting to use almost free software.

THIS DISK IS ONLY \$19.95 (PLUS 8% O.S.T. & \$1.50 SHIPPING) FROM MOORSHEAD PUBLICATIONS  
1300 DON MILLS ROAD, TORONTO, ONTARIO M3B 3M8 PHONE: (416)445-5600 FAX: 416-445-8149  
PLEASE SPECIFY 5 1/4 INCH DISKETTES OR 3 1/2 INCH MICROFLOPPIES



# The Techie's Guide to C Programming

**Part two, in which Doctor Max O'Blivion locates an ancient map which promises of vast treasure and many parenthetical digressions. Danger lurks everywhere.**

STEVE RIMMER

A lot of very zen-like things have been said about programming in C language. I doubt that the greater part of them were original thoughts at the time — zen-like things rarely are. They're simply adapted from previously uttered zen-like things said about related subjects. This, to a large extent, further enhances the zen-like nature of their uttering, somehow suggesting the universality of all human experiences. After all, if you can say roughly the same thing about C language programming and ox gelding there has to be some sort of intelligent design to the universe.

This is how quite a few of those clever sounding slogans for coffee mugs and tote bags come to pass, methinks.

My favourite of these zen-like utterances, which I think I mentioned last month, is the all but immortal "real men don't use Pascal". Add to this that no one over the age of four programs in BASIC and that only people who like pain enjoy assembler and there's little left. We'll discount the yuppie languages like Forth, Ada, COBOL, SnoBOL, Fortran, BLINK, Yawn, gROUCH and Queeg for the moment.

As the gods have clearly indicated

that C is *their* preferred way of dealing with computers, one can do little else but get on with it. As such, in this feature we're going to look at a few new aspects of the language and learn a bit more about compilers.

## How To Kill Cats Quickly

The structure of C programs can be a bit elusive until your brain attaches itself to the nature of the language. It's helpful to remember that everything under C ultimately represents some sort of value, with the largest part of what you find in the average program representing an integer.

This program will echo everything you type on your keyboard to the screen. Let's see how it works.

```
main( )
{
while(putch(getch( ));
}
```

Anyone with an ounce of common sense, or a millilitre of common sense if you've caved in and gone metric, will see that this works by black magic, and that there's little sense in any further discussion. Fortunately, few people willing to invest several thousand dollars in a television

set that only displays letters can be said to be that sensible, so we'll press on.

It will be helpful to start by knowing that *putch*, as we saw last month, will take the character passed to it and print it to the screen of your computer. Thus, if we said *putch(65)*, the letter *A* would appear on the screen, the number sixty five being the ASCII code for the letter *A*. Under C, by the way, we could also say *putch('A')*. A single character in single quotes will be interpreted by C as working out to a numeric value, rather than as a string.

Note that we can only pass *putch* numeric values — ASCII codes — not strings. It prints one character at a time.

The *getch* function is another thing which is built into C. When you call *getch* your program will wait until a key is pressed on your keyboard and it will "return" the ASCII code when *getch* returns. This may be a bit confusing.

This program calls *getch*.

```
main( )
{
getch( );
}
```

In this case, *getch* waits for a key press



# NRI's new at-home training gives you the computer, the software, and the hands-on skills to start a high-paying career as a computer programmer

Now NRI gives you hands-on experience in computer programming with a powerful IBM-compatible computer system and software you keep. One easy step at a time, you build full-featured, powerful programs in BASIC, Pascal, C, and COBOL—today's hottest computer languages. One easy step at a time, you train to be a high-paid computer programmer!

**Your NRI training includes a computer, modem, and invaluable programming software you keep**

Unlike any other course, NRI's at-home training in Computer Programming gives you hands-on experience with a powerful, IBM-compatible Packard Bell VX88 computer system, including 2400 baud internal modem, 512K RAM, disk drive, and invaluable programming software—BASIC, Pascal, C, and COBOL—all yours to keep.

With NRI, you get the skills and the confidence, the computer and the software to build real-world, working programs for a wide variety of business, personal, and professional applications . . . in all, everything you need to step into today's top computer programming jobs.

## **No previous experience necessary**

No matter what your background, NRI ensures you get the know-how you need to take full advantage of every exciting opportunity in computer programming today.

With your experienced NRI instructor always available to help, you quickly cover the fundamentals, then



Carl Barone  
Programmer/Analyst  
NRI Schools

move on to master all four of today's key computer languages—BASIC, Pascal, C, and COBOL—step by easy step. Before you know it, you have what it takes to handle any programming problem you're likely to encounter in your professional career.

**Now, as never before, you can succeed as a computer programmer**

The best news comes from the Bureau of Labor Statistics: As a programmer trained in a variety of computer languages you

can land the programming position of your choice—even make it on your own as an independent programmer. There's no doubt about it—with NRI's complete, at-home, four-language training in Computer Programming, you can write your own ticket to success in this high-paying, top-growth computer career field!

**See other side for highlights of your NRI hands-on training in BASIC, Pascal, C, and COBOL** →

## SEND CARD TODAY FOR FREE NRI CATALOG

☒ **YES!** Please rush me my FREE catalog describing NRI's at-home training in Computer Programming.

Name \_\_\_\_\_ Age \_\_\_\_\_  
(please print)

Street \_\_\_\_\_  
Telephone \_\_\_\_\_

City/Prov./Code \_\_\_\_\_ 5416-029

**Your NRI training in computer programming includes an IBM-compatible Packard Bell VX88 computer with internal modem, 512K RAM, disk drive, monitor, and programming software—BASIC, Pascal, C, and COBOL—all yours to keep!**






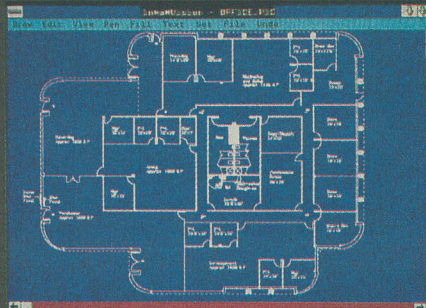
# Now, with NRI, you can learn to program in today's hottest computer languages— BASIC, Pascal, C, and COBOL




You start with BASIC, an extremely popular language used for graphics, teaching, personal, and small business applications.



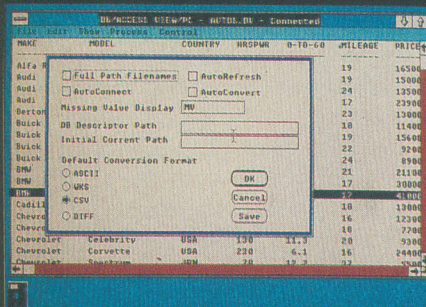Next, you master Pascal, a multipurpose language often used to develop software for computer-aided design (CAD).



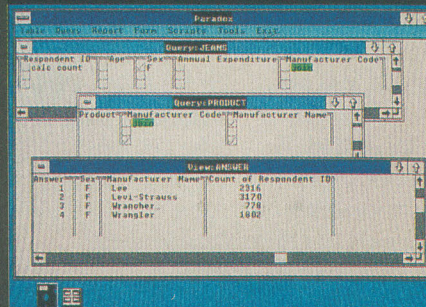You move on to C—hands down, today's hottest computer language—used for everything from systems programming to artificial intelligence.



You wrap up your training in programming with COBOL, the language of business and the most widely used computer language in the world.

NRI's new at-home training in Computer Programming starts by walking you step by step through the fundamentals, easing you into programming with brilliantly detailed instructions, charts, and diagrams.

In no time at all, you have a complete understanding of the programming techniques used every day by successful micro and main-frame programmers. And then the fun really begins.

With your personal NRI instructor on call and ready to help, you use the computer system included in your training to actually design, code, run, debug, and document programs in BASIC, Pascal, C, and COBOL. Then, following easy-to-read instructions, you use your modem—also included—to “talk” to your instructor, meet other NRI students, even download programs through NRI's exclusive programmers network, PRONET.

**Send for your FREE catalog today**

For all the details about NRI's at-home training in Computer Programming, send the postage-paid reply card today. Soon you'll receive NRI's fascinating, information-packed, full-color catalog.

Open it up and you'll find vivid descriptions of every aspect of NRI training. You'll see the IBM-compatible Packard Bell computer included in your course up close in a special, poster-sized foldout section. And, best of all, you'll find out how your NRI training will make it easy for you to build a high-paying career—even a business of your own—in computer programming.

If the card is missing, write to NRI at the address below.


IBM is a registered trademark of the IBM Corporation

**SEND CARD TODAY FOR FREE NRI CATALOG**

**Business  
Reply Mail**

No Postage Stamp  
Necessary if mailed  
in Canada

Postage will be paid by

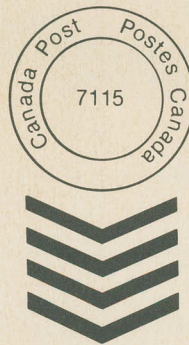

**NRI SCHOOLS**

McGraw-Hill Continuing Education Center  
330 Progress Avenue,  
Scarborough, Ontario  
M1P 9Z9



**NRI**  
**School of Computer Programming**

McGraw-Hill Continuing Education Center  
330 Progress Avenue  
Scarborough, Ontario M1P 2Z5





and the program ends and returns to DOS. The actual value of the key hit gets thrown away, as there's nothing to catch it.

In this case, something more happens.

```
main( )
{
  int i;

  i=getch( );
}
```

This program assigns the value returned by *getch* to the integer variable *i*. However, nothing happens to *i* in this program either.

In theory, every function under C returns something. Much of the time this returned value is of no use to us, and we ignore it. In the case of *getch*, we may or may not use it for anything, depending on whether we're using *getch* to wait for a key press or actually to see which key has been belted.

Let's expand the program a bit further.

```
main( )
{
  int i;

  i=getch( );
  putch(i);
}
```

This program will get a keyboard character and print it to the screen. It waits for a key press with *getch*, assigns the keyboard character to *i* and then uses *putch* to send it to the tube.

We can write this another way.

```
main( )
{
  putch(getch( ));
}
```

Daring souls who've been awake for a few hours might well ask where the integer went. It's still there, sort of. It's just hiding in the depths of C.

In order to properly understand this latest example, we have to know before hand that presented with a set of nested functions like this, C will always resolve the innermost one first. In this case, it will execute *getch* first, derive its returned value... a character code... and then execute *putch* with the returned value of *getch* passed to it. The program itself will create a place to store the returned value of *getch* in the in-

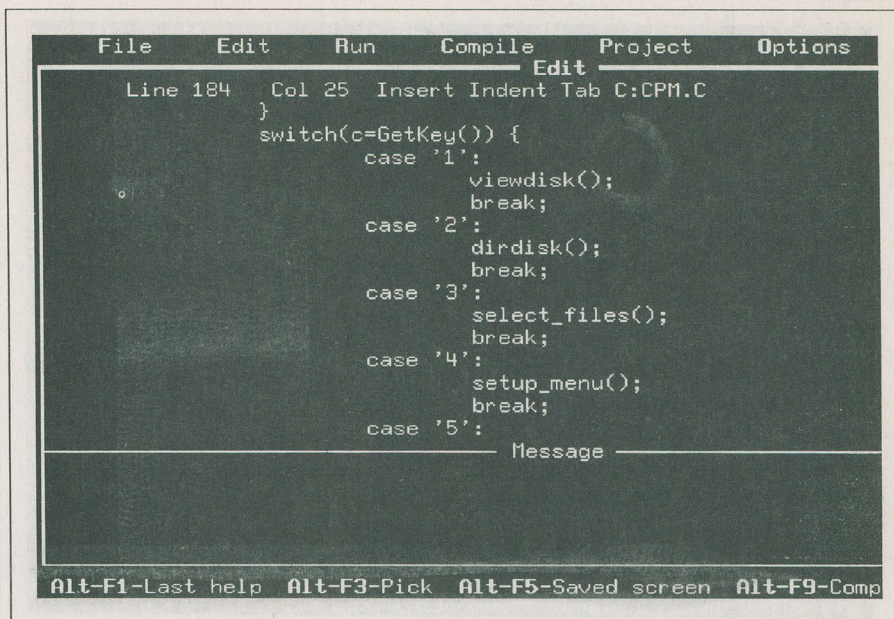


Figure 1. This is an example of a switch statement... or part of one... in a real C program being developed in Turbo C. The *GetKey()* function is an expanded version of *getch*, discussed in this article.

terim. Variables that appear and disappear for these sorts of purposes are called "temporaries", and, as we'll see a bit later in this series, we can often use them to make C do very clever things.

As we noted last month, the *while* statement under C will execute something repeatedly until the condition it's testing becomes false, that is, until it is zero. Thus, this line will execute forever

```
while(1);
```

and should probably be avoided unless you just happen to like rebooting your computer.

This line... as seen in the first example we looked at, actually... will also execute forever.

```
while(putch(getch( )));
```

but at least it'll do something. This will cause *getch* and *putch* to be called repeatedly, echoing what you type to your tube. Actually, you can break out of this loop on a PC by hitting control break.

As it turns out, this isn't really a perfect dumb typewriter program. For example, if you hit *Enter*... a carriage return... the cursor will go back to the beginning of the current line, not down to the start of the next one, as is usually the case when one hits *Enter*. The reason for this is that

C... and your PC... interpret a carriage return literally. The cursor simply returns to the start of the current line. We're used to hitting *Enter* and having DOS or whatever we're typing into issue both a carriage return and a line feed.

## Alien Swamp Monsters

Let's change our program a bit. This is how little, elegantly simple programs quickly swell into huge, multi-headed alien swamp monsters that engulf whole mid-Western American towns. What fun...

```
main( )
{
  int i;

  while((i=getch( ))) {
    putch(i);
    if(i == 13) putch(10);
  }
}
```

There's a lot of new stuff happening here. First off, as you'll notice, we're back using a variable once more. Again, we're testing the returned value from *getch* for the validity which drives our *while* loop — not all that sensible, as you can't actually type character zero at the keyboard to end the loop, but never mind that for now.

The line after the first *putch* is an example of an *if* statement in C. This says



# The Techie's Guide to C Programming

```

File      Edit      Run      Compile      Project      Option
Edit
Line 28    Col 33  Insert Indent Tab C:CPM.C
#define version      0
#define subversion    8

#define HOME          71 * 256
#define CURSOR_UP     72 * 256
#define PG_UP         73 * 256
#define CURSOR_LEFT   75 * 256
#define CURSOR_RIGHT  77 * 256
#define END           79 * 256
#define CURSOR_DOWN   80 * 256
#define PG_DOWN       81 * 256

#define logical_sector 128      /* size of a CP/M lo
#define format_ext     "CPM"    /* extension for for
#define config_file    "CONFIG.CFG" /* name of configura
                                Message
F1-Help F5-Zoom F6-Message F9-Make F10-Main menu

```

Figure 2. Here are some actual uses of the `#define` directive in a C program. Note that they define not only numeric values, but strings as well. This program, in its entirety, translates CP/M diskettes into PC ones.

that if the value of *i* is thirteen, the program is to print character ten as well. If we bear in mind that the ASCII code for a carriage return is thirteen and that of a line feed is ten, the purpose of this line becomes pretty obvious. It causes every carriage return to be followed up by a line feed.

However, the way we test the value of *i* may seem a bit odd. In BASIC, equal signs can be used in two ways. We might say `A=21` to assign one thing to another thing. We also might say `IF A=21 GOSUB 1000` to test the value of a thing. Under C, we differentiate between these two uses.

If we say `a=21` under C, this can only mean that the variable *a* is being assigned the value twenty one. If we wish to test the value of *a*, we must use two equal signs, as in `if(a==21)`. This makes C happy... don't argue with it.

Smart compilers, knowing the propensity of the human digit to miss keys whilst typing more rapidly than the human brain can properly think, check to make sure that these two uses are not interchanged. For example, if we say `while(i=getch( ))`, a good compiler will complain, as this is ambiguous at best. What we want to do, in fact, as we've seen in the example above, is to assign *i* the return value of `getch` and then test the

value of *i* to see if it's true. However, this could also mean that the `while` statement is to regard things as being true so long as the value of *i* is the same as that of the return value from `getch`, which is very clearly not what we want to do.

For this reason, the contents of the tested part of the `while` loop above is enclosed in an additional set of parentheses to force C to evaluate it first and remove the ambiguity.

We might improve this line, actually, and we'll see how the two uses of the equal sign are properly employed. If we change the line with the `while` loop to

```
while((i=getch( ))!= 27) {
```

we will have modified to program to allow for an escape clause — quite literally. This means that the `while` loop should assign *i* the value of `getch` and keep looping so long as *i* does not equal twenty seven. This is the value returned when you hit the escape key. As such, hitting `Esc` will end the program.

The exclamation point is something different as well. When we wish to see if one thing equals another, we use two equal signs. We when wish to see if one thing does not equal another, we use an exclamation point and an equal sign.

There's another problem with this

program. We can't backspace. We also can't deal with tabs. We need more `if` clauses. This is going to start getting a little messy.

Having to program many possible reactions to the value of something, depending on the value, is something which happens quite commonly. As such, C provides us with a very elegant... and somewhat daunting... construct called the `switch` statement. This allows us to do away with a lot of `ifs`, as well as tightening up our code a bit in the bargain.

Let's rehash the program once more.

```

main( )
{
    int i;

    while((i=getch( ))!= 27) {
        switch(i) {
            case 8:
                putchar(8);
                putchar(32);
                putchar(8);
                break;
            case 9:
                printf(" ");
                break;
            case 13:
                putchar(13);
                putchar(10);
                break;
            default:
                putchar(i);
                break;
        }
    }
}

```

I said it was daunting. With each iteration through the `while` loop, the `switch` will evaluate the contents of *i*. If it matches one of the three specific cases we've set up — eight is a backspace character, nine is a tab and thirteen is, as we've seen, a carriage return, it will do whatever is in those cases. Otherwise, it will execute the `default` case, which is simply to print the character to the screen.

The word `default` here is a specific case defined by C. You have to have it called `default` in order for it to behave as a catch all for numbers that don't conform to any of the other, specific cases.

Each case starts with the `case:` statement, naturally enough, and ends with a `break;`. The `break` tells C that the case is done with, and that it should skip ahead to the end of the switch immediately. If you leave the break statement off, C will execute the contents of the next case in the

Continued on page 58



# ALMOST FREE SOFTWARE VOLUME 4

*If it's getting dark and cold around your digs right now, you probably need this collection of almost free software. Pop it into your disk drive and you'll be able to mix yourself up a Depth Charge... or a Flying Scotsman... or a Chelsea Sidecar... three of the many drinks contained in our electronic bartender. While you're getting warmed up, you can go quietly mad playing Son of Tetris. When you can't think anymore, you'll be able to warp out of your dimension watching our electronic pyrotechnics.*

**BCOPY** is one of the cleverest copying programs around. It hides in the background while it's working, so that immediately after issuing a copy command your DOS prompt returns and you're ready for whatever's next. A great little time saver.

**BDS** is a slick pop up electronic engineer's calculator. It handles things like wavelength, capacitance, radio equations and so on.

**CALCQF** will analyze your system and figure out how much you can speed things up by changing the refresh rate of your memory... without crashing your machine. Then it will generate a small COM file to include in your AUTOEXEC file.


**JIVE** translates any English text into... jive.

**LUM** is a sophisticated sideways printing program which is great for spreadsheets or any application wherein regular paper just isn't wide enough. It supports multiple fonts, effects and so on. Requires an Epson FX-80 compatible printer.

**NJFRERAM** will show you how much free memory you have from moment to moment up in the upper right corner of your screen. Great for spreadsheet users, amongst others.

*There's a lot more in this collection... practical programs to speed up your system and even give you a few more pop up windows. This disk will tickle the fancy of anyone who's even considered using a PC.*

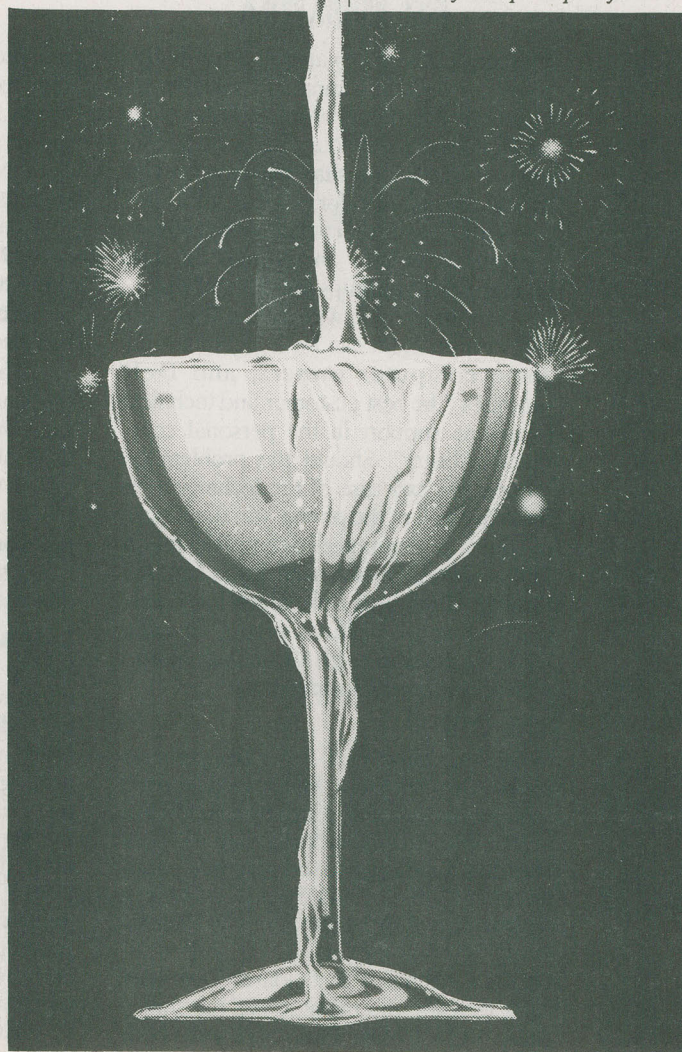*These programs have been scrupulously checked for viruses, trojans, worms and other nasties. If you have any problems with them, you'll find our technical support service ready to help. Finally, as always, if you don't like the disk once you've checked it out you can return it for a prompt refund.*



**ORDER** changes the order in which files come off your disk when you type DIR. This allows you to pre-sort your directories, or adjust them in any order you like to make frequently used programs boot more rapidly.

**PYRO** we've had fireworks programs before... but this is the best. It does EGA fireworks, complete with sound effects, and is truly glorious. Includes C language source code. EGA/VGA card required.

**SOT** is the son of Tetris, the addictive game from the Soviet Union. This one is even more devious.

**STYLIST** is an essential tool for any Ventura Publisher user. It allows you to edit, manipulate and print out any style sheet.

**TONTO** is a SideKick-like program with a host of features, including a clock/calendar for any year since the middle of the sixteenth century, an ASCII chart and a printer setup program.

**MR BOSTON** is the ultimate bartender. It holds recipes and complete directions for zillions of mixed drinks... from the common to the delightfully bizarre... and provides you with an outstanding user friendly program to access and even add to the list.

FINE PRINT: This software has been collected from public access bulletin boards and/or has been placed directly in the public domain by its authors. It is all believed to be in the public domain, or offered as "shareware". As shareware, users of these programs are requested to pay registration fees to their authors, which may entitle you to additional updates, support and documentation. Note that the fee charged for this disk defers our cost in collecting and distributing the software only, it does not replace any requested shareware contributions. This will help to ensure a continuing supply of high quality shareware available at reasonable prices. If you try out this disk, and do not feel that it is fair value, you may return it for a refund or exchange it for a different disk with no questions asked. We do not sell software to people who cannot use it. If you have trouble with disk, you are welcome to call our free technical support service at (416) 445-5600 during normal business hours. Please be prepared to tell us the exact make and model of your computer and the disk and program you are having difficulty with. Please note that we cannot be responsible for any loss, damage or expense resulting from your use of this software, however caused. If you are unable to read your disk, it has probably been corrupted in the mail. You need not call us in this case. Simply return the disk to our software department with a note requesting a replacement. It will be shipped immediately. Please note that this disk does presuppose a reasonable familiarity with your computer. If you are very new to your system, we strongly recommend that you familiarize yourself with it before attempting to use almost free software.

THIS DISK IS ONLY \$19.95 (PLUS 8% O.S.T. & \$1.50 SHIPPING) FROM MOORSHEAD PUBLICATIONS  
1300 DON MILLS ROAD, TORONTO, ONTARIO M3B 3M8 PHONE: (416)445-5600 FAX: 416-445-8149  
PLEASE SPECIFY 5 1/4 INCH DISKETTES OR 3 1/2 INCH MICROFLOPPIES



# Dell 310

**A hot 386 and novel marketing plan bring you leading-edge computing economically.**

**BILL MARKWICK**

**W**hen you're working with a program that does a lot of calculating or video image painting, such as CAD or desktop publishing or spreadsheets, you've probably looked longingly at the 80386 machines on the market.

Today's complex programs can make the PC, XT or even the AT look like a turtle. The hidden-line-removal function of AutoCAD, for instance, makes them look like a turtle that's been bound and gagged.

The 80386 is Intel's answer to the demand for more speed and flexibility in personal computing; with a 32-bit bus structure, a clock speed of 16 to 25 megahertz (depending on price) and the ability to address huge amounts of memory, it's capable of running behemoth programs (or several) at speeds that don't require you to play Solitaire during loading and calculating.

Of course, there's the Number One axiom of all leading-edge technology: *it's gonna cost ya*.

Dell Computer Corporation, originally from Texas, set out to build a high-quality line of 286 and 386 computers that could be compared favorably to the best on the market, and at the same time do something about keeping the price down. They've certainly succeeded on both counts.

## **Direct to Your Door**

Dell's marketing intent was to eliminate the expensive chain of dealers by selling directly to you. The comprehensive list of options lets you choose the computer of your dreams from the many possibilities: the base model is an AT-compatible 80286 at 12.5 or 20MHz, with 80386 models at 20 and 25MHz. The drives available are 3.5" or 5.25" floppies, plus hard drives of 40, 90, 150 and 322MB. The base memory on the 386 machines is 1MB, expandable to 16MB with memory modules in increments of 1, 2, 4 or 8MB.

All machines have a VGA video

board that's compatible with CGA software, and the monitors available are monochrome, monochrome VGA, colour VGA and VGA Colour Plus (which has a finer dot pitch for a sharper image). VGA drivers are included for popular software.

Other options include a Microsoft-compatible mouse, an internal modem, and tape drive backups for the hard disk.

Getting stuck with a hardware or software problem can be a nightmare for some computer owners, and Dell promises "the best customer and technical telephone support in the personal computer industry". Should the problem go beyond the expertise of the technician on the other end of the phone, you don't have to ship your computer back to Richmond Hill or Texas. On-site servicing is handled through Honeywell Bull, which has a network of service offices across Canada. Dell systems come with a 12-month on-site service contract as standard.

## **The 310**

When we asked Dell for a computer to review, they must have had spies dig up my wish list, because they sent a System 310. It's a 386 20MHz motherboard with 1MB of RAM as standard, two serial ports, 1 parallel port, 1 3.5" 1.44MB drive, 101-key keyboard, a 200W power supply, Phoenix BIOS, six 16-bit expansion slots and two 8-bit slots. All this was standard. Then they went to town: the monitor was the super-sharp VGA Colour Plus, there were both 3.5" and 5.25" floppy drives, the hard disk held 150MB, and the motherboard contained an 80387 math coprocessor and 4MB of RAM in total. A mouse plugged into COM1.

The software Dell offers with the systems consists of MS-DOS 3.3 or 4.0 (both enhanced Dell versions), or Microsoft OS/2. *Windows/386* is also available. The review model had all of the above except DOS 4.0.

When it comes to prices, we asked for

and received a thorough price list just in time for it to become obsolete; the Free Trade agreement was whizzed through at a speed never before seen in government work except maybe for collecting taxes, and computers made in the US were the first to be exempted from duty. As a result, prices quoted here were revised and accurate when we went to press, but don't be surprised if there are minor changes here and there.

The base price for the computer and keyboard, with one diskette drive and no hard drive, was \$4299. With the 150MB drive and Colour Plus monitor, the basic system becomes \$8249. Software such as OS/2, enhanced DOS, etc., is optional. If you comparison shop, I think you'll find this a substantial saving over comparable computers such as Compaq or IBM PS2.

## **Unpacking**

Setting up was straightforward and takes minutes. Loading the software onto the hard disk is simplified by the enhanced DOS, which has a Dell utility to do the formatting and partitioning for you. There are quite a few enhancements with DOS, including a disk cache to store frequently-used disk accesses, and Cruise Control from Revolution Software, which gives very good control of the cursor speed while preventing overshoot. There is also a diagnostic disk that lets you check just about every function in the computer.

The Dell 310 is fairly large and heavy, unlike their 200-series, but then it holds a lot (and does a lot). It boots up quickly and quietly; our model held both MS-DOS 3.3 and OS/2, and the computer lets you choose which you want by pressing ESC for DOS. If you don't press anything, the default is OS/2.

I loaded in all the software I could think of and spent a pleasant few days watching things run the way they were meant to. Xerox Ventura desktop publishing software seemed to fill screen after



screen instantly; the 386 finally gives you the power to compute as fast as you can go instead of waiting around for the video section to repaint the image.

AutoCAD, that cumbersome sloth of a program (powerful though it may be) comes to life with the Dell 310. I ran Release 9, which requires the horrendously expensive math coprocessor (\$999.95). At last the fear of the dreaded Regeneration is over. The AutoCAD drawing of St. Paul's cathedral, for example, regenerated in five seconds compared to 30 on my 8MHz 8086. Only the hidden line removal could slow it down: five minutes to produce St. Paul's in hidden-line 3D, compared to enough time to grow a beard with a PC compatible. Incidentally, the Dell mouse, which is made by Logitech and is compatible with the Microsoft driver, is very fast in action, but absolutely precise; it needed only a six-inch square on the desk for perfect results with all programs that used it.

Those of you who are addicted to the Microsoft/Sublogic Flight Simulator have no idea at all what awaits you when you throttle up with a 386, EGA or VGA monitor, and Version 3.0. This is the undisputed King of Simulators. The scenery is sharp and clear instead of jagged wiggling lines, and it unrolls in front of you with movie-film smoothness. The instrument panel is razor-sharp and the colors are beautiful (try a dusk flight over Chicago or the Golden Gate). The Learjet is smooth as silk, instead of lurching out of control from overshoot as it does on slower machines. The Atari and Amiga versions don't even come close.

The much-heralded OS/2, introduced by Microsoft as a replacement for MS-DOS, is like an enormously powerful sportscar for which you can't find the keys. There's no software for it yet — it's a Catch-22 situation in the beginning: you have to produce the system first in hopes that people will write programs for it, but software firms might want to wait until it's popular, which it won't be with no software... Actually, the power of OS/2's multitasking, with each application (including MS-DOS) getting a "computer" of its own, should prove irresistible. 1989 is said to be

the year when we'll start seeing applications.

Just to say I tried it, and to get a taste of its power, I ran MS-DOS as an application under OS/2. The Ctrl-Esc keys let me toggle back and forth between the OS/2 prompt and the DOS program.

Microsoft *Windows386* is a cross between DOS commands and the icon system used by the Macintosh. It lets you load several programs at the same time, and DOS commands are selected from pulldown menus by using the mouse. It's very convenient and tremendously power-

formance, etc., that benchmark programs often give misleading numbers, depending on what task they have the computer do. For example, Norton's SI, long a standard, gives a rating of 24.2, implying that the 310 is 24 times faster than a PC. From timing various bits of complex software, I'd say that ten times is a more realistic figure. Still, SI at least gives a figure that can be used to compare similar systems, and the 310 is the same as the Compaq Deskpro 386/20 and faster than the IBM Model 80/20. It's also faster than either of these with memory tests (PC Labs test) and CPU performance (4.72 million instructions per second, or MIPS — Power Meter test).

The Zenotest software I use to test video speed gave a result of 18, certainly the fastest of any I've tested so far. The Zeno program can move the video BIOS instructions from slow ROM to faster RAM, giving a speed increase of three times, but the Dell's scrolling is practically instantaneous as it is. Type DIR and try to read the files as they fly by.

## Conclusion

The 310 proved to be flawless in operation. It's superbly fast (ask them about the Dell System 325 if it's not quite fast enough for you — it runs at 25MHz) and hugely versatile when it comes to expansion. The ship-direct marketing means a considerable saving over the competition (and very high quality competition it is). Despite the fact that folk wisdom holds that computers are obsolete as soon as they're off the drawing board, I think it's safe to say that the Dell 310 will keep you satisfied for years.

Incidentally, computer manufacturers may not be aware of a clause in the Free Trade agreement. Somewhere in the fine print, it says that they're required to supply journalists with a free 386 system sometime during 1989. I'll just hang on to this Dell 310 to save them the trouble of shipping me one... ■

For further information, contact Dell Computer Corporation, 2 East Beaver Creek Road, Richmond Hill, Ontario L4B 2N3, (416) 881-3513, or toll-free 1-800-387-5752, or FAX (416) 881-3513.



ful, but very difficult to set up for the novice. Once you spend some time learning how to configure the files to keep it happy, it greatly simplifies working with large numbers of files and directories (something you'll soon have with a 150MB disk).

## Benchmarks

I've always been leery of benchmarks. The speed of a computer is so dependent on so many different things, such as bus structure, video scrolling, memory access, math per-



# Simple Codelock

A simple, secure electronic lock release for cars or other uses.

JERRY PENNER

It seems that it's a whole lot easier to lock your keys into your car these days. Automobiles with power locks seem to invite you to do so with open(?) arms. Well, I don't like the way my locksmith snickers and I hate to see anyone get rich from my misfortunes. What I needed was a simple electronic codelock that wouldn't take up too much room or money, or destroy the appearance of my vehicle, but

## PARTS LIST

### Resistors

All .25W, 5%

R1.....47k  
R2.....47k  
R3.....200k  
R4.....1k

### Capacitors

C1 470uF 20V electro.

### Semiconductors

D1.....1N4001 rectifier diode  
IC1.....741 opamp  
Q1 2N6386 NPN 40V 8A Darlington transistor

### Switches

S1.....SPDT momentary switch

### Miscellaneous

Wire, project box, nine momentary switches or keypad

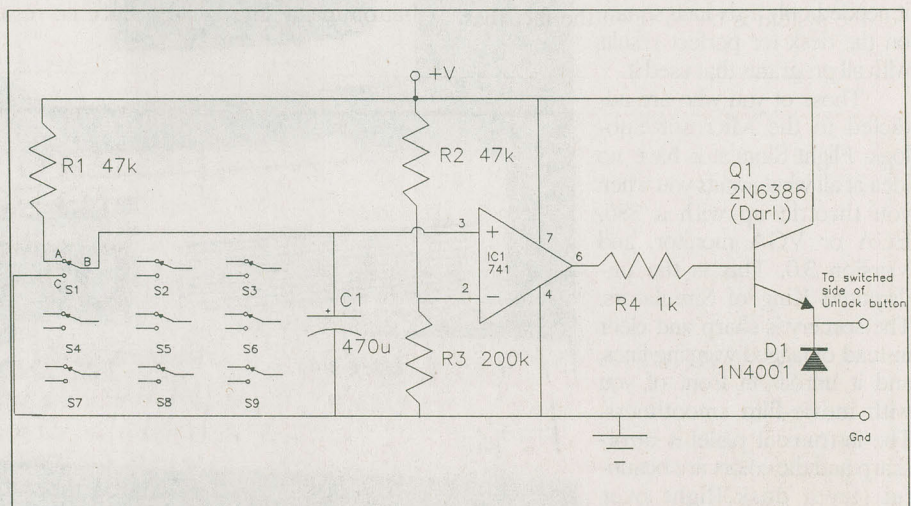


Fig. 1. The schematic of the codelock circuit.

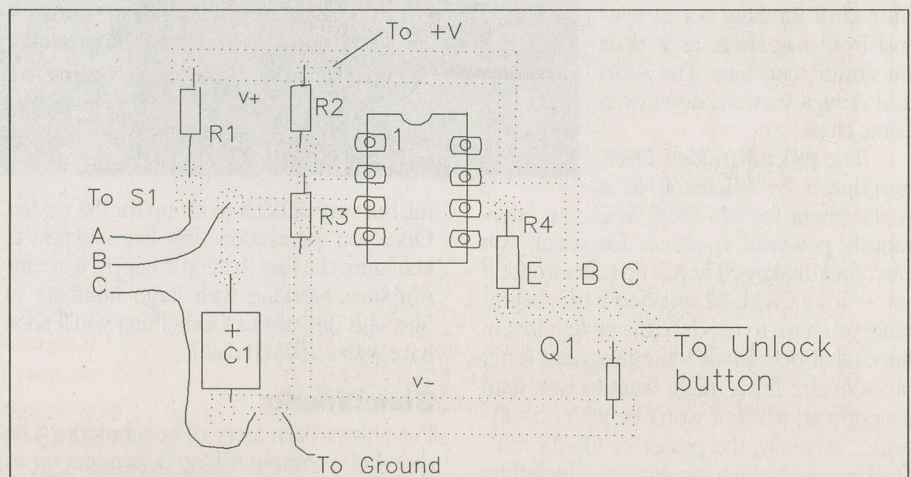


Fig. 2. The parts location, shown enlarged, component side.



would maintain an adequate amount of security. The circuit described here fits the bill perfectly and can be used in a host of other security applications.

### How It Works

The circuit in Fig. 1 compares an RC divider network to a resistor network. When S1 is depressed, C1 charges through R1 and sets the output of IC1 high when the voltage across C1 exceeds the voltage across R3. This takes about 1.5 RC time constants and with the values given comes to about 30 seconds. The timing is unaffected by supply voltage since both the RC divider and the resistor divider reference from +V. This means that as long as the supply voltage is sufficient to operate the op amp, the length of time S1 must remain activated will remain constant. The output of IC1 controls Q1, which parallels the controlled side of the 'UNLOCK' button in the car. The security of the system is based upon the fact that

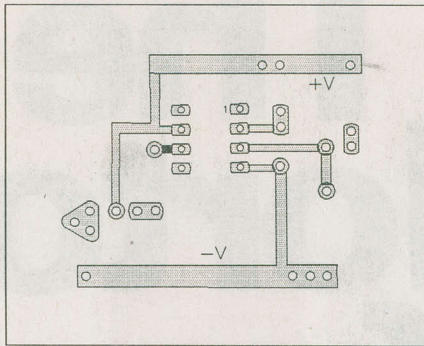


Fig. 3. The printed circuit board, foil side.

anyone seeing a matrix of nine switches will assume it is the front end of sequential-push code lock. Simply pushing any button will do nothing. Pushing the active button for less than the proper time will produce no result, since C1 will discharge when S1 is released. Pushing the active button many times will produce no result


for the same reason. Since the circuit activates on time rather than sequence, hiding the active button in an unlikely place will provide protection against unauthorized entry as well.

### Construction

Construction may be by the method of your choice, but either PC board or perfboard is recommended to keep everything neat. See Fig. 2 for the component layout. Be sure of the wiring of S1 or else the lock may activate itself about 30 seconds after power is applied. Remember that if S1 is going to be exposed to the elements, a weatherproof switch should be used and the connections siliconed.
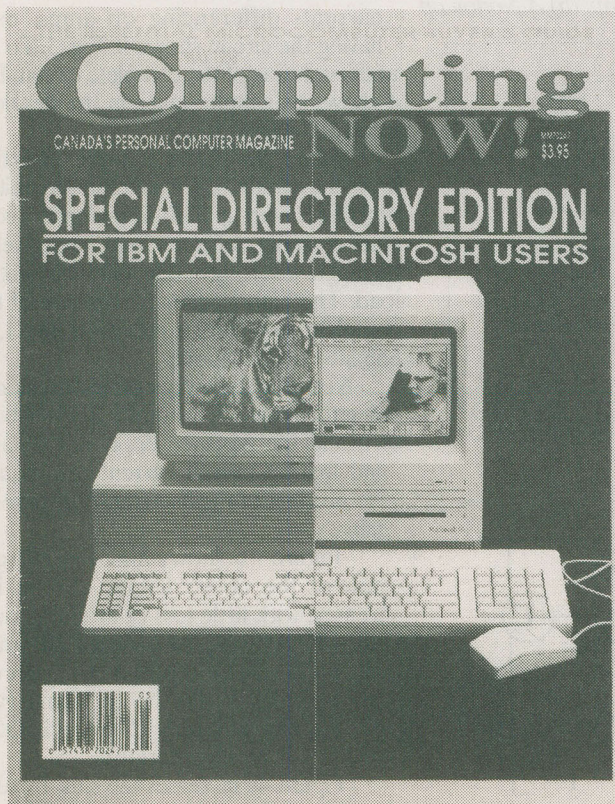
### Getting In

So go ahead, lock your keys in your car; it doesn't matter anymore. It will take you less than a minute to get into your vehicle and you don't have to pull out your hair or your wallet to do it. ■



## THIS MAY, THINGS ARE GOING TO BE A LITTLE BIT DIFFERENT!

Oh, yes — we will be publishing our massive DIRECTORY OF IBM AND MACINTOSH PRODUCTS, just as we have for the past three years.

And: just as in past years, the May issue will be the most complete guide to all the latest and the greatest — a compendium of all the stuff you need, the stuff you want, and all the rest that's just too fascinating to leave out.

However: the 1989 Computing Now! Directory will focus in directly on Canadian sources — the places you can go, and the folks you can ask about the products you've got to find.

This year, it's going to be more useful than ever. Don't miss it.

### THE ANNUAL COMPUTING NOW! DIRECTORY OF IBM AND MACINTOSH PRODUCTS

Coverage will include: communications software, desktop publishing equipment, disk drives, display adaptors, data managers, financial software, games, graphics, I/O interfaces, memory expansions, monitors, modems, networks, printers, programming, languages, project managers, spreadsheets, starter systems, high-end systems, word processors... and a lot more!

Information will be arranged by supplier, with extensive cross-referencing by product category.

For subscription information call (416)445-5600 or Fax (416)445-8149.

For advertising information contact David Stone.



# The Norton Difference

A guide to the underused Norton differencing op amp.

RAY MARSTON

**M**ost popular op amps (Fig. 1a) give an output proportional to the difference between their two input terminal voltages and are thus known as voltage-differencing amplifiers or VDAs. There is however a type of op amp which gives an output voltage proportional to the difference between the *currents* applied to its two input pins. These devices are known as *current-differencing amplifiers* or CDAs. Figure 1b shows the standard symbol of the CDA, also known as a Norton op amp.

The two best known Norton op amps are the LM3900 and the LM359. The LM3900 is a low-cost medium performance IC that houses four identical op amps in a 14-pin PIL package (Fig. 2) and can operate from a single-ended 4–36V power supply. Each of its op amps has a unity-gain bandwidth of 2.5MHz with an open-loop gain of about 70dB, and gives a large output voltage swing. This IC is particularly useful in DC and low frequency applications where several op amp stage are needed in single-ended supply circuits.

On the other hand, the LM359 is a very fast dual Norton amplifier in which each op amp has a unity-gain bandwidth of 30MHz with an open-loop gain of about 72dB, and in which most of the op amp parameters are externally programmable. This IC is particularly useful in video and high frequency amplifier/filter applications.

The LM3900 and LM359 operate in a very different way to conventional op

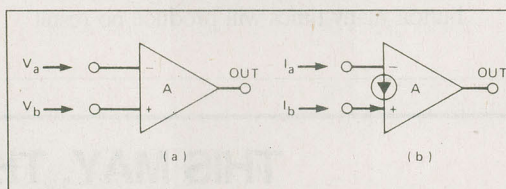


Fig. 1 (a) A conventional op amp. (b) A Norton op

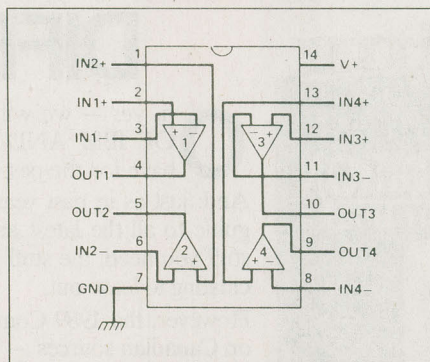


Fig. 2 Connections of the LM3900 quad Norton op amp.

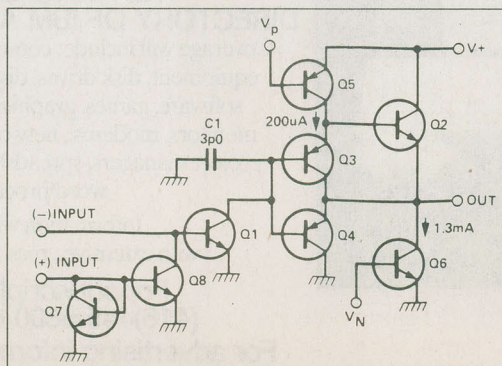


Fig. 3 Circuit of each of the four identical op amp stages of the LM3900.

amps and require the use of special biasing techniques. We will first take a look at the LM3900 and next move on to the faster LM359.

## Inside The Box

The LM3900 incorporates four identical current-differencing op amps, each having the circuit shown in Fig. 3. To aid understanding of the complete circuit, Fig. 4 shows six simple stages in the development of the final design.

Figure 4a shows a basic inverting amplifier circuit. Q1 is a common emitter amplifier with a high-impedance (constant-current) collector load, and gives a high-gain inverting action. Q2 is an emitter load. The high frequency response of the complete amplifiers is rolled off by C1, to enhance circuit stability.

Note that the output of this circuit can swing to within a few hundred mV of both zero and the positive supply rail voltage, and that its overall current gain equals the product of the two transistor current gains.

Figure 4b shows how the current gain of the above circuit can be increased with little loss of available output voltage swing, by adding PNP transistor Q3. The output of this circuit can typically source up to 10mA (via Q2) but can sink only 1.3mA (via Q2's constant-current generator).

Figure 4c increases the sink current by wiring Q4 so that in over-drive conditions it gives class-B operation.

Figure 4d shows transistors Q5 and Q6 used as constant-current generators



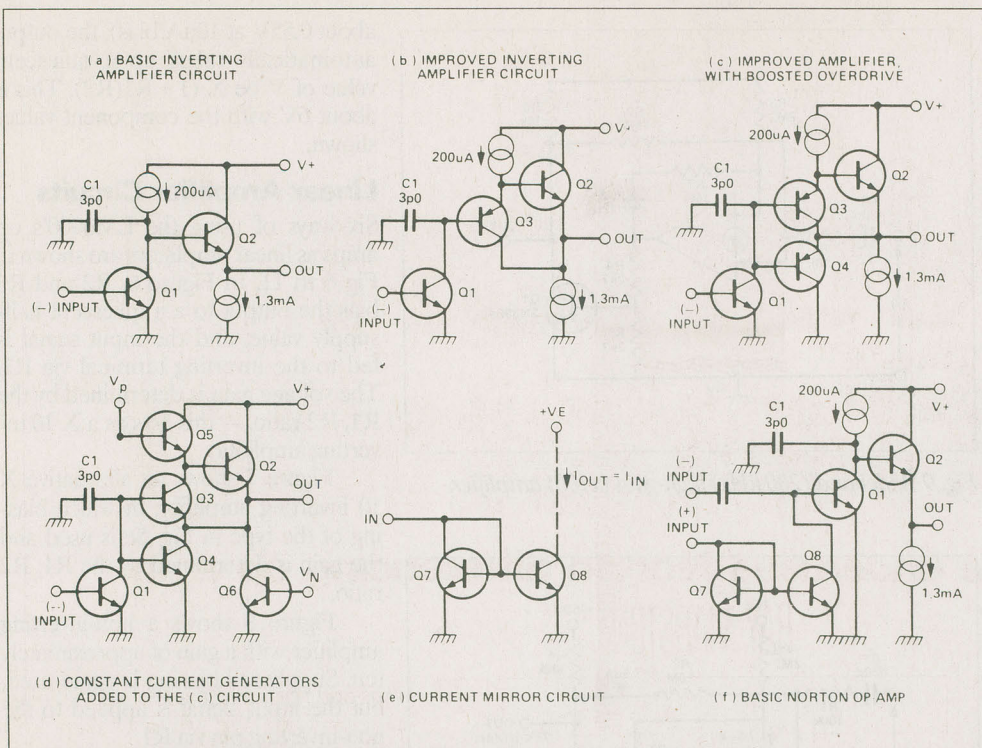


Fig. 4 Development of the LM3900 op amp circuit.

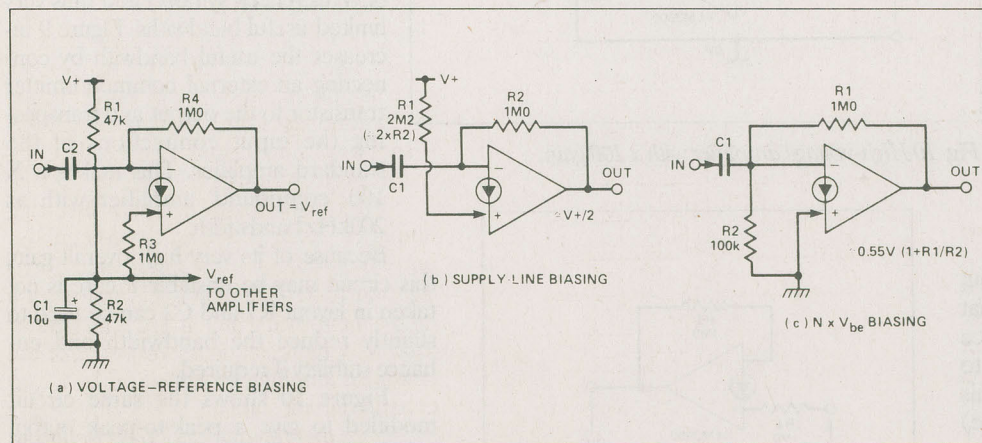


Fig. 5 Methods of biasing LM3900 op amps for linear operation.

(biased via a network that is built into the LM3900 IC).

### Current Mirrors

The Figure 4-d circuit forms the basis of each of the LM3900 amplifier stages, but gives an inverting action. The non-inverting LM3900 requires the assistance of the current mirror circuit of Figure 4e, which is made up of two matched and integrated transistors and simply draws an output current that is almost identical to the input drive current.

The input current is fed to the bases of both Q7 and Q8. Let's say both have current gains of  $\times 100$ , and both are drawing base currents of  $5\mu\text{A}$ . In this case both collector currents are  $500\mu\text{A}$  plus both base currents. The input and output currents of the circuit are thus almost identical (within a few percent), irrespective of the input current magnitude.

Figure 4f shows the current mirror circuit connected to the basic Fig. 4a circuit to give the current-differencing action of the Norton amplifier. The mirror circuit

is driven via the non-inverting input terminal, and the mirror current is drawn from the inverting input terminal, also connected directly to the base of Q1 amplifier stage. Consequently, the base current of Q1 equals  $I_- - I_+$ . This is the difference between the two input currents. The complete amplifier (back in Fig. 3) thus gives the current-differencing op amp action already mentioned.

Note that since both input terminals of the op amp are connected to transistor base-emitter junctions, both inputs act (in

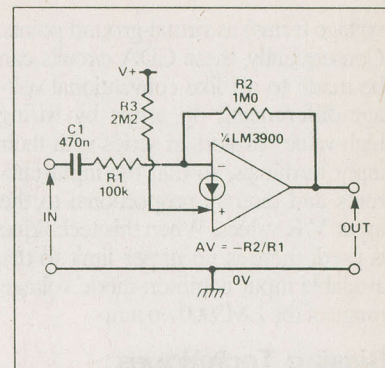


Fig. 6 Inverting AC amplifier with supply-line biasing.

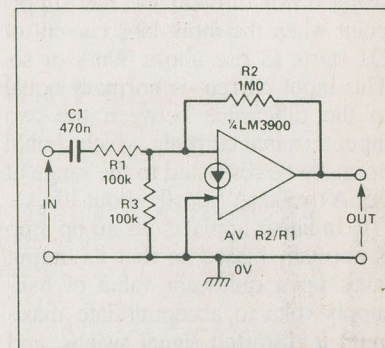


Fig. 7 Inverting AC amplifier with  $N \times V_{be}$  biasing.

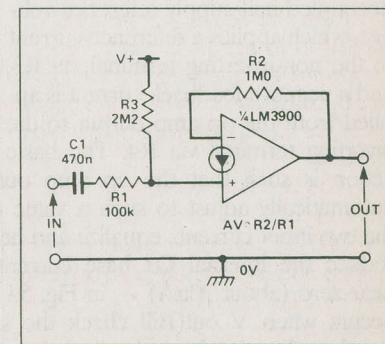


Fig. 8 Non-inverting amplifier.



# The Norton Difference

voltage terms) as virtual-ground points. Consequently, these CDA circuits can be made to act like conventional voltage-differencing op amps by wiring high-value resistors in series with their input terminals, so that the input currents and directly proportional to the input  $V/R$  values. When this technique is used, there is no upper limit to the available input common-mode voltage range of the LM3900 op amp.

## Biasing Techniques

The basic amplifier stages of the LM3900 have high current gains, and the output of the amplifier starts to swing down through the half-supply point when the input bias current of Q1 starts to rise above 30nA or so. This input current is normally equal to the difference between the two input terminal currents, which should normally be restricted to the range of 0.5uA to 500uA (ideally about 10uA).

In linear applications an op amp is normally biased so that its output takes up a quiescent value of half-supply volts to accommodate maximum undistorted signal swings, and Fig. 5a shows how the LM3900 can be biased to meet this condition.

R1, R2 and C1 generate a decoupled half-supply reference voltage, which applies a reference current to the non-inverting terminal via R3, and a negative feedback current is applied from the op amp output to the inverting terminal via R4. The basic action is such that the op amp output automatically adjust to such a value that the two input currents equalize and hence reduce the internal Q1 base current to near-zero (about 30uA) — in Fig. 5a this occurs when  $V_{out}$  (Bill check the size) equals to  $V_{ref}$ . (check the size). In practice, the single reference voltage source can be used to apply biasing for several op amp stages.

A variation of this biasing system is shown in Fig. 5b. The non-inverting terminal is biased from the positive supply rail via R1, which has a value approximately double that of R2, causing the output to bias at a quiescent value of half-supply volts. A minor defect of this biasing technique is that it allows supply line ripple to break through to the output, with gain of 0.5.

Note that in Figs 5a and 5b, the input signal is shown connected to the inverting terminal of the amplifier, but in practice the signal can be connected to either input.

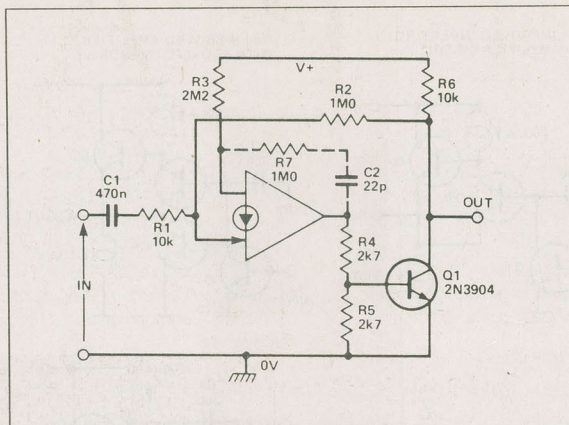


Fig. 9 Wideband (200 kHz) high-gain (x100) amplifier.

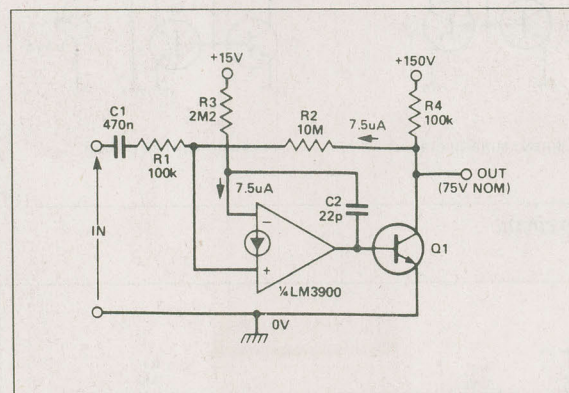


Fig. 10 High-voltage amplifier with x 100 gain.

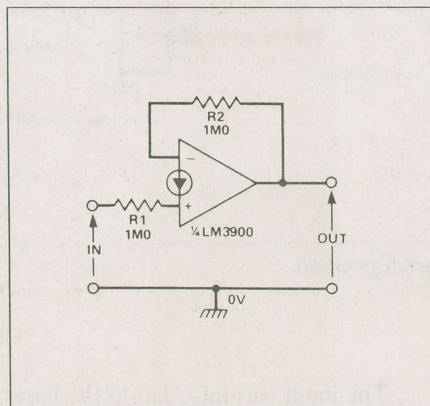


Fig. 11 DC voltage-following buffer.

Figure 5c shows an alternative biasing technique that can be used when the op amp is to operate only as an inverting amplifier. In this case the non-inverting terminal is disabled, and feedback potential divider R1, R2 is applied between the output and the inverting terminal. Consequently, since the inverting terminal acts as a transistor base-emitter junction ( $V_{be}$ ).

about 0.55V at 10uA bias), the output automatically takes up a quiescent value of  $V_{be} \times (1 + R1/R2)$ . This is about 6V with the component values shown.

## Linear Amplifier Circuits

Six ways of using the LM3900's op amps as linear amplifiers are shown in Fig 6 to 11. In Figure 6, R2 and R3 bias the output to a quiescent half-supply value, and the input signal is fed to the inverting terminal via R1. The voltage gain is determined by the R1, R2 ratio — this acts as a X 10 inverting amplifier.

Figure 7 shows an alternative X 10 inverting amplifier, in which biasing of the type in Fig. 5c is used and the gain is determined by the R1, R2 ratio.

Figure 8 shows a non-inverting amplifier with a gain of approximately ten. Supply-rail biasing is again used, but the input signal is applied to the non-inverting pin via R1.

The LM3900 op amps are fairly slow devices with slew rate of only 0.5V/us, (check symbol) and thus very limited useful bandwidths. Figure 9 increases the useful bandwidth by connecting an external common emitter transistor to the output and transposing the input connections of the standard amplifier. This makes a X 100 'compound' amplifier with as 200kHz bandwidth.

Because of its very high overall gain, this circuit may be unstable if care is not taken in layout R7 and C2 can be used to slightly reduce the bandwidth and enhance stability if required.

Figure 10 shows the same circuit modified to give a peak-to-peak output voltage swing of 150V (or whatever voltage is used to power Q1). Note that the output voltage of this circuit has a quiescent value of 75V, causing 7.5uA to be fed to the non-inverting terminal of the op amp via R2. To give correct biasing R3 (powered from the 15V supply rail of the op amp must also apply 7.5uA to the inverting pin of the op amp, as shown).

Finally, Figure 11 shows how to connect an LM3900 op amp as a unity-gain non-inverting amp-lifter or voltage following buffer. The input is connected to the non-inverting terminal via R1 (giving the non-inverting action) and R1 and R2 have equal values thus giving unity gain (note that the circuit would give a gain of X 2 if R1 were half the value of R2). ■



# CLIPART

## FOR PC/XT/AT AND MACINTOSH

NEW

Digital ClipArt is the spice of desktop publishing. However, unless you have a scanner and a ready source of hard copy clipart at your disposal, you'll have a hard time amassing a library of images. At least, it used to be.

Almost Free Ventura ClipArt picture collections are disks full of image files. They will work with Ventura 1.1, and we include a utility to make them suitable for use with the original 1.1 release or


the patched one. Each disk has a variety of pictures, both for spot illustrations and full pages. They're suitable for reproduction on any output device. Almost free clip art for the PC now includes a utility program to convert all of these pictures to PC Paintbrush PCX files, as well as one to convert them to the GEM/IMG files used by Ventura publisher. The Macintosh versions of these collections use the MacPaint file format. All this for only \$19.95 each.

### VOLUME 7

ANBORD2  
BIGBEN  
BORDER4  
CIVWAR  
DRUIDESS  
FISH  
GARDENWA  
GIRL12  
INSECTS  
LIONCUB  
MINTPLAN  
NATURE  
PIE  
RUINS  
WEAVING  
WMAP  
MISC1
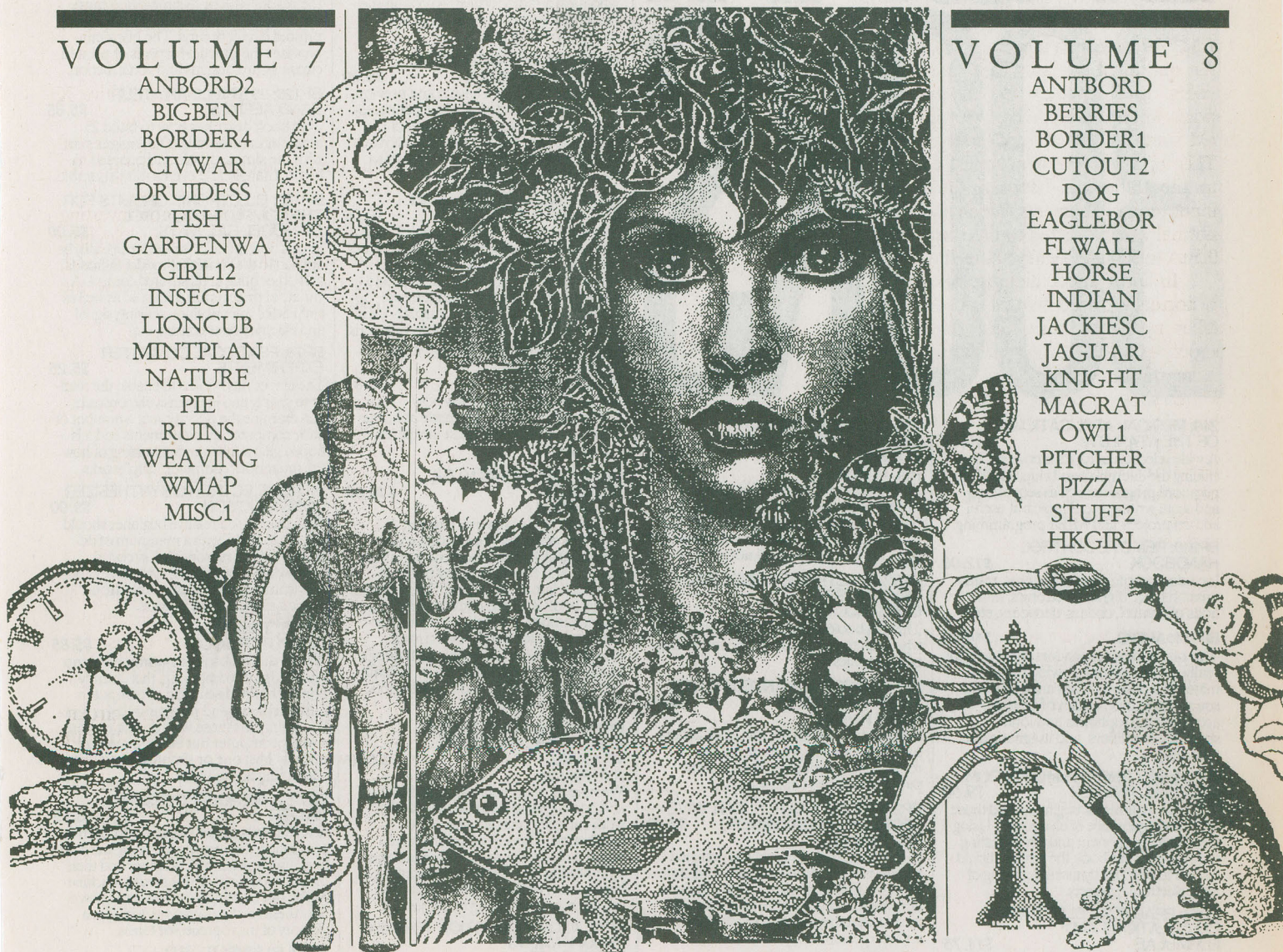
### VOLUME 8

ANTBORD  
BERRIES  
BORDER1  
CUTOUT2  
DOG  
EAGLEBOR  
FLWALL  
HORSE  
INDIAN  
JACKIESC  
JAGUAR  
KNIGHT  
MACRAT  
OWL1  
PITCHER  
PIZZA  
STUFF2  
HKGIRL



FINE PRINT: This software has been collected from public access bulletin boards and/or has been placed directly in the public domain by its authors. It is all believed to be in the public domain, or offered as "shareware". As shareware, users of these programs are requested to pay registration fees to their authors, which may entitle you to additional updates, support and documentation. Note that the fee charged for this disk defers our cost in collecting and distributing the software only, it does not replace any requested shareware contributions. This will help to ensure a continuing supply of high quality shareware available at reasonable prices. If you try out this disk, and do not feel that it is fair value, you may return it for a refund or exchange it for a different disk with no questions asked. We do not sell software to people who cannot use it. If you have trouble with disk, you are welcome to call our free technical support service at (416) 445-5600 during normal business hours. Please be prepared to tell us the exact make and model of your computer and the disk and program you are having difficulty with. Please note that we cannot be responsible for any loss, damage or expense resulting from your use of this software, however caused. If you are unable to read your disk, it has probably been corrupted in the mail. You need not call us in this case. Simply return the disk to our software department with a note requesting a replacement. It will be shipped immediately. Please note that this disk does presuppose a reasonable familiarity with your computer. If you are very new to your system, we strongly recommend that you familiarize yourself with it before attempting to use almost free software.

THIS DISK IS ONLY \$19.95 (PLUS 8% O.S.T. & \$1.50 SHIPPING) FROM MOORSHEAD PUBLICATIONS  
1300 DON MILLS ROAD, TORONTO, ONTARIO M3B 3M8 PHONE: (416)445-5600 FAX: 416-445-8149  
PLEASE SPECIFY 5 1/4 INCH DISKETTES OR 3 1/2 INCH MICROFLOPPIES



# BABANI BOOKS

## 246: MUSICAL APPLICATIONS OF THE ATARI STS \$15.00

A wide selection of topics is covered, including the internal sound chip, MIDI, applications programs such as sequencing and score writing, etc. Simple but useful add-on projects and MIDI programming.

## BP240: REMOTE CONTROL HANDBOOK \$12.00

Includes remote control systems, transmission links, digital electronics, methods of control, coders, decoders, etc.

## BP111: AUDIO \$14.00

This one is ideal for readers who want to really get into sound. A wide range of material is covered from analysis of the sound wave, mechanism of hearing, acoustics, microphones and loudspeakers, amplifiers, and magnetic disc recording.

## BP239: GETTING THE MOST FROM YOUR MULTIMETER \$9.00

This book is aimed at beginners and those of limited experience of electronics. Using the simple component and circuit testing techniques in this book the reader should be able to confidently tackle servicing of most electronic projects.

## BP53: PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE \$11.75

A book that bridges the gap between complicated technical theory and the "cut and try" method. A good reference book.

## BP174: MORE ADVANCED ELECTRONIC MUSIC PROJECTS \$12.00

Complementing Book PB74, "Electronic Music Projects", BP174 provides more advanced projects, such as a flanger, a phaser, mini-chorus and ring modulators, percussion synths, etc. Each project has an Introduction circuit diagram and constructional notes.

## BP113: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 2 \$9.00

R.A. Penfold  
A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

## BP92: ELECTRONICS SIMPLIFIED - CRYSTAL SET CONSTRUCTION \$5.25

This is a book written especially for those who wish to participate in the intricacies of electronics.

## BP192: MORE ADVANCED POWER SUPPLY PROJECTS \$8.00

Robert Penfold.  
A companion to BP76, this book covers switched mode supplies, precision regulators, tracking regulators, computer-controlled supplies, etc.

## BP222: SOLID STATE SHORT WAVE RECEIVER FOR BEGINNERS \$7.80

R.A. Penfold  
In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components.

## BP197: INTRODUCTION TO THE AMSTRAD PCs \$20.00

The Amstrad PC is an MS-DOS computer for general and business use. This book explains all you need to know to start computing.

## BP150: AN INTRO TO PROGRAMMING THE SINCLAIR QL \$7.80

Helps the reader make the best use of the Sinclair QL's almost unlimited range of features. Complements the manufacturer's handbook.

## BP48: ELECTRONIC PROJECTS FOR BEGINNERS \$7.80

F.G. Rayer, T. Eng. (CEI), Assoc.IERE  
Another book written by the very experienced author - Mr. F.G. Rayer - an in it the newcomer to electronics will find a wide range of easily made projects. Also, there are a considerable number of actual components and wiring layouts, to aid the beginner.

## BP135: SECRETS OF THE COMMODORE 64 \$5.85

This book is intended as a beginner's guide to the Commodore 64.

## BP155: INTERNATIONAL RADIO STATIONS GUIDE \$9.00

An invaluable aid in helping all those who have a radio receiver to obtain the maximum entertainment value and enjoyment from their sets.

## BP130: MICRO INTERFACING CIRCUITS - BOOK 1 \$9.00

Aimed at those who have some previous knowledge of electronics, but not necessarily an extensive one, the basis of the book is to help the individual understand the principles of interfacing circuits to microprocessor equipment.

## BP131: MICRO INTERFACING CIRCUITS - BOOK 2 \$9.00

Intended to carry on from Book 1, this book deals with practical applications beyond the parallel and serial interface. "Real world" interfacing such as sound and speech generators, temperature, optical sensors, and motor controls are discussed using practical circuit descriptions.

## BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$5.85

This book sets out to show how Electronic Music can be made at home with the simplest and most inexpensive equipment.

## BP74: ELECTRONIC MUSIC PROJECTS \$10.00

R.A. Penfold  
Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fux Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser Units, Tremelo Generator, etc.

## BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.80

R.A. Penfold  
We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

## BP86: AN INTRODUCTION TO BASIC PROGRAMMING TECHNIQUES \$5.85

This book is based on the author's own experience in learning BASIC and also in helping others, mostly beginners to programming, to understand the language.

## BP234: TRANSISTOR SELECTOR GUIDE \$15.00

Listings of British, European and eastern transistor characteristics make it easy to find replacements by part number or by specifications. Devices are also grouped by voltage, current, power, etc., includes surface-mount conversions.

## BP233: ELECTRONIC HOBBYIST HANDBOOK \$15.00

A single source of easily located information: colour codes, pinouts, basic circuits, symbols, etc.

## BP101: HOW TO IDENTIFY UNMARKED IC's \$1.95

An unusual and fascinating chart that is highly recommended to all those interested in electronics and which will hopefully pay for itself many times over, by enabling the reader to use IC's that might otherwise have been scrapped.

## BP121: HOW TO DESIGN AND MAKE YOUR OWN PCBs \$5.85

The purpose of this book is to familiarize the reader with both simple and more sophisticated methods of producing printed circuit boards. The book emphasizes the practical aspects of printed circuit board designs and construction.

## BP125: 25 SIMPLE AMATEUR BAND AERIALS \$5.85

This book describes how to build 25 amateur band aerials. The designs start with the simple dipole and proceed to beam, triangle and even a mini-rhombic.

## BP180: ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILWAYS \$9.00

Shows how home computers can easily be applied to the control of model railroads and other quite sophisticated control. A variety of projects are discussed as well as circuits for train position sensing, signal and electric points control, etc.

## BP78: PRACTICAL COMPUTER EXPERIMENTS \$5.25

The aim of this book is to enable the reader to simply and inexpensively construct and examine the operation of a number of basic computer circuit elements and it is hoped gain a fuller understanding of how the mysterious computer "chip" works.

## BP185: ELECTRONIC SYNTHESIZER CONSTRUCTION \$9.00

With this book a relative beginner should be able to build, with a minimum of difficulty and at a reasonably low cost, a worthwhile monophonic synthesizer and also learn a great deal about electronic music synthesis in the process.

## BP115: THE PRE-COMPUTER BOOK \$5.85

Aimed at the absolute beginner with no knowledge of computing, this entirely non-technical discussion of computer bits and pieces and programming is written mainly for those who do not possess a microcomputer but either intend to one day own one or simply wish to know something about them.

## BP72: A MICROPROCESSOR PRIMER \$5.25

In an attempt to give painless approach to computing, this inexpensive book will start by designing a simple computer and then the short-comings of this simple machine will be discussed and the reader is shown how these can be overcome. Includes a glossary of microprocessor terms.

## BP42: 50 SIMPLE LED CIRCUITS \$5.85

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components.

## BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE \$9.00

This book is designed to help the user find possible substitutes for a popular user-oriented selection of modern transistors and includes devices produced by over 100 manufacturers.



**BP140: DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS \$15.00**

Shows equivalents and pin connections of a popular user-oriented selection of Digital Integrated Circuits. Includes European, American and Japanese devices.

**BP100: AN INTRODUCTION TO VIDEO \$5.85**

This book is for the person who has just, or is about to buy or rent video equipment but isn't sure what it's all about.

**BP136: SIMPLE INDOOR AND WINDOW AERIALS \$10.00**  
**TEMPORARILY OUT OF PRINT****BP156: AN INTRODUCTION TO QL MACHINE CODE \$10.00**

The powerful sinclair QL microcomputer has some outstanding capabilities in terms of its internal structure. With a 32-bit architecture, the QL has a large address range, advanced instructions which include multiplication and division. These features give the budding machine code programmer a good start at advanced programming methods. This book assumes no previous knowledge of either the 6808 or machine code programming.

**BP93: ELECTRONIC TIMER PROJECTS \$7.80**

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually.

**BP141: LINEAR IC EQUIVALENTS AND PIN CONNECTIONS \$23.80**

Find equivalents and cross-references for both popular and unusual integrated circuits. Shows details of functions, manufacturer, country of origin, pinouts, etc... includes National, Motorola, Fairchild, Harris, Intersil, Philips, ADC, AMD, SGS, Teledyne, and many other European, American and Japanese brands.

**BP7: RADIO AND ELECTRONICS COLOUR CODE AND DATA CHART \$3.00**

Opens out to Wall Chart approximately 584 X 457mm. Includes many Radio & Electronics Colour Codes in use in UK, USA, Europe and Japan. Covers Resistors, Capacitors, Transformers, Field Coils, Fuses, Battery Leads, etc.

**BP144: FURTHER PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE \$15.00**

This book covers many aspects of electronics where a knowledge and familiarity of the appropriate formulae is essential for a fuller understanding of the subject. An essential addition to the library of all those interested in electronics be they amateur, professional or student.

**BP225: A PRACTICAL INTRODUCTION TO DIGITAL ICs \$7.00**

This book deals mainly with TTL type chips such as the 7400 series. Simple projects and a complete practical construction of a Logic Test Circuit Set are included as well as details for a more complicated Digital Counter Timer project.

**BP47: MOBILE DISCOTHEQUE HANDBOOK \$7.80**

Divided into six parts, this book covers such areas of mobile "disco" as: Basic Electricity, Audio, Ancillary Equipment, Cables and Plugs, Loudspeakers, and Lighting. All the information has been subdivided for quick and easy reference.

**BP147: AN INTRODUCTION TO 6502 MACHINE CODE \$10.00**

The popular 6502 microprocessor is used in many home computers; this is a guide to beginning assembly language.

**BP59: SECOND BOOK OF CMOS IC PROJECTS \$7.80**

This book carries on from its predecessor and provides a further selection of useful circuits, mainly of a simple nature. The book is well within the capabilities of the beginner and more advanced constructor.

**BP88: HOW TO USE OP-AMPS \$11.80**

E.A. Parr  
A designer's guide covering several op-amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made a non-mathematical as possible.

**ELEMENTS OF ELECTRONICS - AN ON-GOING SERIES \$11.80 EACH****OR ALL 5 BOOKS FOR \$44.00**

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

**BP62: BOOK 1.** This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

**BP63: BOOK 2.** This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

**BP64: BOOK 3.** Follows on semiconductor technology, leading up to transistors and integrated circuits.

**BP77: BOOK 4.** A complete description of the internal workings of microprocessor.

**BP89: BOOK 5.** A book covering the whole communication scene.

**BP194: MODERN OPTO DEVICE PROJECTS \$8.00**

This book provides a practical design guide to modern optoelectronics, including such things as fibre optics, ultra-bright LEDs and passive IR detectors.

**BP37: 50 PROJECTS USING RELAYS, SCR's & TRIACS \$7.80**

F.G. Rayer, T. Eng., (CEI), Assoc. IERE.  
Relays, bi-directional triodes (TRIACS), and silicon controlled rectifiers (SCRs), have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification and ready adaptation of them to individual needs.

**BP95: MODEL RAILWAY PROJECTS \$7.80**

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered included controllers, signals and sound effects: stripboard layouts are provided for each project.

**BP84: DIGITAL IC PROJECTS \$7.80**

F.G. Rayer, T. Eng. (CEI), Assoc. IERE.  
This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome.

**BP44: IC 555 PROJECTS \$10.00**

E.A. Parr, B.Sc., C. Eng., M.I.EE.  
Every so often a device appears that is so useful that one wonders how life went on before it. The 555 timer is such a device included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

**BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.80**

R.A. Penfold  
Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, and more.

**BP49: POPULAR ELECTRONIC PROJECTS \$10.00**

R.A. Penfold  
Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types, Radio Projects, Audio Projects, Household Projects and Test Equipment.

**BP99: MINI-MATRIX BOARD PROJECTS \$7.60**

R.A. Penfold  
Twenty useful projects which can all be built on a 24 X 10 hole matrix board with copper strips. Includes Door-buzzer, Low-voltage Alarm, AM Radio, signal Generator, Projector Timer, Guitar Head-phone Amp. and more.

**BP103: MULTICIRCUIT BOARD PROJECTS \$7.80**

R.A. Penfold  
This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects.

**BP98: POPULAR ELECTRONIC PROJECTS \$7.80**

R.A. Penfold  
This book contains 21 projects with some experience.

**BP195: AN INTRODUCTION TO SATELLITE TELEVISION \$15.00**

For the absolute beginner or anyone thinking about purchasing a satellite TV system, the story is told as simply as such a complex one can be.

**BP106: MODERN OP-AMP PROJECTS \$7.80**

R.A. Penfold  
features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types.

**BP107: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1 \$9.00**

R.A. Penfold  
A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown.

**BP127: HOW TO DESIGN ELECTRONIC PROJECTS \$9.00**

Although information on stand circuits blocks is available, there is less information on combining these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs.

**BP122: AUDIO AMPLIFIER CONSTRUCTION \$6.75**

A wide circuits is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or stripboard layout are included. Most of the circuits are well within the capabilities of even those with limited experience.

**BP179: ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS \$12.00**

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge the gap.

**BP108: INTERNATIONAL DIODE EQUIVALENTS GUIDE \$7.00**

Cross-references European, American and Japanese diode part numbers. Besides rectifier diodes, it includes Zeners, LEDs, Diacs, Triacs, SCRs, OCIs, photodiodes, and display diodes.

**BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - BOOK 2 \$7.60**

R.A. Penfold  
This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered.

**BABANI BOOKS  
EXCLUSIVELY AVAILABLE  
IN CANADA FROM  
MOORSHEAD  
PUBLICATIONS.  
ORDER YOUR  
SELECTIONS  
BY TELEPHONE:  
(416) 445-5600 OR  
FAX: 416-445-8149  
OR WRITE TO US AT  
1300 DON MILLS ROAD,  
NORTH YORK, ONTARIO  
M3B 3M8**



# TECH TIPS

Circuits for the experienced constructor


## 8-Way Stereo Selector

This circuit provides noiseless remote selection and routing of eight audio signals, either stereo or balanced pair mono, using simple non-locking push-switches.

The BCD counter IC2 is disabled from counting IC1's 1MHz clock rate by the wired high on pin 1. A momentary closure of SW2, say, is sufficient and the switching action is effectively debounced. The code 0010 is now present on all the ICs so that LED 2 on IC4 is now lit and inputs A2 and B2 are connected to the outputs of IC5 and IC6.

SW8 selects BCD 1000 inhibiting the 4051s and providing an 'off' facility. ICs 5 and 6 may, of course, be remote from the selection and indicating circuitry — advantageously sited with respect to the audio signal paths.

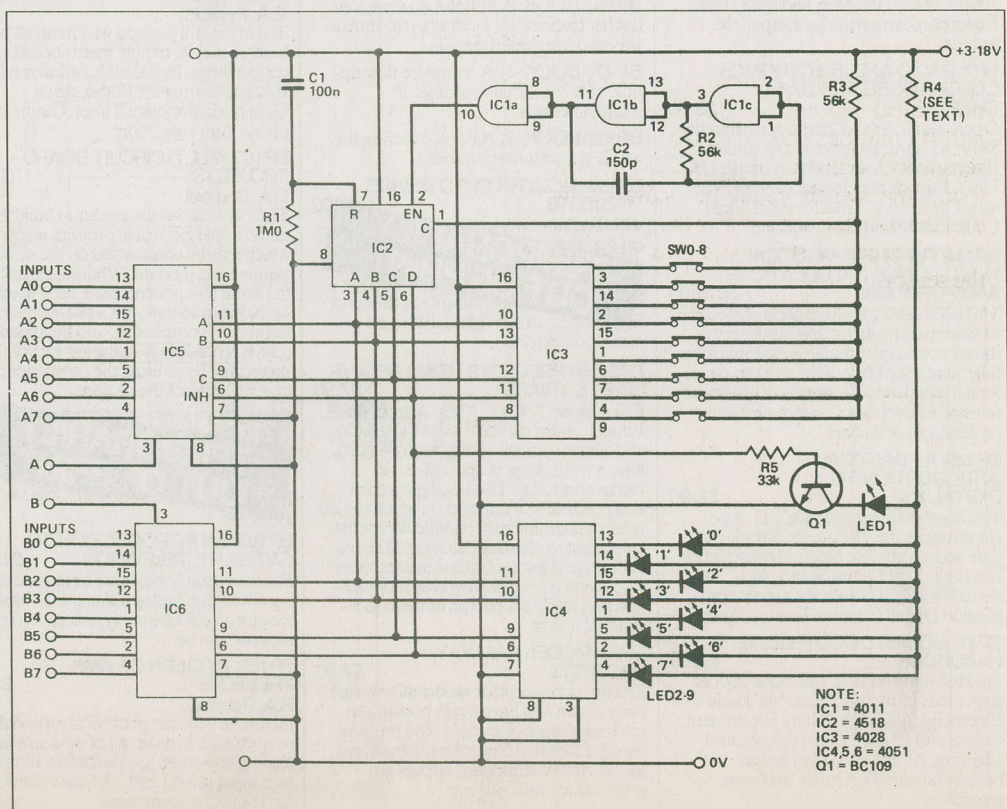The power requirement is only about 1/2mA above the required by the LEDs. Select R3 to suit the supply voltage assuming 25mA for the LED (so 140R for 6V, 260R or 9V, 380R for 12V, 500R for 15V and so on).





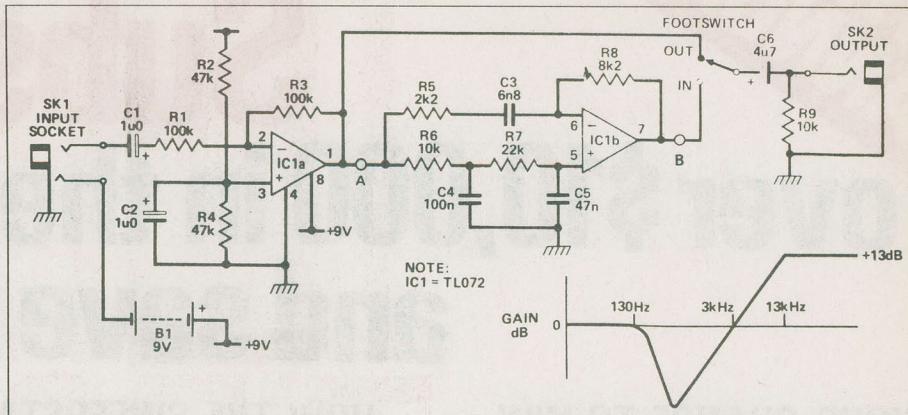
# Guitar Preshaper

Some upmarket bass and guitar amps are fitted with a preset tone circuit to give an instant clean modern sound without the tedious EQ setting. In this circuit IC1b filters high and low frequencies, then recombines them to produce a frequency response approximately as shown. This produces a clean bright sound for either 6-string guitar or bass.

The circuit can be built as a footpedal powered from a 9V battery (no power LED is included to extend battery life).





# Cheap Touch Switch

This circuit, originally designed as the switch of an alarm system for a disabled person, takes advantage of the high input impedance of the 2N7000 'FETlington.' The high value resistor R1 pulls the gate of Q1 to the positive rail. If the operator's finger is placed across the sensor contacts, the gate voltage falls close to zero. This switches Q1 off.

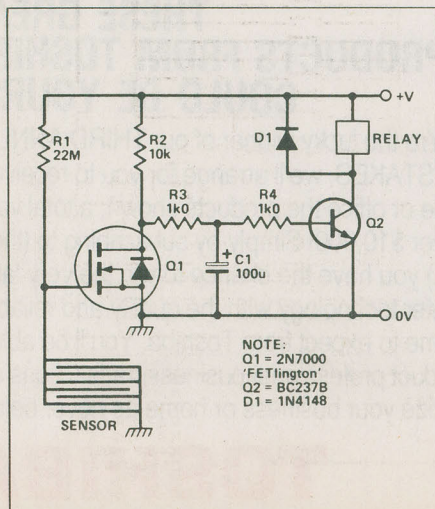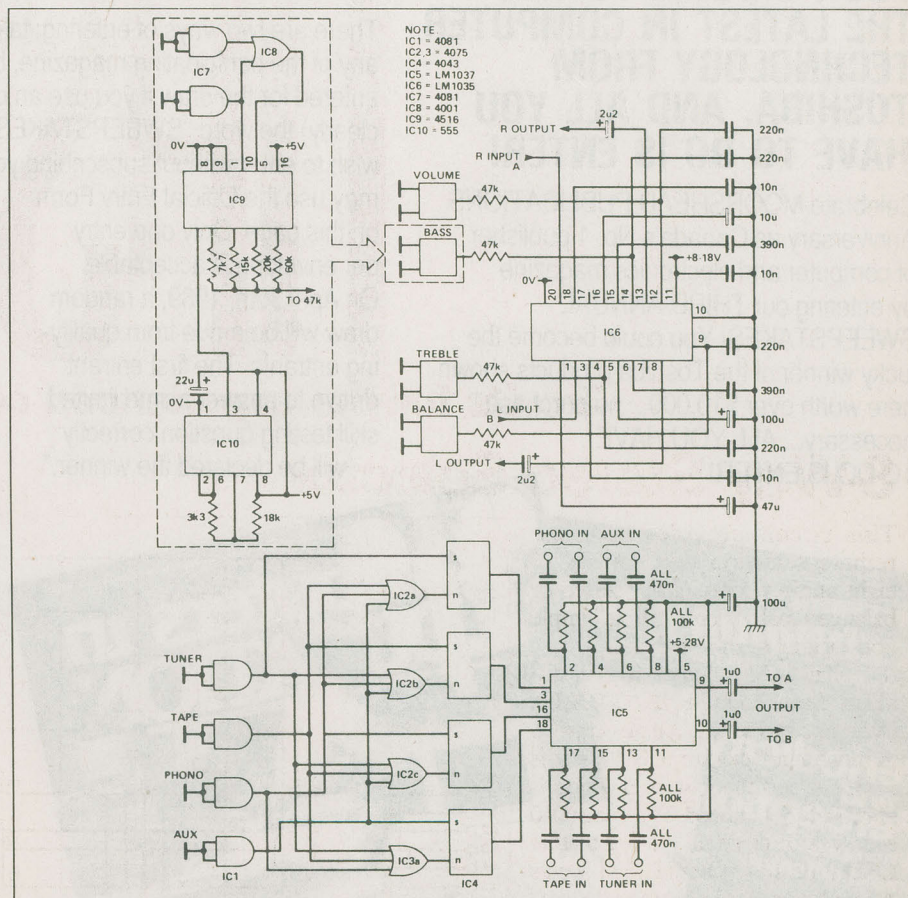Q2 acts to invert the signal from Q1 and so the relay is normally de-energised. R3 and R4 provide the correct voltage at the base of Q2. C1 adds some delay to overcome any 'contact' bounce from the sensor.

The type of transistor used for Q2 is not critical and nor is the supply rail voltage. R1 may be reduced to 10M to reduce sensitivity. With a value of 22M it was found the switch could be activated by breathing on the sensor! For the prototype a small piece of stripboard was used for the sensor.



## Touch Controlled Pre-amp

A touch controlled pre-amp with touch plate selection of inputs and volume, bass, treble and balance can be easily constructed with the help of the LM1037 and 1035 audio control ICs. The touch plate sensors rely on the tied inputs of the AND gates (IC1, 11, 21, 31, 41) floating low and being taken high by a touch on the plate.

IC2, 3 form a latching arrangement so that each touch on an input selector plate will set the relevant flip-flops and reset the others.

The four flip-flop outputs are used to switch on a pair of inputs to IC5 through to IC6. This uses the DC voltage from the four identical volume bass, treble and balance circuits to filter and attenuate the stereo channels.

The DC control voltage is obtained by weighting the 4-bit output from up/down counter IC13 (23, 33 and 43). The counter is clocked by the 555 timer in astable mode and enabled to count up or down by IC11 and IC12.



**THIRD  
ANNUAL**

# MOORSHEAD PUBLICATIONS **Subscribe Now**

## over \$10,000 in the latest computer products and save up to 58% off

### **YOUR CHANCE TO WIN THE LATEST IN COMPUTER TECHNOLOGY FROM TOSHIBA. AND ALL YOU HAVE TO DO IS ENTER!**

Celebrate MOORSHEAD PUBLICATIONS Anniversary as Canada's No. 1 publisher of computer and electronics magazine by entering our THIRD ANNUAL SWEEPSTAKES! You could become the lucky winner of the Toshiba products shown here worth over \$10,000... no purchase necessary... **ALL YOU HAVE TO DO IS ENTER!**

### **HOW THE SWEEPSTAKES WORK**

There are two ways of entering: take out a new subscription, or renew one, to any of the participating magazine, before April 15th, 1989 and your name will be entered for the draw if you use an official entry form OR if you write (boldly and clearly) the word "SWEEPSTAKES" on other cards or forms. If you wish to enter without subscribing you may use the Official Entry Form on this page. Only one entry per envelope is acceptable. On April 30th, 1989, a random draw will be made from qualifying entrants. The first entrant drawn to answer a time limited skill testing question correctly will be declared the winner.\*



### **THESE GREAT PRODUCTS FROM TOSHIBA COULD BE YOURS!**

If you're the lucky winner of our THIRD ANNUAL SWEEPSTAKES, we'll arrange for you to receive at your home or office the products shown; a total value of over \$10,000! Simply by subscribing to (these publications) you have the chance to win the very latest in computer technology with the quality and reliability you've come to expect from Toshiba. You'll be able to conduct professional business transactions and computerize your business or home as never before!

**TOSHIBA**  
**WE MEAN BUSINESS**  
INFORMATION SYSTEMS DIVISION






# **IONS SWEEPSTAKES** **ow and Win!** **puter technology from Toshiba** **on your subscription!**
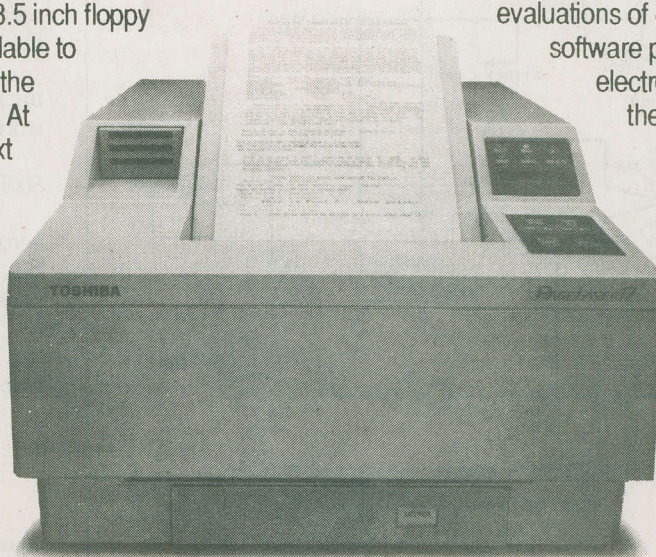
## **GAS PLASMA LEGEND FROM TOSHIBA**

The new T3100e offers true AT performance in a package small enough to take anywhere. Based on the extremely successful and award winning T3100/20 portable PC, this outstanding updated machine takes advantage of the latest advances in portable computer technology and packs more speed, memory and power than ever before into an even smaller and lighter package. The T3100e features an 80286 microprocessor running at 12MHz, a fast 20Mb internal hard disk drive plus a 1.44Mb 3.5 inch floppy disk drive, and 1Mb of RAM standard expandable to 5Mb. Boasting a brilliant gas plasma display, the new T3100e provides outstanding resolution. At 640 x 400 pixels, it's perfectly suited for all text and graphics applications. With all standard ports including parallel, two serial, RGB, and external 5.25 inch floppy, this amazing machine also has an 8-bit expansion slot for all industry standard and Toshiba proprietary communications cards or for an expansion chassis. The Toshiba T3100e, at less than thirteen pounds, is the portable computer that truly combines the convenience of a portable with superior desktop AT performance.



## **MAKE THE MOST OUT OF YOUR TOSHIBA SYSTEM WITH THE MAGAZINES OF THE MOORSHEAD GROUP... COMPUTING NOW!, ELECTRONICS & TECHNOLOGY TODAY, COMPUTERS IN EDUCATION.**

Enter your subscription(s) and receive in-depth evaluations of computers, peripherals, and software plus the latest happenings in electronics & technology. Expand the use of your microcomputer with probing articles on programming break-throughs and important news that will increase your "computer consciousness"! You will find applications and innovations you can use directly on any computer and keep abreast of the newest developments in microcomputing! Closing dates for entries April, 15th 1989.

## **THE NEW PAGELASER 12**

Laser printer quality with a whole lot more. Outstanding full-page print quality and graphics, with its resolution of 300 dots/inch. And at 12 pages/minute it's incredibly fast. Long product life at 600,000. It holds up to 750 sheets, more paper than anyone else. Up to 2MB of memory and a 16-digit English-Language panel display. A high duty cycle of 10,000 pages/month. It comes standard with many features including Serial and Parallel RS232 Interfaces.

\*IBM PC-AT is a registered trademark of International Business Machines Corporation.

\*Employees and their families of Moorshead Publication and Toshiba Canada are not eligible to enter.

**THIRD  
ANNUAL**

## **OFFICIAL ENTRY FORM MOORSHEAD PUBLICATIONS SWEEPSTAKES**

- ☐ Yes, enter my name in the **SWEEPSTAKES** for \$10,000 in **TOSHIBA** products  
☐ Start my subscription to ☐ Computing Now! ☐ Electronics & Technology Today ☐ Computers in Education for the term checked below as a saving of up to 58% on the newsstand rates.  
☐ One Year for \$19.97 ☐ Two Years for \$36.97  
☐ NO, I don't wish to subscribe now, but tell me if I've won.

Name \_\_\_\_\_ Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Province \_\_\_\_\_ Postal Code \_\_\_\_\_

Check one: ☐ Payment enclosed ☐ Charge my: ☐ American Express ☐ Visa ☐ MasterCard.

Card No. \_\_\_\_\_ Expiry Date \_\_\_\_\_

Special subscription rates are for SWEEPSTAKES only,  
(Savings are up to 21% off regular subscription rates)

### **MOORSHEAD PUBLICATIONS**

1300 Don Mills Road, North York (Toronto) Ontario M3B 3M8 Tel: (416) 445-5600 Fax: 416-445-8149





## Low Current Siren

This efficient circuit provides an output of 10V RMS (approx 103dB at 1m) at a current consumption of only 30mA.

Low frequency oscillator IC1a varies the frequency of audio oscillator IC1b by switching in and out C2. The rapidly varying audio signal is gated by IC1c to output amplifier stage Q2, 3 and an inverted signal is passed to Q4, 5.

The piezo transducer is connected between the stages with 20V peak-to-peak across it.

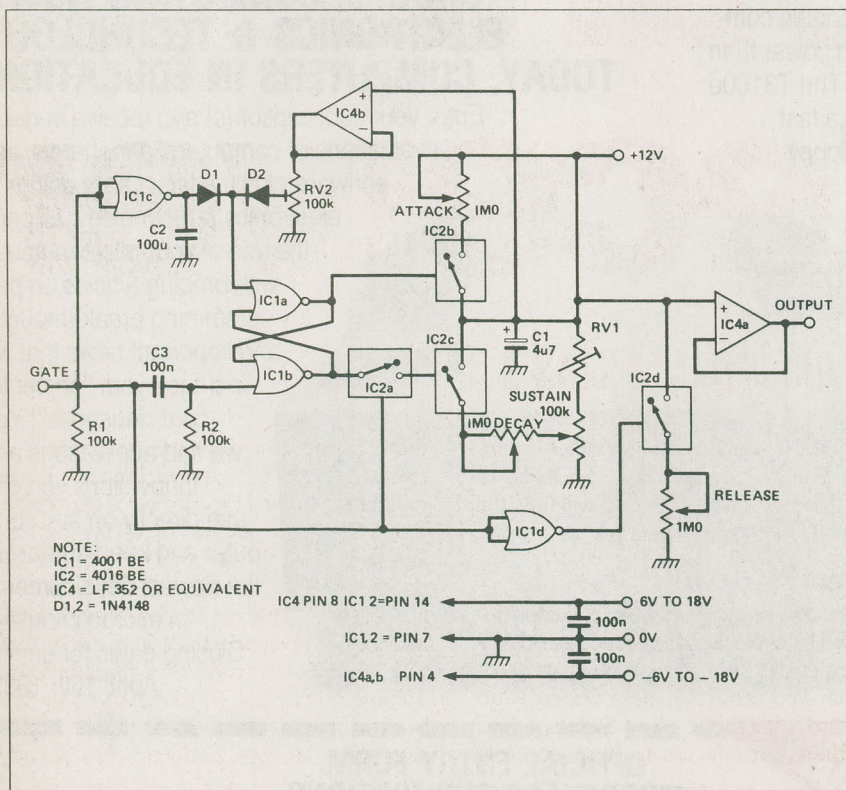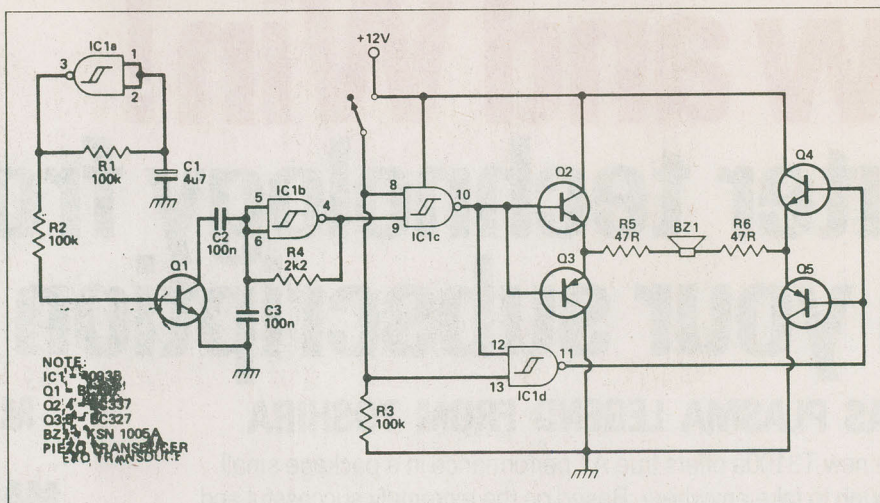Resistors R5 and R6 serve to limit the current and stabilize the output stages.



## Envelope Generator

This envelope generator was designed to boost the performance of my ancient monophonic synthesizer which came equipped with only one. This way I can control either the VCA or VCF with each generator. It's a no-frills ADSR generator and it's small and cheap.

C1 charges at a rate set by the attack pot when the gate goes high (at the start of a note). At a certain voltage (set by RV2), the flip-flop of IC1a, b

resets and C1 discharges at a rate set by the decay pot until it reaches the voltage set by the sustain pot. When the gate is removed (note off) C1 discharges through the release pot.

RV1 sets the maximum sustain level which should be set to match the voltage controlled device. IC4 buffers the voltage across C1 for the output.

I used this circuit with a Moog Rogue with excellent results.

## Super Woofer


This circuit enables a single centrally placed woofer to be added to a stereo system. This gives a cost effective bass enhancer which still preserves the stereo picture via the original speakers.

The right channel is driven in antiphase and the right hand speaker is reverse connected to restore the phase.

C1 and C2 as shown give a crossover at about 800Hz — other values could be tried.

The single bass speaker is bridge connected across the antiphase outputs via inductor L1. This has the incidental advantage of cancelling out in-phase hum and vertical turntable rumble.

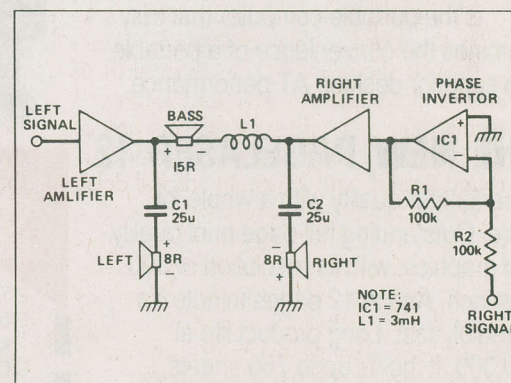Note that for a system playing records only, the inverting IC circuit could be removed by reversing one half of the stereo cartridge.



*The circuits shown are from readers, and while we make every effort to reproduce them accurately, E&TT cannot be responsible for circuit operation.*



# Pioneer's Surround Sound AV Receiver

TIMOTHY B. PALMER-BENSON

The VSX-9300S is one of the most interesting and sophisticated A/V products I've ever come across and in view of what it can do, its \$1,200 suggested list price gives you quite a bargain. In a sense, Pioneer is tackling the last frontier in home audio with the VSX-9300S: the rebirth of surround sound in a new and improved format. This unit gives you the very best of this new technology: Dolby Pro-Logic Surround Sound, with adjustable digital delay as well as Simulated and Stadium Sound, a real 125 watts RMS power per channel with low distortion and 30 watts per channel on the rear. With this and a host of other features, the unit has all that most people will ever need when it comes to bringing the theatre into their homes.

There are facilities for connecting and processing video signals from two VCRs, two-way dubbing, a video disc player input, a split-screen video enhancer (for comparing enhancement with the original) and a VCR audio noise filter (see fig.1). The unit can remember five acoustic control environments and comes with a Smart Remote (an infrared control box that can

be taught the control codes of other equipment). For those who like to be lulled to sleep, there's even a timer that will turn the power off after 60 or 30 minutes.

## Controls

A newcomer to the VSX-9300 is faced with a myriad of controls. Microprocessors offer an inexpensive way of operating a lot of functions and some Japanese designers go overboard with them. Nevertheless, I find that when sensibly used, these controls

make consumer equipment much easier to operate and in the case of Pioneer, I take my hat off to the ergonomics of the design. The VSX-9300's station ID display is an example of this. As you preset one of up to 20 stations, you can also assign it a four character ID and store it in the unit's non-volatile memory. This concept is taken still further with what Pioneer calls a "Hyper Intelligent Tuning System" — HITS for short — that lets you scan all the named stations beginning with the four character IDs already

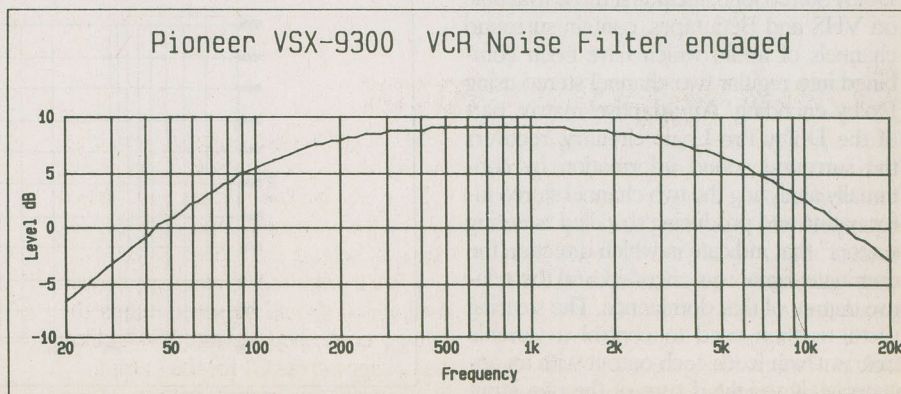


Fig. 1. The Pioneer VSX-9300 with the VCR noise filter engaged.



# Pioneer's Surround Sound AV receiver

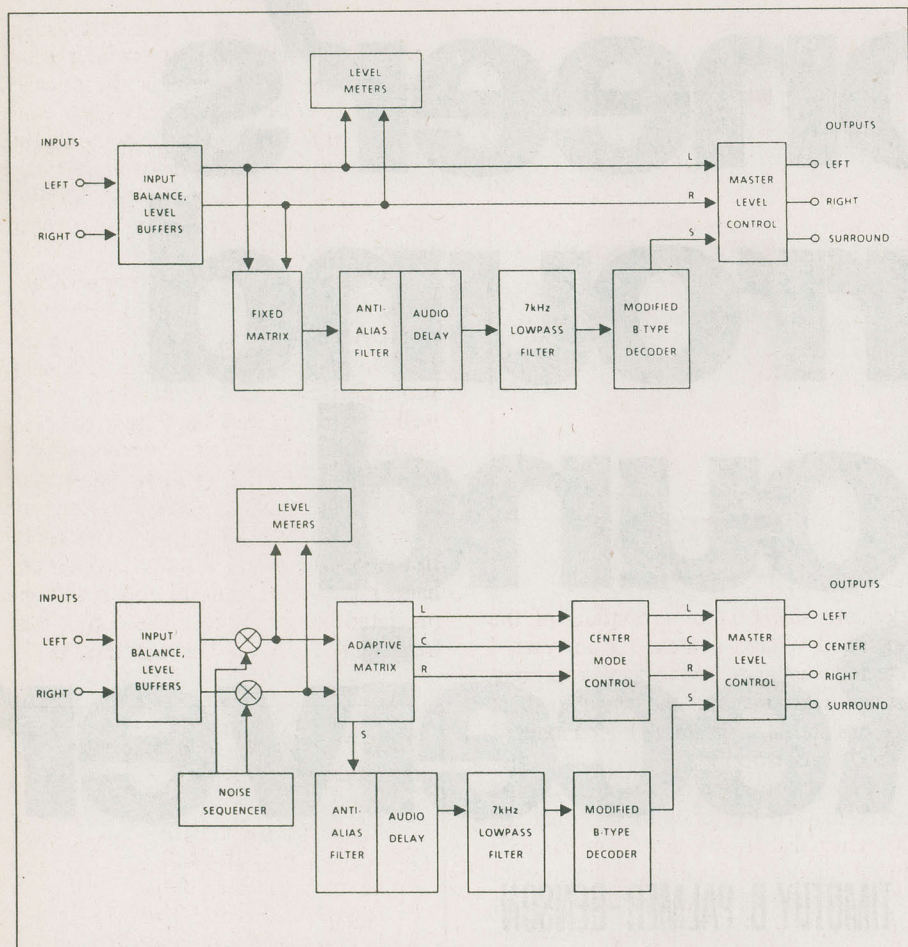


Fig. 2. The Dolby surround decoder block diagram (top) and the Dolby Pro Logic surround decoder block diagram (bottom).

entered.

## Decoding

Unquestionably, the VSX-9300's biggest drawing card is the Dolby Pro-Logic Surround Sound circuitry licensed from Dolby Labs. Dolby Pro-Logic decodes motion picture soundtracks in a manner similar to that used in movie theatres equipped with Dolby Stereo. All movies that bear the Dolby Stereo logo, including those available on VHS and Beta tapes, contain surround channels of audio which have been combined into regular two channel stereo using Dolby encoding. An adaptive matrix, part of the Dolby Pro-Logic circuitry, recovers the surround sound information by continually analyzing the two channel stereo information and producing so called "steering vectors" that indicate in which direction the dominate signal was encoded and the relative degree of that dominance. The steering vector is then used to control a variable matrix which feeds each output with an appropriately weighted sum of the two input signals. The procedure results in proper

location of sounds in a 360 degree listening environment. An additional benefit is a "steered" centre channel which puts dialogue on the screen. Pro-Logic is said to be especially effective in ensuring that listeners both on and off "axis" benefit from the surround sound effect. Separation is nominally 25dB between left centre and

right centre, and 25dB between left, right front and surround. This is a substantial improvement over the passive Dolby surround decoder which gives only 3dB of separation.

All Dolby Surround decoding systems include Dolby B type noise reduction, a time delay for the rear or side speakers and 7kHz bandwidth limiting. The normal delay is 20 milliseconds but with the Pioneer, 15 and 30 millisecond delay is also available (the delay is accomplished via digital circuitry). Delay is used because it helps the ear establish directionality. Bandwidth limiting is used to mask the effect of any phase errors in the encoding and decoding process since high frequency errors are more noticeable.

Note that the block diagram of the Dolby Pro Logic Surround decoder (fig.2) as it appears in the VSX-9300S does not show that the receiver has additional circuitry for Stadium and Simulated surround sound. The "Noise Sequencer" shown in this diagram is used to adjust volume on each channel (this can be done from the listening/viewing position with the remote control). The sequencer generates band-limited noise that is gated alternately to left, centre, right front and surround channels. The noise appears for two seconds in each channel as soon as Pro Logic is engaged and one has selected "Test".

## Outputs

Dolby has also included in its licensing agreement with manufacturers a bass splitting function for home use. Dolby surround sound systems in movie theatres use a full frequency range centre channel to help locate dialogue on the screen as well as left and right speakers. In private homes this is not considered so important because the left and right speakers are likely to be closer together, so Dolby includes three additional settings. The normal set-

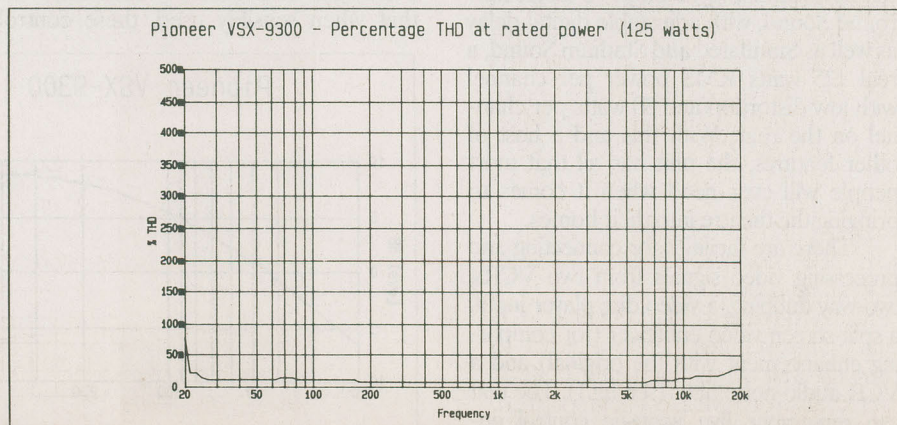


Fig. 3. Percentage of Total Harmonic Distortion at rated power (125W).



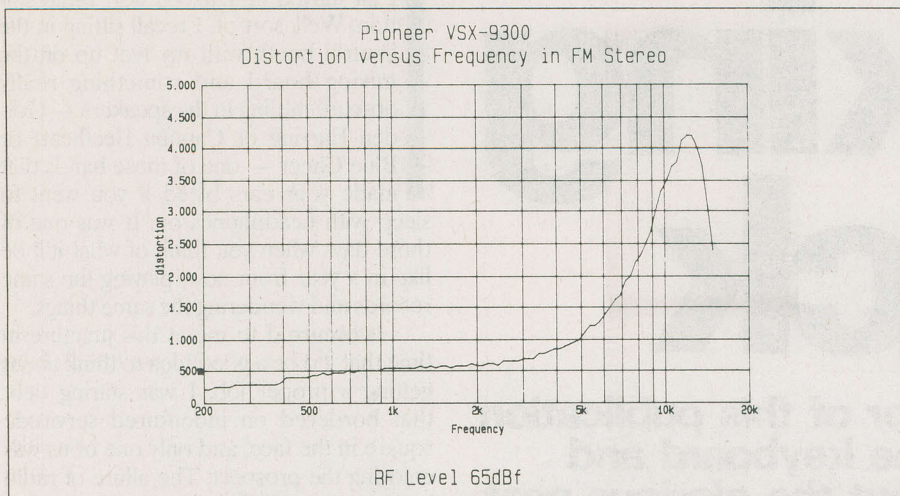


Fig. 4. Distortion versus frequency in FM stereo.

ting separates bass information below 100 Hz and distributes it equally to the left and right channels. What's left, which is anything above 100Hz, is available for a small centre channel amplifier and speaker, such as the ones in a TV set. The wide setting provides full frequency range output to the centre channel. The third setting, or what is referred to as "Phantom", distributes the entire centre channel signal to the front left and right channel speakers.

The VSX-9300S uses a single power supply for both the front and surround channels. There is no centre channel amplification, just a line output that is approximately 4dB higher than the left and right front line outputs.

### Specs

I found my unit capable of generating 135 watts of continuous power into two 8 ohm loads in both front channels with no more than 0.03% THD. This signal level was achieved with the volume control wide open and only 158-millivolts applied to the CD input. The receiver is rated at 125 watts per channel with no more than 0.005% THD into 8 ohms; however, I was unable to confirm this extremely low distortion figure (see fig.3). I was pleased to note that the VSX-9300S maintained its rated power output with low distortion even with an AC line voltage of 110 volts. Dynamic headroom as per the IHF standard measured 1.67dB, a little less than claimed.

Signal-to-noise via the CD and VCR inputs, compared to a 500-mv input to achieve a 1-watt output, measured 77dB, A weighted, also somewhat less than specified. I fear my measurement result was caused either by power grounding or by the lack of

adequate shielding or grounding of the motorized volume control. At any rate, I detected what appeared to be microprocessor noise leaking into the signal path at medium and high volume levels. Pioneer's own S/N spec is 98dB.

FM performance is acceptable. Some people may be fooled by the fact that the FM tuner section will burst into life with several stations in urban areas without an antenna connected. Unfortunately, this is an indication of poor shielding which could affect the tuner's specified 80dB IF interference ratio and which did affect my measurements. Usable sensitivity measured 22dBf in mono (IHF), stereo separation was 36dB at 1kHz, and the S/N for a mono signal was 42dB. THD measured 0.5% in stereo at 1kHz and was substantially higher at 6kHz as can be seen in fig.4. Noise in the phono section was down 65dB. Phono equalization (fig.5) was reasonably accurate with 0.5dB error in the mid bass.

Although some of these measurements don't indicate spectacular performance, one must remember the price of this unit and that it is primarily intended to create a movie theatre in the home. In this area it excels, with impressive separation figures in the Pro-Logic mode. Table 1 shows what this Pro-Logic surround sound receiver can do.

While these figures are impressive, it is the sound field that this unit is capable of producing that impressed me the most. I've heard this unit used with a 50-inch projection TV and a laser disc player as well as with smaller TVs. Believe me, with the right soundtrack, the sound bowls you over. The VSX-9300S has enough power to make the visual and audio experience of a movie like *Top Gun* truly memorable. In the video realm, I found the video enhancer particularly useful and really appreciated the ability to make copy either from VCR 1 to VCR 2 or viceversa. ■

Table 1. Separation measurements; test signal 1kHz, 400mv.

Fr. Left to Fr. Right	51dB
Fr. Right to Fr. Left	54dB
Fr. Left to Fr. Centre	29dB
Fr. Right to Fr. Centre	31dB
Fr. Left to Left Surround	43dB
Fr. Right to Left Surround	44dB
Fr. Centre to Fr. Left	22dB
Surround to Fr. Left	20dB
Fr. Centre to Fr. Right	37dB
Surround to Fr. Right	38dB
Fr. Centre to Left Surround	47dB
Surround to Right Fr.	38dB
Fr. Centre to Right Surround	47dB
Surround to Centre	32dB

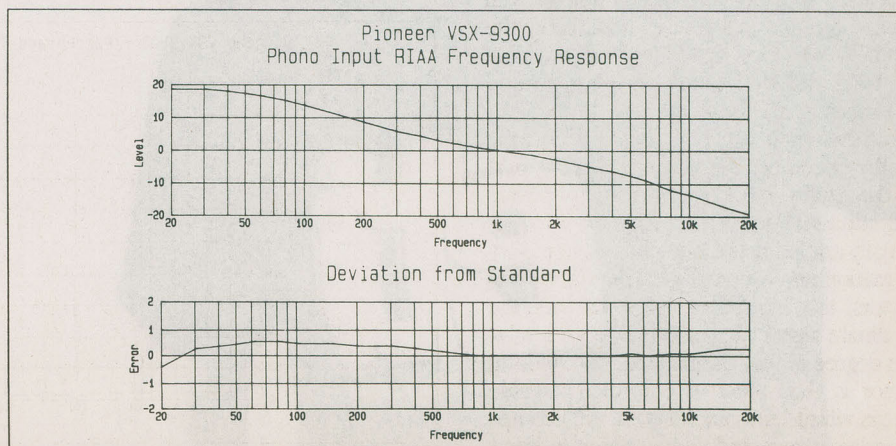


Fig. 5. Phono input RIAA response (top) and deviation from the standard (bottom).



# Looking Back

**In which a former editor of this publication drags himself to the keyboard and reminisces tearfully about the glorious past, interjecting the odd lie and half truth to keep things interesting.**

STEVE RIMMER



It all started in a 10,000 watt radio station. Well, sort of. I recall sitting in the control booth with my feet up on the mixing board and something really obscure rattling in the speakers — Golden Earring or Captain Beefheart or Blue Cheer — one of those bands that made your ears bleed if you went to sleep with headphones on. It was one of those days when you think of what it'll be like in a year from now, playing the same records and wondering the same things.

It occurred to me at this juncture in time that it'd be a good idea to think about getting a proper job. I was staring debt that bordered on indentured servitude square in the face, and only one of us was enjoying the prospect. The allure of radio had long since dissipated.

I was perusing a copy of one of the magazines I wrote freelance stuff for when I noticed that they wanted an editorial assistant. The idea sparked my imagination. It would be interesting to work in a place with a horizontal ceiling. Journalism seemed to be one of those professions which shares with radio a lack of pressing demands on one's wardrobe. It seemed like a regular paycheck without the need to wear a suit.

The record prepared to end. I put a tape on and tried to decide how many lies I could tell on a resume without its being obvious.

Within a week I was trying to figure out how to get a Consumer's Distributing desk on top of the boss's station wagon so I could have a real flat space to work at as assistant editor for ETI. Things were unquestionably looking up.

## **International Blue Velvet**

Electronics Today International, as it was called at the time, was a very different sort of magazine when I started working for it. The company was a lot smaller, for one thing. I think there were about eight people there when I showed up. With the exception of Halvor Moorshead, who actually started the company and owns the whole party, I'm the last one of that crowd still to be associated with the company it has become.

The company had just finished its first expansion when I arrived, propitiously, two days after all the moving had been completed and the heavy lifting was over with. The new offices were spacious, with everyone having a desk and a room to put it in. Within the year they'd be cramped again, and within a year after that the company was to become split over two buildings. Things were growing.



The former assistant editor of Electronics Today, John Van Lierde, was leaving to go back to school. I was to spend three months as the editorial assistant on the magazine, and then step up to his job.

Working for a small publishing company is rarely boring. Halvor liked to say that a lot. Because the company couldn't afford to have all sorts of specialized people on staff, the assistant editor was expected to be quite a few of them. This included handling things like photography, writing, designing projects, lifting boxes of magazines and building trade show booths.

One of the perennial problems at the time, one which has not really gone away to this day, was figuring out what to stick on the covers. Occasionally this would work itself out because something in the magazine would engender an obvious stock photograph. Most of the time, though, we had to take the pictures ourselves. We had this camera, sort of, an aging Bronica which had more loose pieces than tight ones. It tended to come springing apart at odd times, occasionally launching bits of itself into space when you attempted to wind the film on. Some of the unusual cropping that showed up on the ETI covers of the day were not so much inspired photography as compensation for light leaks.

One of the more original covers had to do with soldering. The idea was to have a soldering iron that seemed to be burning through the cover, exposing the first few pages beneath. The effect was coming along nicely when the cover it was burning through caught fire before the camera.

When I arrived at ETI, the magazine was being typeset on an IBM composer, which is a sort of glorified Selectric typewriter. Shortly after this, we acquired a Compugraphic EditWriter, a *real* typesetting machine. It actually had memory, about eight kilobytes of it, and a monitor rather than a roll of paper. It was so... post-Victorian.

Still a year or two from actually having a working word processor of my own, I used to stay late just to be able to write on the Compugraphic rather than using an electric typewriter. The thought of doing anything meaningful on it is frightening now, but at the time it was so unspeakably high tech.

About eleven minutes after the warranty on the Compugraphic expired, it did too. Service men came and service men went, but the Compugraphic remained obdurate. It worked about half the time, and emitted long strips of uniformly black galley film for

the other half. It was over a month before we realized what the problem was. Cindy, the girl who actually set the type, had a fetching smile and equally fetching curves. The service men showed up but they just stood there, transfixed, and never got anything done. Cindy thought it was the funniest thing she'd seen in ages.

After a long time Compugraphic admitted that they couldn't fix the machine. Halvor and I took turns sitting in the typesetting room with an oscilloscope, a pile of schematics which turned out to be for the wrong machine and a desoldering bulb. After a long time we managed to replace most of the bad memory in the thing, and it limped reluctantly into the future. Halvor promised me that one day we would take the Compugraphic out into the parking lot and blow it to hell. This thought sustained me in my darker days.

The most popular project of the entire time I was working there was the amazing 400 watt amplifier. It used a whole bucketful of output transistors, a power transformer that came with its own pickup truck and a heatsink which caused a modest aluminum shortage every time someone tried to build one, but it certainly could pump out 400 watts. There were three or four places around town selling kits for the things, and they could barely keep all the parts in stock.

A lot of souls built these things who shouldn't have. People would try them out with ten watt car speakers and discover, amidst a lot of burning paper and smoking alnico five, that a four hundred watt amplifier can put out better than ten watts of hum and background noise if you aren't careful. My favourite four hundred watt amplifier tale is about a fellow who called and wanted to know if he could build two and bridge them to get one and a bit kilowatts out of them. Headphones of the gods, to be sure.

### Flasks and Beakers

A part of ETI was scientific, rather than electronic. In months wherein nothing much was happening electronically, the purely scientific bits sort of swelled up and overwhelmed the magazine. One of the most notable of these was the dreaded Shroud of Turin issue. It wasn't really planned that way, but the other features in the magazine were solid, workable and not really cover material. There was, however, this really interesting bit about the shroud that was supposed to have been using to bury Christ in.

The problem with the shroud article

was that if it had been just a bit longer it could have been a book. Not knowing a whole lot about the shroud, and, as such, not knowing what could be edited out of the thing, I was at a bit of a loss over how to reduce the thing beyond simply removing its voluminous padding. As such, it ran a little long.

About two month ago, someone actually got to carbon date the ol' shroud. It turns out, after all the fuss that's been devoted to it, to have been a medieval fake. Nice try, though.

People liked to think of ETI as having a monstrous project laboratory with at least a dozen lab coated technicians running around spouting differential calculus at anyone who would listen. This wasn't exactly the case. When John Van Lierde left and I moved up a notch, there was this free desk in my office. It became the project lab. Prior to this, I think the project lab had been the kitchen table in John's apartment.

We were a bit shy of equipment, too. Most of it was mine. The oscilloscope used only the best 1950s vintage vacuum tubes, and I rarely attempted to design anything which required looking at non-sinusoidal waveforms much above twenty kilohertz during this period; the limited frequency response of this aging box tended to make everything above the audio spectrum into sine waves, and damned small ones at that. By comparison, the signal generator could only do unclipped sine waves above about five kilohertz, and then only if it was lying on its side. I had a capacitor meter which always said that the capacitors it was testing had shorted, which it turned out they always had, as it was putting about three hundred volts across them.

Despite these little traumas, we did some pretty decent projects. I now have a 60MHz dual trace scope, a working capacitor meter, and the same signal generator, actually... I keep meaning to get a new one. However, it's amazing how little fabulous test equipment really affects what you do. Electronics is very much more ingenuity and very much less expensive tools than most people would imagine.

When I started working there, ETI was being pasted up by a lone artist, Sarah Jane Newman. She worked faster than the human eye could follow. One day Halvor stuck his finger on something she was slicing away at and she very nearly removed it. She maintained that he bled non-repro blue.

While we had an intercom of sorts, Sarah never liked it very much. She communicated with typesetting by shouting. The place had an echo. She had a fairly



## Looking Back

thick accent. The typesetting machine had a pretty loud fan. Communication was not always what it might have been.

The summer after I started, Halvor decided that the company required a second production artist, and he elected to import one. He'd known a fellow named Terry Fletcher back in Britain, and he paid to have him move over here and come to work for ETI. Terry was... unique. The magazine quickly became riddled with little cartoon characters he liked to draw. The schematics he rendered started to sport baroque looking curls and ogives. He liked to shout at Cindy too. Cindy liked to throw things at Terry. That end of the building was a little dangerous close to press day.

Terry and his family moved into a sort of monstrous old house with a five degree list to starboard down near the lake. After a winter of trying to make sense of it, they decided that it would be an asset to have a housekeeper. They sent for the daughter of a neighbour of theirs back in Britain, who came to spend the summer. I recall being told that she was a really nice girl from a good family, and that it would be appreciated by all concerned if I could stay away from her so they wouldn't have to explain to her parents why she was returning in greater numbers than she arrived.

We got married about a year after that. I haven't seen Terry in a long time, but I doubt he's wholly forgiven me. I'm fairly certain Meg's parents haven't forgiven him.

### Big Bang

Testing projects continued to be a chal-

lenge. Halvor arranged for us to get a better scope, which was like something handed down from on high. As the Compugraphic was not ready for detonation at the time, I dropped a brick through the cathode ray tube of the old scope as a substitute. More than satisfying, this.

Great projects are not simply handed to you. It's more of an affliction. Take the amazing movement alarm project. It was a 110 decibel horn in a plastic box with a trembler switch. If you tried to move the box, the horn went off. In order to reset it... well, that was a problem. The trembler was a little sensitive in the early prototype. In fact, just pushing the reset button was enough to set it off. It became obvious that the box had to be dismantled and the batteries removed before everyone went deaf. Suddenly, without any warning, an alien space craft appeared overhead and beamed up all the Phillips screwdrivers... at least, that was my explanation. The horn blared on.

Fortunately, you can't run a 110 decibel horn from a nine volt battery for very long, and it petered out after a while. The lawyer down the hall inexplicably moved to larger quarters a while after that.

One day someone from Commodore called. I'd thought they made office furniture and calculators, but they had this computer and they asked if we were interested in having a look at it. I had nothing going at the time, so I agreed to write it up for the next issue. The next edition of ETI sold as few magazines every did before or will again.

This was really the beginning of the magazine's interest in microcomputers. There'd been features about them before, but this was a machine that people could actually buy and do something with, if admittedly, not all that much. In the next few

months we ran more computer reviews, all received with similar acclamation. Within the year, Halvor had asked me to pass the assistant editor's position for ETI over to someone else and start something called Computing Now.

One of my last functions for ETI was to hire my replacement. Halvor suggested that if I put an ad in the paper I'd probably get about a zillion calls and, for this reason, it would be handy to dream up six simple questions to weed out the people who knew nothing about electronics. The six questions went something like this.

1. What's the value of a resistor with the colours yellow, purple, yellow on it?
2. If you have a transformer with a thousand windings in the primary and ten thousand windings in the secondary, how many volts will come out of it if you put ten volts in?
3. What does AM stand for when used in conjunction with radio reception?
4. Roughly how many ohms of DC resistance would you expect to see across an eight ohm speaker coil?
5. If you have identified the base and the emitter of a transistor, what leads are left?
6. What is the end of a silicon diode with a stripe around it usually called?


We decided initially that we wouldn't consider anyone who couldn't get all these right. Three days into the hiring, when no one had even come close, we decided that we'd at least interview anyone who could manage four of the six — as soon as someone called who could do this. Toward the end, we were down to giving serious consideration to anyone who could get the resistor question and make an intelligent guess at any of the others.

Then one guy called and breezed through the whole works. Bill Markwick came to work as editor of ETI, and, through several magazine name changes and shifts of locale, is still at it.
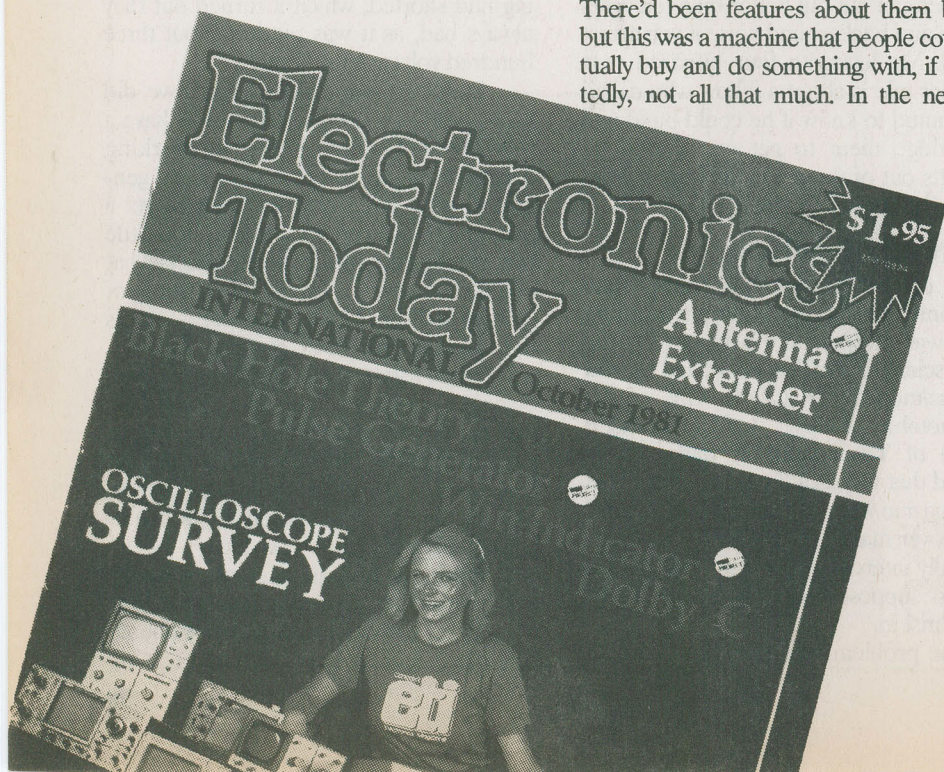
### Closing the Book

There are a lot of people and incidents from this period that I haven't mentioned. I could cite a lack of space, but, in truth, few of them would be interesting out of context. You had to be there.

There's nothing like the inspired chaos of working for a small, dynamic publishing company. If the editions of ETI which we produced during that time lacked polish in a few places, they were unquestionably never dull. Like the job of editing them and making them come to pass, they were always rushing off and doing something different. ■





# MARKET PLACE

## INTRODUCING OUR NEW ICEs

### 1) KEM — 7810

#### In-Circuit Emulator for NEC one-chip CPU uPD7810 series.

This in-circuit emulator can work with any computer which can emulate terminal mode via a RS-232 port. It has a very powerful set of dynamic debugging functions in firmware for both hardware and software designers.

It has two optional boards, KEM — 7810-APPKIT for actual application and a KEM — 7810-CPU with firmware and a sample program to demonstrate the capabilities of this CPU.

**\$899.00**

### 2) KEM — 8031

#### In-Circuit Emulator for Intel MCS-51 family of CPUs.

This unit is similar to KEM — 7810 but for Intel CPUs. It has single-step, de-assemble command, Go (execute), R (input hex file), x (display registers), Block move, F (fill memory), C (compare) and many others necessary for dynamic debugging.

**\$798.00**

For the above units, we provide technical support in the form of coupons (5). Just fax us the question with an attached coupon.

## 36 HOUR SERVICES for prototyping plate-thru' hole

### PRINTED CIRCUIT BOARDS

For fast turn-around of your engineers' design, KEM offers competitive prices for plate-thru' hole PCB in prototyping or sample quantity. Our whole set-up is most efficient in speedy service at an affordable price.

Just send your plot files & aperture list on disk or modem to our dedicated DATALINE.

The PCBs are shipped by Loomis overnight.

Please fax us for more information.

### K.E.M. Electronics Ltd.

Mail to: Box 69126, Station K, Vancouver, B.C. V5K 4W4

Office: 879 East Hastings, Vancouver, B.C. V6A 1R8

Tel.: (604) 251-1514 Fax: (604) 251-5280.

# Get the best of professional desktop publishing

- Brochures •Catalogues •Forms •Instructions
- Parts Lists •Price Lists •Sales Flyers
- Production Information •Technical Documentation
- Training Manuals •Directories
- Corporate Identity Packages •Annual Reports
- Menus •Magazines...
- and much more

Call

# MP

COMMUNICATIONS

Kenneth Marskell  
(416)445-5600

A Division of MOORSHEAD PUBLICATIONS:

1300 Don Mills Road, North York, Ontario M3B 3M8 FAX: 416-445-8149



# Versatile Alarm Circuit

A simple but comprehensive home burglar alarm.

PAUL CHAPPELL

**H**ere's a burglar alarm that can use keyswitches, the usual continuity loop, and an anti-tamper loop. Figure 1 shows the component overlay for the project and Fig. 2a shows the circuit.

Figure 3 shows how to build the completed circuit into a suitable box — a die-cast aluminum box is a good choice — and how to connect up the power supply and relay. The PCB can be held in place with double-sided adhesive pads or tape, or you can drill a hole in the board and use a nut, bolt and spacer. A single bolt will be quite enough — there's nothing heavy on the board. The relay can lie on its back, glued in place, with the contacts facing upwards. The smoothing capacitor C7 can be fixed with a double-sided adhesive pad or with a capacitor clip.

The transform-

er show has two secondary windings; if you're using a 12V centre-tapped type, you can just tape the centre-tap wire out of the way. For the rectifiers D4-D7 you can either use individual 1N4000-series devices or an encapsulated bridge rectifier — whatever you've got in your parts box.

The very first switch in the anti-tamper loop is a microswitch to protect

the control box itself. If anybody removes the lid, the switch will open and sound the alarm. This is one of the many ways the alarm protects itself. The anti-tamper loop prevents any interference with the wiring. Cutting the alarm wires will sound the bell, removing the plug or cutting the power cord will activate the alarm — and it still finds time to protect all the doors and win-

dows in your house, to check up on pressure mats and infrared sensors, and to do all the other things a burglar alarm should.

## Entry And Exit Delay

With so many features, it's hard to imagine what could be added to the basic alarm to fill up the rest of the PCB. But there is one feature you'll find on almost all commercial alarm controllers that the circuit so far doesn't have: entry and exit delay.

With the basic alarm system, the key operated switch to turn the circuit on and off

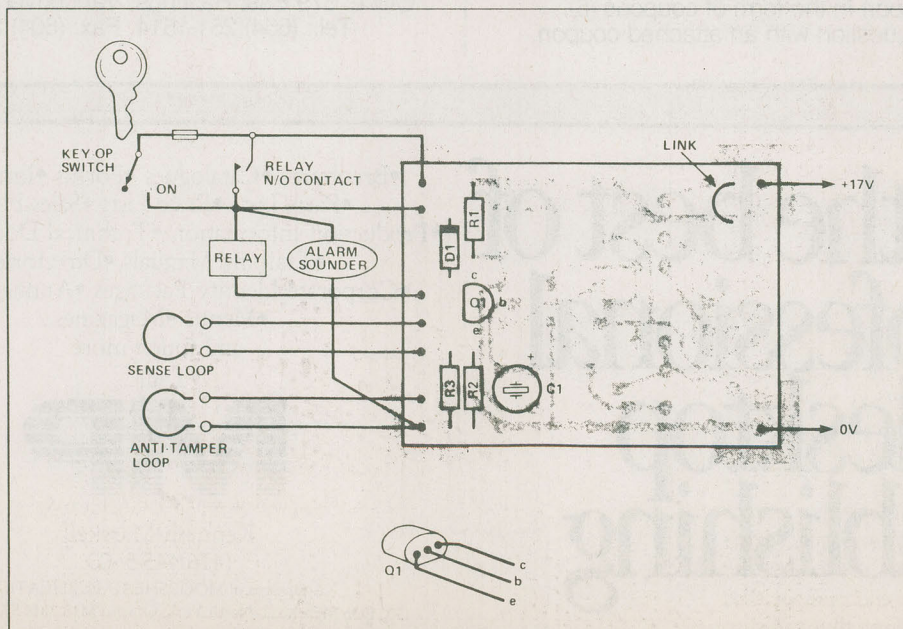


Fig. 1 Component overlay for the free Burglar Buster PCB.



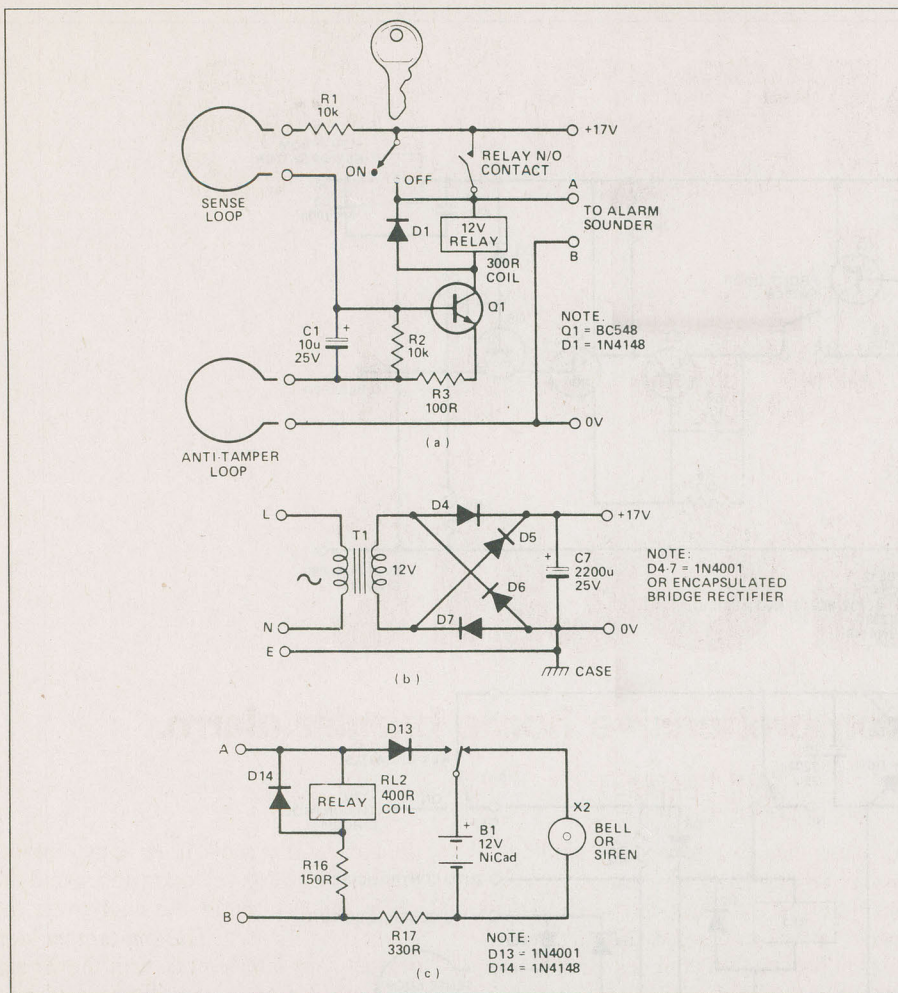


Fig. 2 The circuit diagram of the Burglar Buster (a) The main control box. (b) A suitable power supply (c) A simple alarm siren.

must be outside the house. When you leave, you turn on the alarm from outside. When you return, you turn it back off again before entering the house. The key-op switch being outside the protection of the alarm system, is a point where the circuit can be attacked.

With entry and exit delay, the idea is to wire the front door in a separate loop to all the other doors and windows. When you turn on the alarm, the main loop is activated at once but the front door contact remains inactive for, say, thirty seconds. This gives you time to get out of the house and, as long as the door is closed within the delay period, the alarm won't ring. This time there's nothing outside the house to be interfered with so the alarm system is much safer.

When you return home, there's another delay to give you time to get back in but now it's not enough just to shut the front door — a burglar could manage that easily enough. The only thing that will stop the alarm from being activated is if it's

turned off with the key within the thirty seconds.

The circuit is shown in Fig. 4a. When you turn on the alarm, power is applied to the board, and C4, which will have no voltage across it initially, begins to charge via R6 Q5 and Q4. Transistor Q4 is held on by the charging current and in turn holds on Q3.

If the front door is closed it will prevent C2 from charging. If the front door is open, C2 will charge via R1 and Q2 and after about thirty seconds the current in the main loop will no longer hold Q1 in conduction so that the alarm will sound. Closing the front door during this period will discharge C2 via D2 and the loop will derive its current from Q3 and Q4.

In the meantime C4 is still charging. After about forty seconds the current falls below the value needed to maintain Q4's b-e voltage across R5 and at the same time provide current for Q4. At this point the charging continues via R5 but Q4 now relies on Q3 for its base current. Transistor Q3 is quite happy to provide the base current as long as nobody opens the front door. As soon as this happens, Q3 and Q4 both drop out and since Q5 is no longer supplying them with any priming current they won't switch on again even if the door is closed. Now the only way to stop the alarm from ringing after C2's charge period is to use the key. Otherwise the circuit ticks on remorselessly.

The power supply and relay circuit for this version of the alarm is shown in

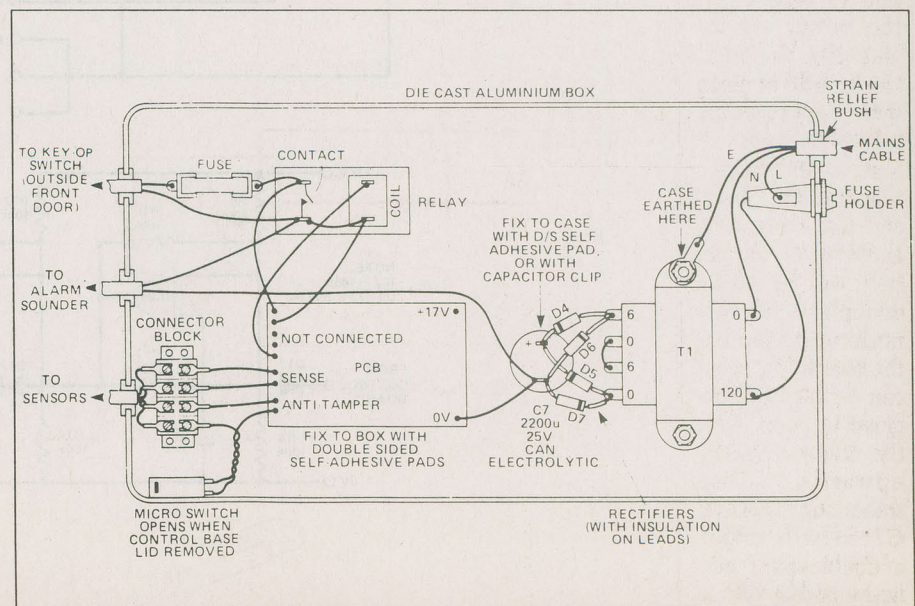


Fig. 3 Installation and off-board wiring.



# Versatile Alarm Circuit


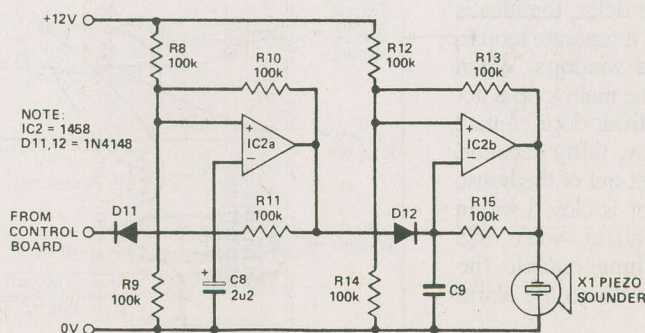
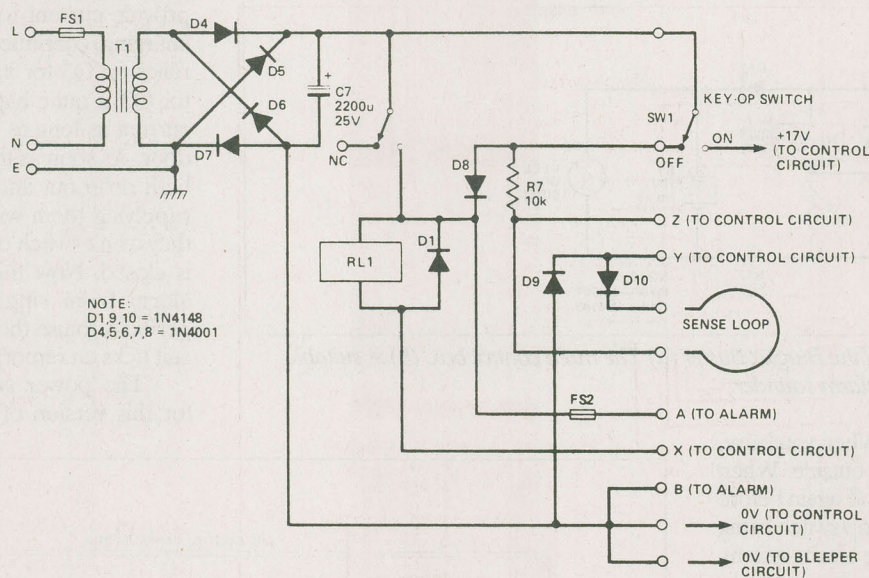


Fig. 4 (a) The expanded control circuit. (b) The expanded PSU and relay circuit. (c) A warning circuit for timed entry and exit.

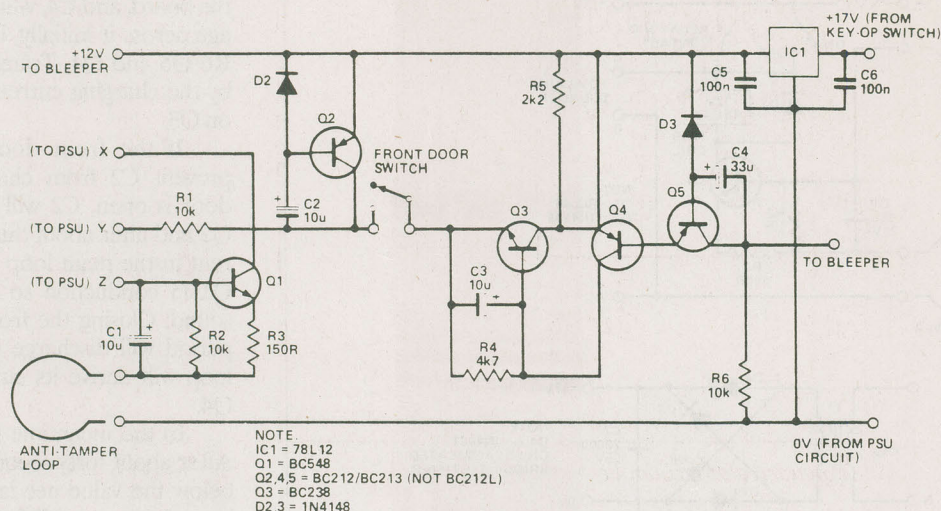

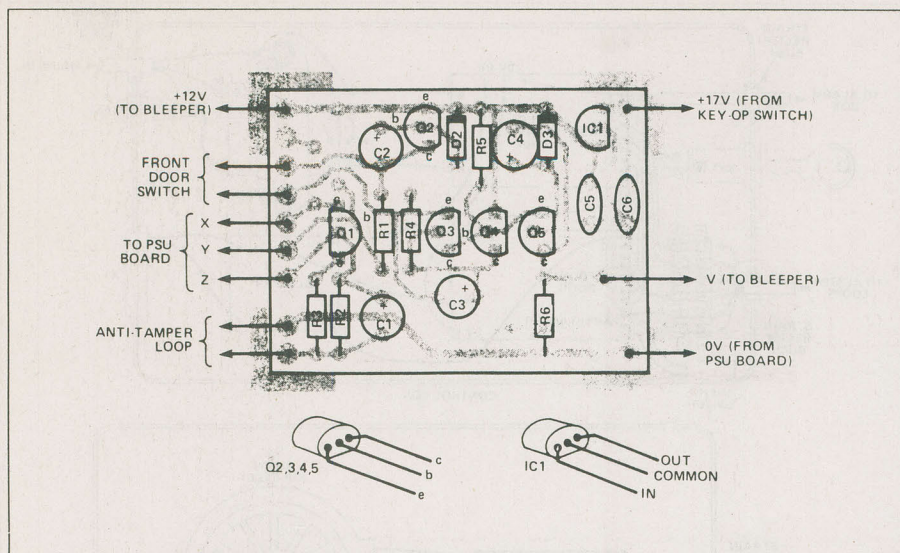


Fig. 5 Component overlay for the expanded alarm controller.

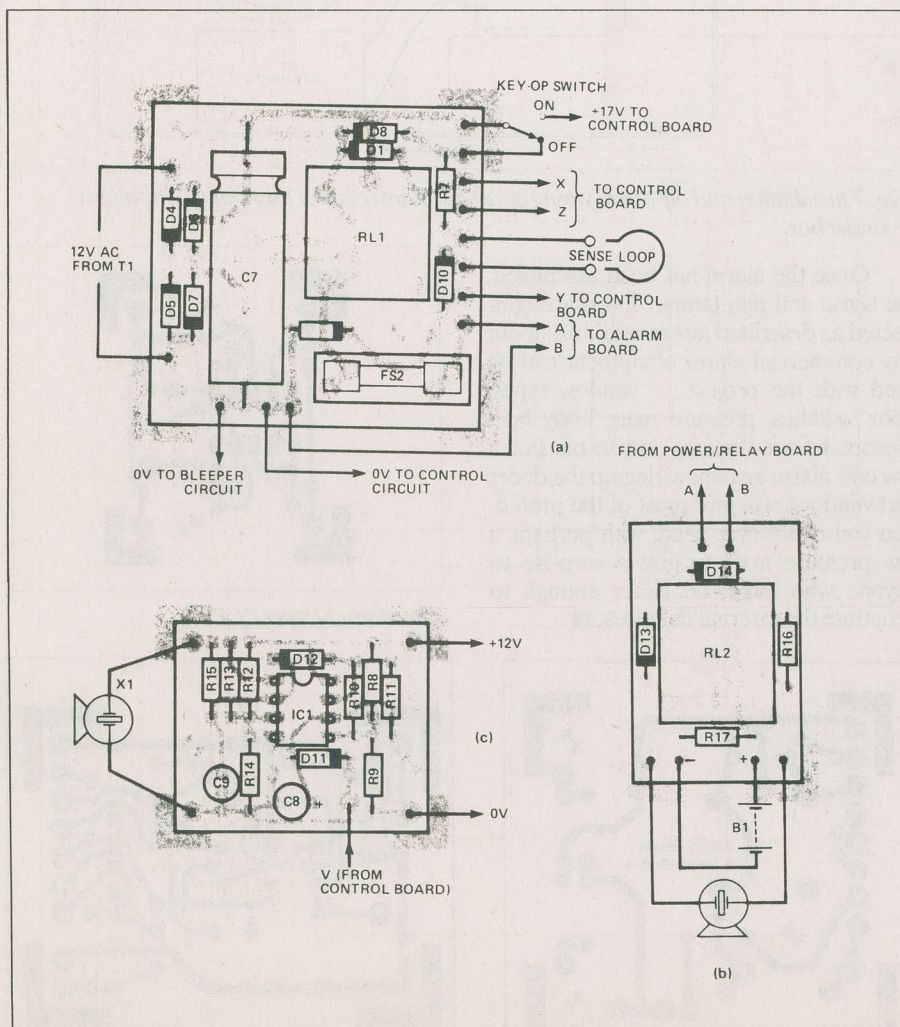


Fig. 6 Component overlays for the expanded Burglar Buster. (a) The power and relay board. (b) The bleeper board. (c) The alarm board.

## PARTS LIST

### Resistors

(all 1/4W 5%)  
 R1, 2, 6, 7 10k  
 R3 100R (150)  
 R4 4k7  
 R5 2k2  
 R8-15 100k  
 R16 150R  
 R17 330R

### Capacitors


C1, 2, 3 10u elect  
 C4 33u elect  
 C5, 6 100n  
 C7 2200u elect  
 C8 2u2 elect (or tant)  
 C9 4n7

### Semiconductors

IC1 78L12  
 IC2 1458  
 Q1, 3 2N3904  
 Q2, 4, 5 2N3906  
 D1-3, 9-12, 14 1N4148  
 D4-8, 13 1N4001
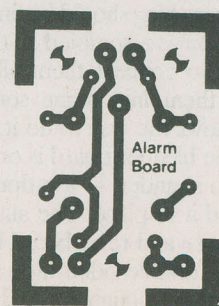
### Miscellaneous

RL1, 2 Relays, 12V  
 300-400R coil  
 X1 Piezo sander  
 X2 12V siren or bell  
 T1 transformer, 6VA, 12V secondary  
 FS1 250mA slow-blow fuse  
 FS2 250mA fast-blow fuse  
 SW1 key operated switch  
 B1 12V or 2x6V NiCad battery  
 Case for control unit, case for sounder unit, panel fuse holder.  
 Fuse clips, connector block, micro switch, strain relief bushes, hardware for mounting transformer and PCBs. Power cable. Connecting wire, door switches, window foils and other accessories to suit your installation.



The alarm board PCB.



## Versatile Alarm Circuit

Fig. 4b. Diode D1 is now mounted on the PSU board to reduce the number of interconnections between the two PCBs. The timing circuit are reset when the key-op switch removes power from the control board. Capacitor C3 discharges through R6 and D3 (in much less than forty seconds since Q5 is no longer in action to multiply up the timing period) and C2 discharges via D2 on the control board and D9 on the PSU board. Components R7 and D10 allow Q1 to work independently of the rest of the circuit — you can change the off position on the switch to a 'standby' function by leaving out D8 so that any interference with the anti-tamper loop will still trigger the alarm when the main loop is disabled.

Figure 4c shows a useful addition to the alarm. It's quite unnerving to turn the circuit on and know that at any moment the alarm might sound, without knowing quite when. The bleeper of Fig. 4c begins to sound as soon as the alarm is turned on. When it stops sounding, you've got about ten seconds left before the alarm deafens you.

The alarm sounder itself is shown in Fig. 2c. This circuit (for use with the basic or expanded versions of the alarm) is built into its own box and mounted so that it can be heard from outside the house. If you put the circuit itself outside, remember to use a weatherproof box. Spraying the circuit with a protective waterproofing compound wouldn't hurt, either.

Component overlays for all these circuits are shown in Figs 5 and 6. None of the circuit boards should give you the slightest trouble. If you are 'expanding' the basic version of the control board, note that R1 is soldered in a different position and that R16 is now 150R to suit the specified relay. Apart from that, try to bend the component leads carefully and not too close to the body (the component's body, not yours.), remember to melt the solder over the joint and not over the iron, don't cook the transistors and IC for too long and everything should be fine.

Once you've assembled all the boards you'll want to connect them all together and build them into some sort of box. Figure 7 shows the way to do it. The best place for the bleeper board is on the back of the piezo sounder — use double-sided tape to hold it in place. The alarm board and the power and relay board both have relays on — double-sided tape might not be quite strong enough to hold them, so both have screw holes. Apart from that Fig. 7 more or less explains itself.



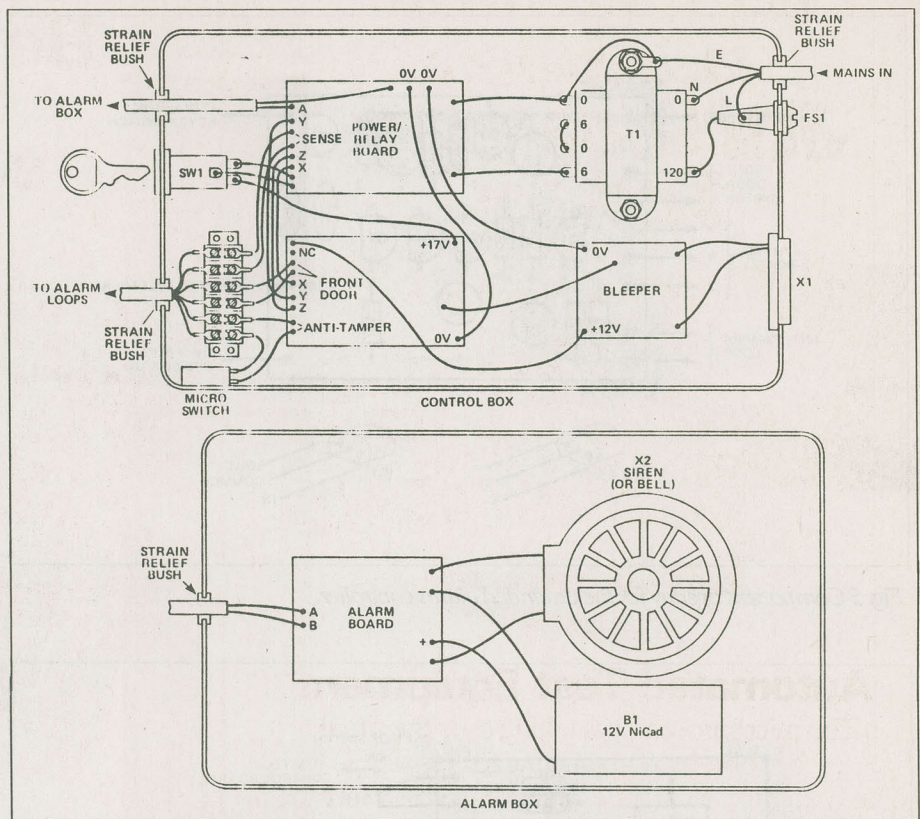


Fig. 7 Installation and off-board wiring of (a) the alarm control box and (b) the alarm sounder box.


Once the alarm has been assembled, the sense and anti-tamper loops are connected as described last month. Just about any commercial alarm equipment can be used with the project — window tapes, door switches, pressure mats, body heat sensors, infrared beams and so on. For a low cost alarm system, wiring up the doors and windows will give most of the protection you could ever need, with perhaps a few pressure mats to give a surprise to anyone who might be clever enough to penetrate the external defences. ■

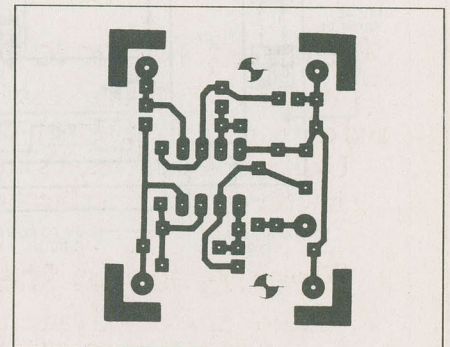

The alarm bleeper PCB.

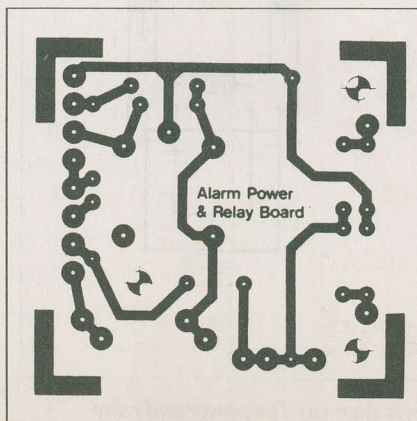

The alarm power and relay PCB.

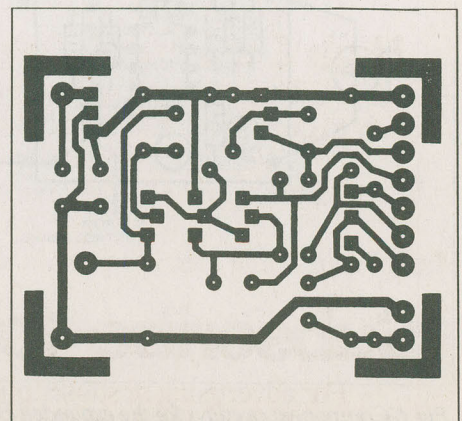


The main PCB, foil side.



# NEXT MONTH IN

## *Electronics & Technology Today*

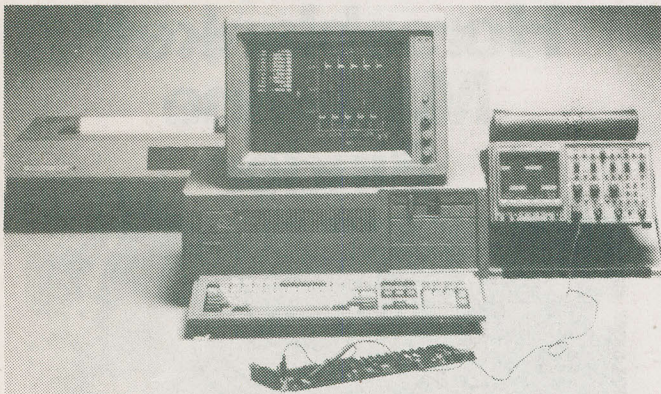

### Automated Test Equipment

The microprocessor is taking over the ritual of point-by-point testing for repair, quality control, etc. It doesn't have to cost a fortune, as you'll see in our roundup of basic systems that save time on the testbench.

### Infrared Remote Project

A simple system that's easy to build and can control a relay for on-off switching. Unlike most remotes, it's immune to interference from ambient infrared.

### Electronics in the 90s

A look at what you can expect in electronic design for the 1990s, based on what's cooking in the labs now.

### High Definition Television

Hi-def TV is a reality, with several systems ready to go as soon as standards are developed.

We look at what's new in the wide-screen, 1000-line market.


Plus, of course, the usual projects, articles and news!

## Subscribe today!

For advertising or subscriptions, please call (416) 445-5600, FAX 445-8149.

**SUBSCRIBE TODAY**  
Be sure of your  
issue  
each month

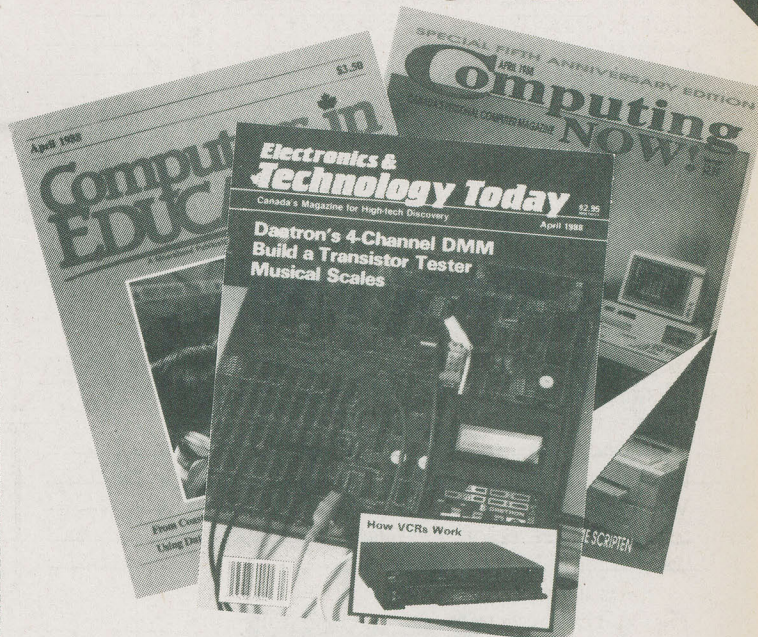SEE SPECIAL  
SUBSCRIPTION  
OFFER ON PAGE 32



### Moorshead Publications

1300 Don Mills Road, Toronto, Ontario M3B 3M8

**SUBSCRIPTIONS:** ☐ NEW SUBSCRIPTION ☐ RENEWAL

**Electronics & Technology Today**

☐ One year (12 issues) \$22.95 ☐ Two years (24 issues) \$37.95

**Computing Now!**

☐ One year (12 issues) \$22.95 ☐ Two years (24 issues) \$37.95

**Computers in Education**

☐ One year (10 issues) \$25.00 ☐ Two years (20 issues) \$45.00

**Outside Canada (US Dollars)**

For U.S. please add \$3.00 per year ☐ Other countries add \$5.00 per year ☐

NAME

ADDRESS

TOWN/CITY  PROVINCE/STATE

CODE  DATE

POSTAL CODE

☐ Cheque enclosed DO NOT send cash

☐ MasterCard Account No.

☐ Visa Account No.

☐ American Express Account No.

Expiry Date

Signature

To order Books, Back Issues, Binders, Software and Special Publications, see over.



# ORDER FORM

## Software

_____	_____	\$	_____
_____	_____	\$	_____
_____	_____	\$	_____
	Sub Total	\$	_____
	Tax (Ontario Residents) 8%	\$	_____
	Postage	\$	_____
	Total Enclosed	\$	_____

## Bookshelf

CODE (e.g. BP12)	TITLE (Short form acceptable)	PRICE
_____	_____	\$ _____
_____	_____	\$ _____
_____	_____	\$ _____
_____	_____	\$ _____
_____	_____	\$ _____

## Special Publications

ITEM	QUANTITY	AMOUNT
_____	_____	\$ _____
_____	_____	\$ _____

## Binders


ITEM	QUANTITY	AMOUNT
Moorshead Publications \$9.75 each (Ontario Residents add 8% P.S.T.)	_____	\$ _____

## Back Issues

\$4.00 each. Ontario residents add 8% P.S.T. Some issues may be out of stock. Please call the Reader Service Department at (416)445-5600 or enclose a self-addressed, stamped envelope for a complete list of available issues.

Orders from the Bookshelf are tax exempt.  
Please add \$1.00 for postage.  
Ontario residents add 8% P.S.T.  
for Specials and Software.
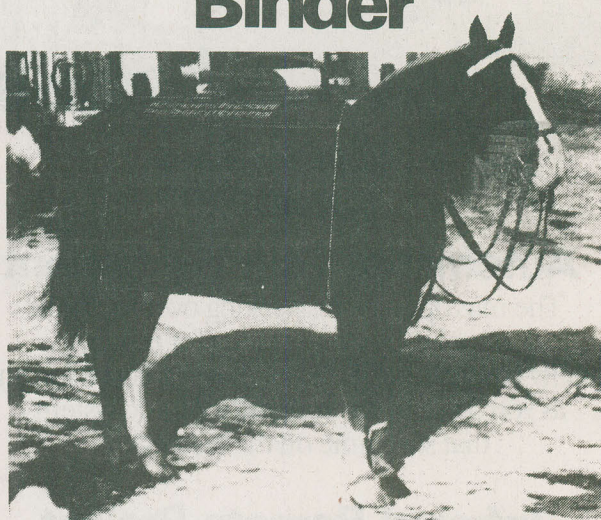
# The Electronics and Technology Today Horseblanket/ Magazine Binder



One day one of Toronto's Finest parked his horse at the firehall next door to us, making him fair game for yet another in our series of great, unforgettable, stupid binder ads.

Our binders are covered in sturdy vinyl, and use spring rods to hold a year's worth of magazines without cutting or punching, allowing them to open flat for reading or photocopying.

They're available from us for \$9.75, which includes postage and handling. Ontario residents add 8% (Ouch!) provincial sales tax.

We would also like to point out that  
(a) Toronto policemen generally use cars, and  
(b) because the binders are magazine-sized, they work as blankets only if the horse is under 36 inches long.

Send to:

**Binders**  
**Moorshead Publications**  
1300 Don Mills Road, Toronto, Ontario M3B 3M8



# Train for a High-Paying Career as a Computer Service Technician

**Only NRI teaches you to service all computers as you build your own fully XT-compatible micro—now with 512K RAM and 20 meg hard drive!**

Jobs for computer service technicians will almost double in the next 10 years according to Department of Labor projections, making computer service one of the top 10 growth fields in the nation.

Now you can cash in on this opportunity—either as a full-time industry technician or in a computer service business of your own—once you've mastered electronics and computers the NRI way.

## **Get inside the powerful, fully XT-compatible Packard Bell computer system**

To give you hands-on training with the absolute in state-of-the-art computer technology, NRI includes the powerful new Packard Bell VX88 computer as the centerpiece of your training. You build this 512K, fully IBM PC/XT-compatible computer from the keyboard up, plus you now go on to install a 20 megabyte hard disk drive to complete your total computer system.


## **Understanding you get only through experience**

You need no previous background in electronics to succeed with NRI. You start with the basics, rapidly building on the fundamentals of electronics with bite-size lessons. You perform hands-on experiments with your NRI Discovery Lab® and then move on to master such advanced concepts as digital logic, microprocessors, and computer memories.
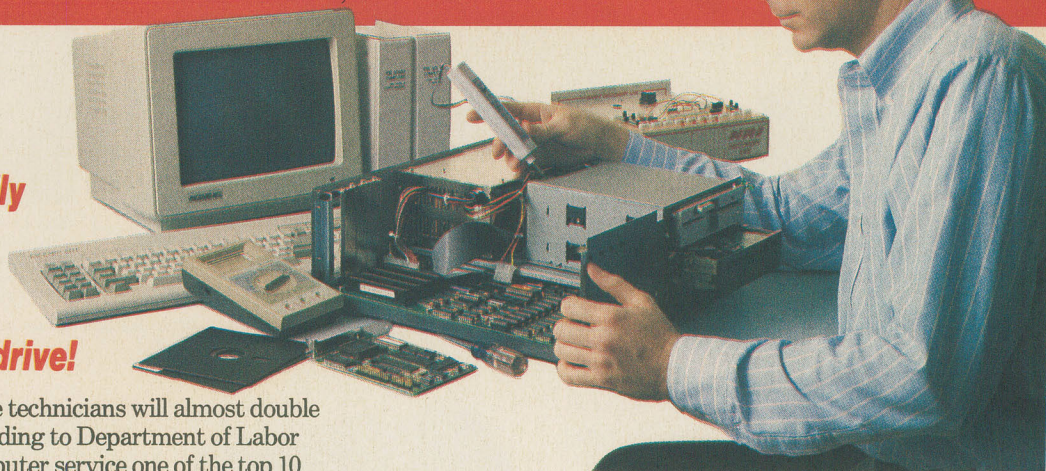
## **Learn at home in your spare time**

With NRI, you learn at your own convenience in your own home. No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. And all throughout your training you've got the full support of your personal NRI instructor and the entire NRI technical and support staff. They're always ready to answer your questions and help you whenever you need it.

Get all the facts from NRI's free 100-page catalog. Send today!




## **Your incomparable hands-on training includes all this:**

NRI's unique Discovery Lab® lets you design and modify circuits, diagnose and repair faults • Hand-held digital multimeter, complete with "talk-you-through" instructions on audio cassette • Digital logic probe lets you visually examine computer circuits • The latest Packard Bell VX88 computer with "intelligent" keyboard and 5¼" floppy disk drive • 20 megabyte hard disk drive you install internally • 16K ROM, 512K RAM • MS-DOS, GW-BASIC, and exclusive word processing, database, and spreadsheet software • Reference manuals, programming guidelines, and schematics.

**See other side for highlights of NRI "hands-on" computer training** →

## SEND CARD TODAY FOR FREE NRI CATALOG

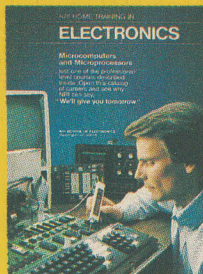

### COMPUTERS AND MICROPROCESSORS

This training prepares you to service all computers as you build your own fully IBM PC/XT-compatible computer. Total systems training includes 5¼" floppy disk drive, 20 meg hard disk drive, monitor, test equipment, software, and the NRI Discovery Lab®.


### ☒ Check one FREE catalog only.

- |  |  |
|--|--|
| <input type="checkbox"/> Computers and Microprocessors | <input type="checkbox"/> Security Electronics        |
| <input type="checkbox"/> TV/Video/Audio Servicing      | <input type="checkbox"/> Electronic Music Technology |
| <input type="checkbox"/> Robotics                      | <input type="checkbox"/> Basic Electronics           |


Name _____ (Please print) _____ Age _____	
( )	
Address _____	Telephone _____
City/Prov./Code _____	



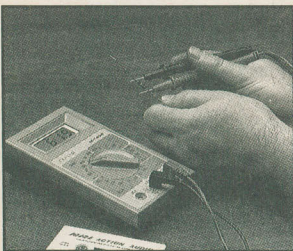
# Get In-Demand Computer Servicing Skills With NRI "Hands-On" Training



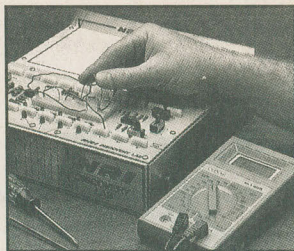
Using NRI's unique Action Audio Cassette, you're talked through the operation and practical applications of your hand-held digital multimeter—the basic, indispensable tool for the computer specialist.



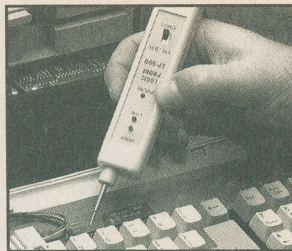You set up and perform electronics experiments and demonstrations using your NRI Discovery Lab®. You even interface the lab with your computer to "see" keyboard-generated data.



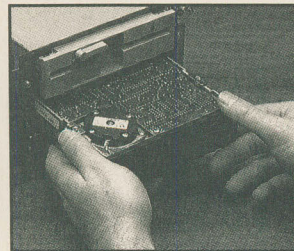After you build this digital logic probe, you explore the operation of the Packard Bell detached "intelligent" keyboard and its dedicated microprocessor.




Next, you install the 5¼" floppy disk drive, learning disk drive operation and adjustment. You later improve your data storage capacity dramatically by installing a powerful 20 meg hard drive.
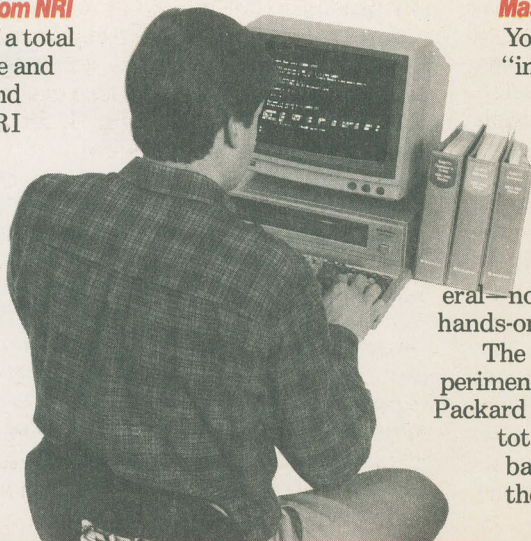
## Total Computer Systems Training, Only From NRI

No computer stands alone . . . it's part of a total system. So if you want to learn to service and repair computers, you have to understand today's computer *systems*. And only NRI builds meaningful training around just such a powerful computer system—the new Packard Bell VX88 computer, complete with monitor, floppy disk drive, hard disk drive, and valuable software—all yours to train with and keep.

The VX88 features full IBM PC/XT compatibility, the breakneck speed of an advanced CMOS V40 CPU, and big-system raw power: 512K RAM and full expandability for future system growth.



## Mastery Is "Built-In"

You assemble the Packard Bell "intelligent" keyboard, install the power supply and 5¼" floppy disk drive, and attach the high-resolution monitor. You then go on to install a powerful 20 meg hard drive—today's most-wanted computer peripheral—now included as part of your NRI hands-on training.

The many demonstrations and experiments you perform as you build your Packard Bell computer system give you a total mastery of computer operation, based on a thorough knowledge of the intricacies of computer theory.

## SEND CARD TODAY FOR FREE NRI CATALOG

### Business Reply Mail

No Postage Stamp  
Necessary if mailed  
in Canada

Postage will be paid by



## NRI SCHOOLS

McGraw-Hill Continuing Education Center  
330 Progress Avenue,  
Scarborough, Ontario  
M1P 9Z9



### 100-Page Free Catalog Tells More . . . Send Today!

Send the postage-paid card today for NRI's free 100-page catalog that gives all the facts about NRI computer training, plus career training in robotics, TV/video/audio servicing, electronic music technology, and many other fields. If the card is missing, write to NRI at the address below.

IBM is a registered trademark of International Business Machines Corp.

## NRI School of Electronics

McGraw-Hill Continuing  
Education Center  
330 Progress Avenue  
Scarborough, Ontario M1P 2Z5



# How Stepping Motors Work

Precise control of rotating shafts is possible with these unique motors.

DR. H. VIRANI

**E**lectric step motors are ideally suited for driving the lead screws of numerically controlled machines. The quantized stepping motion is readily specified in digital form; hence the motors are simply controlled by computers.

A typical positioning system comprises a lead screw or rack and pinion driven by an electric motor. The expense of a DC motor, together with its associated position measuring system and controller, has caused many manufacturers to adopt step motor drives. These drives allow simple control and can give reliable adjustment-free operation in a properly designed system. However, it is worth noting that at least one major computer manufacturer has switched from step motors to DC motors because of "mechanical adjustment problems". When the position is determined numerically, it is quantized. The quantization error is usually (but not always) set to be less than the backlash and pitch errors in the mechanical system. For an electric step motor, the position quantum is typically one step, although this may be less if micro-stepping is used. Step sizes typically range from 0.36 to 30 degrees (1000 to 12 steps per revolution) but may be as small as 0.0014 degrees in microstepping applications.

In a numerically controlled machine, the position is determined by a computer and the position quantum is normally set equal to the movement produced by a single motor step. This provides a direct correspondence between the positioning system and the position number within the computer. Thus it is possible to implement a very simple position control system by using a micro computer and a step motor. Such a system is shown in Fig. 1, for a three phase reluctance step motor.

In the next section, the various types of step motors are briefly described. This is followed by a brief outline of the types of electronic drive circuits used for step motors.

## Step Motors

There are three types of electric step motors: the variable reluctance (VR) step motor, the permanent magnet (PM) step motor, and the hybrid step motor. These are described in order. A VR step motor is shown schematically in Fig. 2.

It operates by attracting the nearest pair of rotor lugs to the stator pole pair which is magnetized. The rotor moves so as to align the lugs with the active pole pair. Further active phase (which supplied the current to the active coil) is turned off and the next phase is activated. The new

active phase establishes a new magnetic field displaced from the original field and the rotor moves to realign its salient poles with the new stator field. The process continues as further steps are taken.

The VR step motor will operate with phase currents in either direction. Thus a minimum of three phase is required to establish reliable rotation characteristics. The three phases may supply three sets of coil wound on a single laminated stack as shown in Fig. 2. This configuration is known as a single stack VR step motor and it is commonly used in small low cost motors.

Alternatively, each phase may be wound on its own stack of laminations which is keyed into a housing. Up to seven stacks can be keyed into the housing at appropriate angles. This would be known as a seven stack VR step motor. Multistack VR motors typically use a common rotor. The mutual coupling between phase of a multistack VR motor is much less than for a single stack VR step motor.

The PM step motor has a cylindrical rotor which has alternating north and south permanent magnetic poles distributed around the circumference of the rotor. At least two phases are attached to the stator coils with the same number of magnetic pole pairs on the stator. The magnetization of these stator poles can be

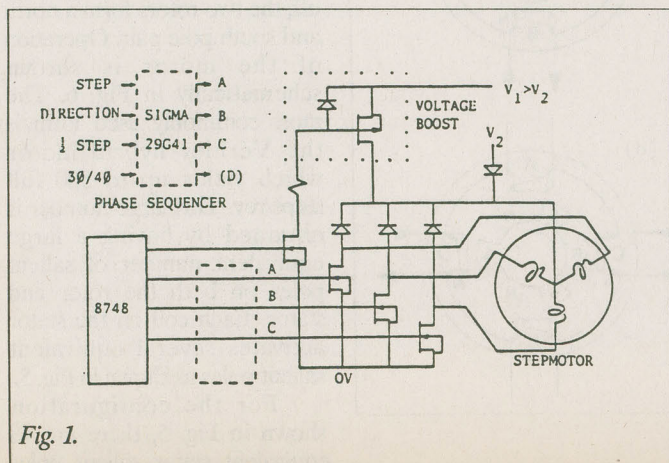


Fig. 1.

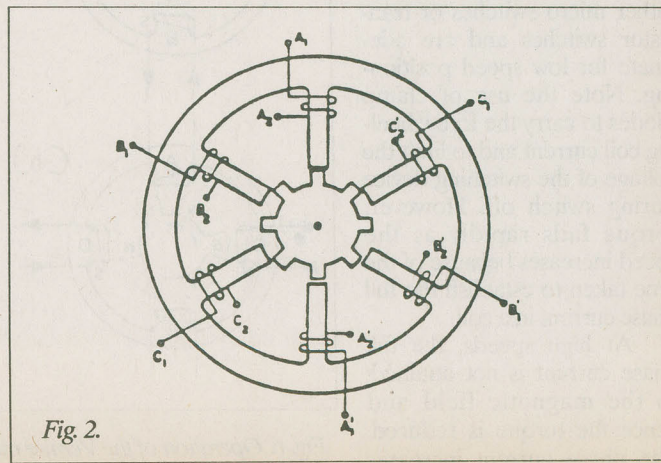


Fig. 2.



# How Stepping Motors Works

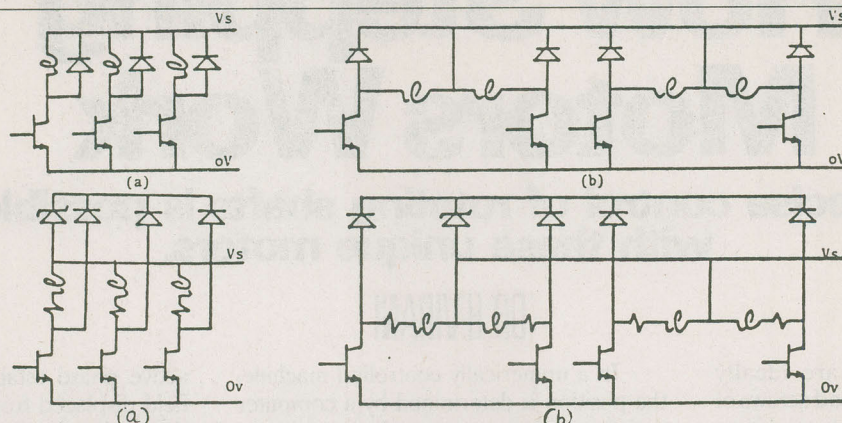


Fig. 3a and b (top) Simple switched drives for VR (left) and hybrid or PM motors (left).  
Fig. 4a and b (bottom) Drives for bifilar-wound motors.

moved one step by reversing the current in one phase. The rotor then moves by one step to realign its magnetic poles with the opposite magnetic poles on the stator. The permanent magnets on the rotor generate a large back emf at high step rates. This precludes the simple switched drive circuit in high speed positioning systems.

Some PM step motor systems include velocity feedback coils and are quite suitable for microstepping applications. The hybrid step motor combines features of both VR and step motors.

A pair of offset salient rotors are on the same shaft. The rotors are separated by an axially aligned permanent magnet; the drive schematic for such a bifilar-wound step motor is shown in Fig. 3b.

## Drive Circuits

A simple switch unipole drive for variable reluctance motors is shown in Fig. 3a, and a drive for bifilar wound PM or hybrid motors is shown in Fig. 3b. These simple drives could use either micro switches or transistor switches and are adequate for low speed positioning. Note the use of clamp diodes to carry the free wheeling coil current and to limit the voltage of the switching device during switch off. However, torque fails rapidly as the speed increases because of the time taken to establish the full phase current in a coil.

At high speeds, the full phase current is not attained, so the magnetic field and hence the torque is reduced. The phase current increases

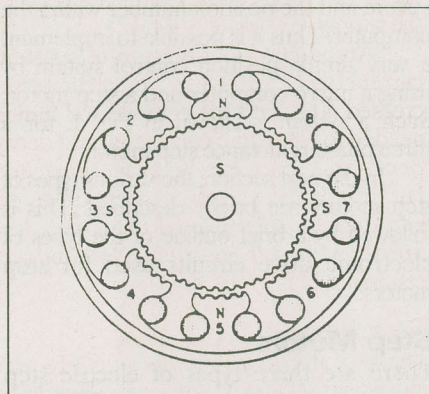


Fig. 5. The Vernier stepping motor has a large number of poles for up to 500 steps/rev.

from zero and exponentially approaches the rated value. The time constant for the exponential rise is  $L/R$  where  $L$  is the inductance of the coils attached to the phase and  $R$  is the total phase resistance. For the simple drive circuits shown in Fig. 3,  $R$  is the resistance of the coils. The current risetime constant can be reduced by increasing the phase resistance as shown in Fig. 4a and 4b.

The supply voltage is increased so that the same maximum phase current is attained. There is another current reducing effect present in PM and hybrid motors at higher speeds. The permanent magnets on the rotor generate a back EMF which increases with speed. This decreases the effective voltage across the coils which results in reduced torque. Thus the increased supply voltage decreases this effect and is a great advantage for these motors.

Volts up to 240V DC are used.

When a phase is switched off, the two rotors form a north and south pole pair. Operation of the motor is shown schematically in Fig. 6. The most commonly used form is the Vernier hybrid motor which yields up to 500 full steps/rev. This large number is obtained by having a large equivalent number of salient poles on both the rotor and stator. Each coil on the stator activates several equivalent salient poles as shown in Fig. 5.

For the configuration shown in Fig. 5, there are 48 equivalent stator salient poles

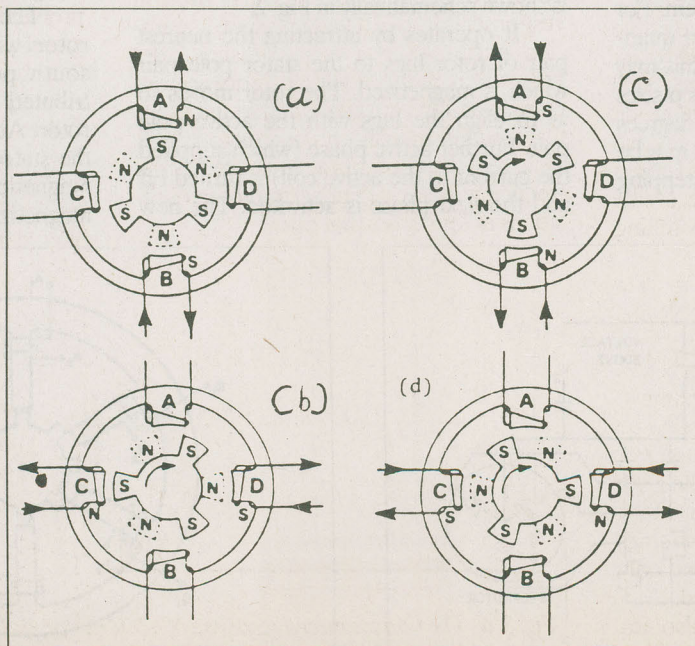


Fig. 6. Operation of the Vernier motor.



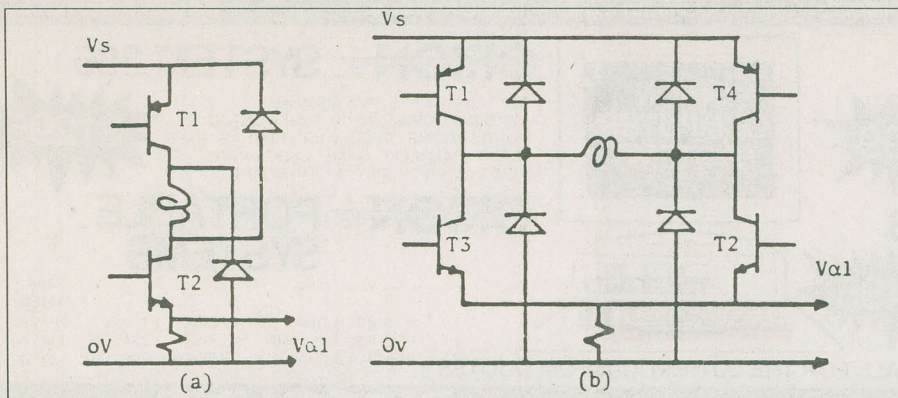


Fig. 7(a) A single-ended drive circuit with suppression (freewheel) diodes, and (b) a bridge circuit which doubles the voltage applied to the load.

on four pole pairs (2/phase) and 50 rotor salient poles which gives 200 full steps/rev. Torque is increased by axially extending the stator coils and adding more pairs of magnetized salient rotors along the rotor shaft.

The motion of the hybrid step motor is dependent on the magnitude and direction of the magnetic field in the air gap. Hence a PM or hybrid step motor will often have two windings on a pole so that a magnetic field can be established in either direction by using one or other of the two coils. This continues to circulate through the freewheel diodes which protect the transistor switches against destructive breakdown voltages.

The phase current gradually decays to zero as does the magnetic field produced by the "off" phase. This decaying field contributes a new "on" phase.

The time for which the negative torque component acts is reduced by including active suppression of the "off" phase current by means of Zener diode (or equivalent). This increases the reverse voltage across the phase when it is turned off. Suppression voltage limits are set by the high voltage limit of the switching device less the supply voltage.

A bridge circuit such as that shown in Fig. 7 doubles the effective voltage applied to a coil.

However, it does require four switching devices per phase for the common two phase hybrid step motor. This may be reduced to two devices if a split power supply is used, but this doubles the high voltage requirements of the devices. For a three phase PM step motor, the windings can be connected in star or delta and only two devices per phase are connected.

The bridge circuit shown also includes a current sensing resistor so that the drive current can be controlled to

produce a constant current output. This is effective at all but the highest step rates when the motor's back emf approaches the supply voltage.

An additional advantage of constant current drives is that the torque can be increased 40%, and the complicated timing needed to overcome current lag and decay problems can be largely ignored. However, these constant current drives do introduce considerable RFI and the additional current harmonics may induce resonance in the motor.

## Resonance

The slow stepping response of a VR step motor is shown in Fig. 8a, and it illustrates the underdamped second order response of the system.

Notice in Fig. 8b, that the motor has reversed because of forward motion response. It is found that unreliable operation occurs over a band of step rates centred on those at which resonance occurs, ie, at the natural frequency and its integral subharmonics. In some motors, limit cycle resonance occurs at twice the natural frequency step rate, and parametric oscillations at four times that rate.

## Reliable Operation

In all cases, resonance effects are reduced by increasing the amount of energy dissipated during each step. Increases in the friction load, changes in gearing, back lash reduction or drive voltage changes can all affect resonance of the step motor. These can also adversely affect the maximum speed. A viscous Lanchester damper has the advantages of damping only the acceleration. Hence it does not reduce the top speed but does reduce resonance. However the device does require periodic adjustment and can be difficult to set correctly.

The above suggestions can cure many resonance problems but other requirements may preclude their use. The use of feedback can eliminate resonance. Essentially off phases are operated at less than 1% of rated current by a constant current chopper drive circuit and the on phase is operated at 100%. The current rise time for an off phase is proportional to the inductance in that phase, and hence to the rotor position. Thus the feedback information is obtained within the electronic drive circuitry and the motor is completely standard. This approach is well suited to multi-stack VR motors.

## Conclusions

In many applications, a step motor is an open loop control system that gives excellent results, as both its position and velocity are predetermined. The addition of electronic rotor position detection provides actual position and velocity information which can be used to overcome resonance problems. The step motor may then run as a brushless DC motor, but it does not need the expensive position encoders and velocity tachometers required for DC motors. The step motor is ideal for numerically controlled systems and robots, as the motor is simple and the complexity is restricted to the drive circuitry, which is remote from the machinery. ■

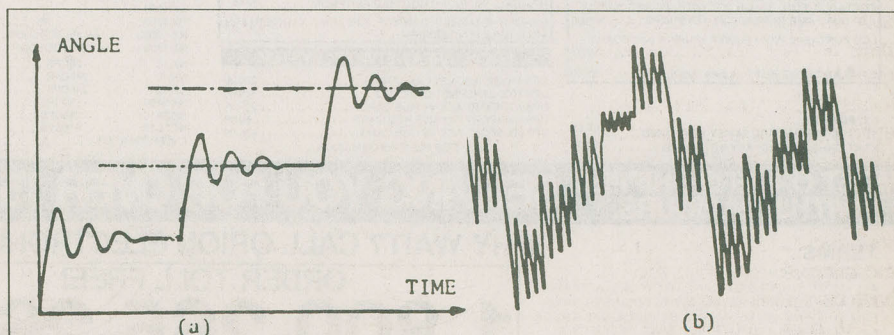


Fig. 8(a) The underdamped response of a VR motor. In (b) the motor has reversed because of forward motion response.





IMPORTERS &amp; DISTRIBUTORS

ELECTRONICS SUPPLIES INC.

INDUSTRIAL — COMMERCIAL — EDUCATIONAL

SALES &amp; SERVICE

## ORION SYSTEM 88


4.77/10 MHZ MOTHER BOARD, 256K MEMORY  
360K DISK DRIVE AND ADAPTER, MONO-  
CHROME OR COLOUR VIDEO, ADAPTER,  
SERIAL, PARALLEL, GAME, CLOCK PORT,  
150W POWER SUPPLY, AT KEYBOARD.

\$599

## ORION SYSTEM 386

1MB MEMORY, 16/20 MHZ MOTHER BOARD,  
1.2MB DISK DRIVE, 16 BIT DISK CONTROLL  
MONOCHROME OR COLOUR VIDEO ADAPTER,  
SERIAL, PARALLEL, GAME, CLOCK PORT,  
200W POWER SUPPLY, AT KEYBOARD.

\$2495

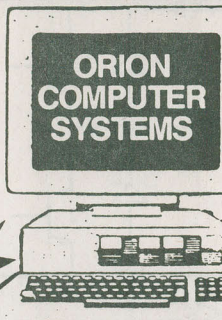

## ORION SYSTEM 286

6/10/12.5 MHZ MB, 512K MEMORY  
1.2MB DISK DRIVE, 16 BIT DISK CONTROLL  
MONOCHROME OR COLOUR VIDEO ADAPTER,  
SERIAL, PARALLEL, GAME, CLOCK PORT,  
200W POWER SUPPLY, AT KEYBOARD.

\$1295

## ORION PORTABLE SYSTEMS

	9" AMBER DUAL CRT	1295 00	1895 00	2995 00
LCD 600x400 SCRN		1645 00	2245 00	3345 00
PLASMA 600x400 S		2395 00	2995 00	4095 00

CALL FOR THE LOWEST CUSTOM QUOTES

386  
1MEG

## HARDWARE, SOFTWARE &amp; PERIPHERALS AT DISCOUNT PRICES

## SEAGATE HARD DISK SYSTEM

20MB (DRIVE CONTROLLER/CABLE) ..... 399.95  
30MB (DRIVE CONTROLLER/CABLE) ..... 429.95  
WE CARRY THE MOST EXTENSIVE LINE OF  
REG. OR HIGH DENSITY DRIVES & CONTROLLERS.  
(CALL FOR A COMPLETE PRICE LIST!)

## FLOPPY DISK DRIVES

PANASONIC OR EPSON (YOUR CHOICE)  
5 1/4" 360K DSD ..... 119.95  
5 1/4" 1.2M HIGH DENSITY ..... 139.95  
3 1/2" 720K DSD ..... 129.95  
3 1/2" 1.44M HIGH DENSITY ..... 145.95  
HARDWARE & MOUNTING BRACKET  
-FROM 3 1/2" - 5 1/4" ..... 9.95

## HARD &amp; FLOPPY DISK CONTROLLER

XT FLOPPY CONTROLLER ..... 39.95  
XT HIGH DENSITY CONTROLLER ..... 74.95  
XT HARD DRIVE CONTROLLER ..... 85.95  
XT RLL HARD DISK CONTROLLER ..... 99.95  
AT HARD DISK/FLOPPY CONTROLLER ..... 189.95  
AT RLL HARD DISK CONTROLLER ..... 299.95  
AT HARD DISK CONTROLLER ..... 169.95  
80M TAPE BACKUP SYSTEM FROM ..... 895.00

## MODEMS / FAX

1200 HAYES COMP. INTERNAL ..... 99.95  
1200 HAYES COMP. EXTERNAL ..... 129.95  
2400 HAYES COMP. INTERNAL ..... 189.95  
2400 HAYES COMP. EXTERNAL ..... 199.95  
FAX CARD 4800 WITH SOFTWARE ..... 649.00  
FAX CARD 9600 WITH SOFTWARE ..... 995.00  
PANAFAX UP-150 WITH PHONE ..... 1895.00  
PANAFAX UP-250 WITH PHONE ..... 2595.00

## SCANNERS

HANDY SCANNER 2.5" ..... 299.95  
HANDY SCANNER 4" ..... 399.95  
LOGITECH SCANNER 4" ..... 299.95  
CAT IMAGE SCANNER (FOR PRINTER) ..... 895.95  
CHINON DESK SCANNER ..... 1295.00  
SHAPE DESK TOP ..... 1295.00

## MICE

LOGITECH SERIAL ..... 99.95  
LOGITECH BUS ..... 119.95  
LOGITECH HIRES ..... 149.95  
LOGITECH 2 BUTTON ..... 69.95  
MOUSE PAD ..... 7.95  
IBM COMPATIBLE LOGITECH FIRM ..... 29.95  
JAVIS CANADIAN MADE ..... 64.95

## DIGITIZERS

KEMAN CT 1770 1000 LINE/INCH ..... 495.00  
TITAN KT2000 400 LINE/INCH ..... 550.00  
TITAN KT3000 1000 LINE/INCH ..... 595.00

## POWER SUPPLIES

150W ULCSA ..... 99.95  
200W ULCSA ..... 139.95  
200W ULCSA FOR TOWER CASE ..... 189.95  
AT STYLE CASE FLIP UP FOR -  
-XT OR BABY AT MOTHER BOARD ..... 69.95  
AT FULL SIZE CASE WITH HARDWARE ..... 109.95  
AT TOWER CASE ..... 225.95

## PORTABLE FOR AT OR XT WITH POWER SUPPLY -

- 9" DUAL AMBER MONITOR, KEYBOARD ..... 895.00  
LCD PORTABLE WITH POWER SUPPLY KEYBOARD ..... 1150.00  
SAME AS ABOVE BUT PLASMA DISPLAY ..... 1795.00

## KEYBOARDS

XT/AT 5000 STANDARD 84 KEY KEYBOARD ..... 69.95  
XT/AT ENHANCED 101 KEY KEYBOARD ..... 89.95

## IBM COMPATIBLE BOARD

MOTHER BOARD  
4.7/10MEG XT OK ..... 129.95  
6/8/12 MEG AT 286 OK ..... 395.00  
10/12 MEG. AT 286 4MEG EMS OK ..... 475.00  
16/20 286 "NEAT" ..... 895.00  
16/20 386 4MEG EMS OK ..... 1250.00

## VIDEO ADAPTER

MGA HERCULES COMP. W/ PRINTER PORT ..... 89.95  
CGA COLOR GRAPHIC VIDEO ADAPTER ..... 59.95  
EGA 640x350 256K ..... 199.95  
SUPER EGA 640x480 256K ..... 299.00  
EGA 800x800 ..... 395.00  
ATI GRAPHIC SOLUTION ..... 199.00  
ATI WONDER CARD ..... 359.00  
57 MGA/CGA AUTO SWITCH ..... 149.00  
ATI VIP MGA/CGA/EGA/VGA ..... 459.00

## I/O CARDS

XT PARALLEL PRINTER PORT ..... 29.95  
XT RS232 SERIAL PORT ..... 34.95  
XT I/O + 2 (S/PIC/G) ..... 79.95  
XT MULTI I/O (S/PIC/G/DISK CONTR) ..... 89.95  
XT GAME PORT (TWO PORT) ..... 29.95  
AT GAME PORT (TWO PORT) ..... 49.95  
TIME CARD WITH BATTERY BACK UP ..... 49.95  
AT I/O SERIAL/PARALLEL ..... 69.95  
AT I/O SERIAL/PARALLEL/GAME ..... 79.95

## MEMORY CARDS

XT 576 RAM CARD OK ..... 54.95  
XT 2 MEG EMS 3.1 32.4 OK ..... 129.00  
AT 2 MEG EMS OK ..... 149.00  
2.5 MEG EXPANSION CARD ..... 109.00

## APPLE COMPATIBLE COMPUTER

BOARDS  
III LASER 128EX II + IIe/IIc COMP. ..... 649.00  
LASER DISK DRIVE "C" COMPATIBLE ..... 199.95  
LASER DISK DRIVE II+ COMPATIBLE ..... 199.95  
80 COLUMN CARD AUTO SWITCH ..... 99.95  
280 CARD FOR CPM ..... 69.95  
SERIAL PRINTER CARD MODEM/PRINTER ..... 99.95  
NICE PARALLEL PRINTER CARD ..... 99.95  
16K RAM (LANGUAGE CARD) ..... 69.95  
SPEECH CARD ..... 75.00  
COLOR MODULATOR KIT ..... 19.95  
POWER SUPPLY ..... 119.95  
DISK CONTROLLER CARD ..... 69.95

## SPECIALTY INDUSTRIAL BOARDS

## FOR IBM COMPUTERS

SA-1208D ANALOG INPUT ..... 495.00  
SI-1203 ANALOG OUTPUT BOARD ..... 535.00  
SC-1602 A/D-D/A CARD ..... 495.00  
SI-3232 INDUSTRIAL CONTROL MODULE ..... 549.95  
SI-7210C IEEE 488 CARD (GPIB) ..... 349.95  
SI-8255 8255 I/O CARD ..... 149.95  
SI-8255 RS-422 CARD ACTIVE PORT ..... 119.95  
SI-5124 FROM WRITER FOR 4EPROM ..... 299.95

WE CARRY A LARGE SELECTION OF EMPROM WRITER,  
UNIVERSAL  
PROM PROGRAMMER (CALL FOR INFO.)

AB SWITCH BOXES SERIAL/PARALLEL, AUTO - OR  
MANUAL, WITH/ WITHOUT BUFFER FROM ..... 39.95  
GENDER CHANGER DB9/15/25 F/F/ M/M, CONVERTERS,  
BOOSTERS, MINISTESTERS.

## LOCAL AREA NETWORK SYSTEM

UPS 110/210 ARCNET LANCARD ..... 229.00  
UPS 1000 ETHERNET LANCARD ..... 349.00  
UPS 400 4PORT ACTIVE HUB CARD ..... 229.00  
UPS 404 4PORT PASSIVE HUB CARD ..... 59.95  
UPS 808 8PORT ACTIVE HUB CARD ..... 495.00  
CALL FOR FULL INFORMATION.

## HIRES MONITORS

GOLDSTAR  
4215 RGB ..... 399.95  
4095 EGA ..... 499.95  
1430 VGA ..... 599.95  
2115 12" AMBER SWIVEL BASE ..... 139.95  
2025 12" AMBER COMPOSITE ..... 129.95  
PACKARD BELL AMBER SWIVEL BASE ..... 129.95  
TTX MONITORS  
1201A ..... 12" COMP. AMBER MONOCHR. .... 129.95  
1400F/A ..... 14" TTL AMBER FLAT SCREEN ..... 179.95  
1452FW/14" ..... VGA AN.WHT FL. SCREEN ..... 199.95  
2410 ..... 14" RGB 43mm POL. TILT/SW ..... 399.00  
2410AG ..... 14" RGB 43mm A.G.L. TILT/SW ..... 445.00  
2411 ..... 14" RGB 38mm POL. TILT/SW ..... 475.00  
2411AG ..... 14" RGB 38mm A.G.L. TILT/SW ..... 499.00  
2422 ..... 14" EGA 31mm A.G.L. TILT/SW ..... 575.00  
1435 ..... 14" MULTI SYNC ..... 599.00  
1310 ..... 14" ELECTROHOME M. SYNC ..... 850.00  
1910 ..... 19" ELECTROHOME M. SYNC ..... 3250.00

## DATATRAIN MONITORS: COLOUR

DC2005 ..... 14" 41mm DOT P. RGB T/S ..... 449.95  
DC2055 ..... 14" 52mm DOT P. RGB T/S ..... 349.95  
DC3535 ..... 14" 31mm D.P. EGA/CGA/T/S ..... 549.95  
DC355 ..... DOT PITCH 41mm EGA/CGA ..... 479.95  
DC355 ..... DOT PITCH 41mm VGA ..... 499.00  
DC800 ..... M.RES VGA/DIG. D.P. 31mm ..... 679.95

## DATATRAIN MONITORS: MONOCHROME

V240A ..... 12" AMBER COMPOSITE ..... 139.95  
V242 ..... 12" TTL AMBER OR GREEN ..... 134.95  
V252 ..... 12" M.RES MONO AMB/GRN ..... 149.95  
V262A ..... 12" FLAT SCREEN TTL AMBER ..... 159.00  
V272 ..... 14" DUAL FREQ. AMBER/WH ..... 189.95  
V282 ..... 14" D. FREQ. FLT SCRN AWH ..... 199.95  
V502 ..... 12" ANLG VGA/MCGA MONO WH. .... 199.95

## PRINTERS

ROLAND PRINTERS  
PR1012 ..... 144CPS DOT MATRIX ..... 249.95  
PR1112 ..... 192CPS DOT MATRIX ..... 299.95  
PR1212A ..... 219CPS DOT MATRIX ..... 475.95  
PR1250 ..... 288CPS DOT MATRIX ..... 549.95  
PR1215 ..... 216CPS WIDE CARRIGE ..... 699.95  
PR1550 ..... 288CPS WIDE CARRIGE ..... 799.95  
PR2450 ..... 240CPS WIDE CARRIGE ..... 999.00  
PR2017 ..... 17CPS DAISY WHEEL ..... 449.95

## EPSON 9 PIN DOT MATRIX PRINTERS

LX-800 ..... 180/150CPS DRAFT/30/25 NLQ ..... 275.00  
LX-800BA ..... 180/150CPS DRAFT/30/25 NLQ ..... 449.00  
EX-1000 ..... 250/45CPS DRAFT/NLQ SL TP ..... 899.00  
EX-800 ..... 250/45CPS DRAFT/NLQ SL TP ..... 899.00  
FX-1050 ..... 264/50CPS D/NLQ 132CLM ..... 950.00  
FX-286 ..... 200/40CPS D/NLQ 132CLM ..... 799.00  
FX-850 ..... 285/54CPS D/NLQ SMARTPARK ..... 650.00  
FX-86E ..... 200/40CPS D/NLQ 80 CLM ..... 549.00  
24-PIN LETTER QUALITY DOT MATRIX PRINTERS  
LQ-1050 ..... 264/220/88/73CPS ..... 1095.00  
LQ-2500 ..... 270/80CPS DRAFT/NLQ ..... 1499.00  
LQ-500 ..... 180/80CPS DRAFT/NLQ ESC/P ..... 575.00  
LQ-850 ..... 264/220/88/73CPS ..... 895.00  
DX-10 ..... EPSON 10CPS DAISY WHEEL ..... 349.00  
SQ-2500 ..... 540/180CPS DRAFT/NLQ ..... 1495.00  
24 NOZZLE INKJET 132 C/LP ..... 1495.00

## STAR PRINTERS

NX-100 ..... 144CPS 7C/LCOLOUR ..... 289.00  
NX-1000C ..... 144CPS 7C/LCOLOUR ..... 399.00  
NX-1000 ..... 144CPS 7C/LCOLOUR ..... 399.00  
NX-15 ..... 120CPS ..... 549.00  
NR-10 ..... 240CPS ..... 599.00  
NR-15 ..... 270CPS ..... 799.00  
NX-2400 ..... 170CPS ..... 549.00  
NB24-10 ..... 216CPS ..... 775.00  
NF74-15 ..... 216CPS ..... 995.00  
LASER PRINTER ..... 2995.00

## ORION DISKETTES

100% ERROR FREE &amp; LIFETIME WARRANTY

## ORION BRAND 5 1/4" DISKETTES

002D ..... 360K DS/DD ..... 8.95  
002HD ..... 1.2M DS/HD ..... 17.50  
FOR COLOUR ADD ..... 3.00

## ORION BRAND 3 1/2" DISKETTES

0F2D ..... 1M DS/DD ..... 19.95  
0F2HD ..... 2M DS/HD ..... 49.95  
FOR COLOUR ADD ..... 4.00

## NO NAME DISKETTES

5 1/4" DS/DD 360K ..... 4.99  
FOR COLOUR ADD ..... 3.00  
3 1/2" 1M ..... 14.99  
FOR COLOUR ADD ..... 4.00

FOR QUANTITY DISCOUNTS CALL

KAO

KAO is for keeps

KAO MD20 5 1/4" 360K DS/DD ..... 9.95  
KAO MD20H 5 1/4" 1.2M DS/HD ..... 19.95  
KAO COLOUR DISKETTES ADD ..... 3.00  
KAO MF2DD 3 1/2" 1M DS/DD ..... 22.50  
KAO MF2HD 3 1/2" 2M DS/HD ..... 49.95  
KAO COLOUR DISKETTES ADD ..... 3.00  
KAO DISCAROO 3 1/2" IN POUCH ..... 29.95

## ROLAND PLOTTERS

DX-880A ..... B-SIZE 8 PEN ..... 1395.00  
DX-885 ..... B-SIZE AUTO PEN ..... 1695.00  
DX-908A ..... B-SIZE ELECTROSTATIC ..... 1995.00  
DX-990 ..... B-SIZE ES. PAPER HOLD ..... 2195.00  
DPX-2200 ..... C-SIZE FLATBED ..... 5750.00  
DXP-3300 ..... D-SIZE FLATBED ..... 6995.00  
DX-1100 ..... A/B SIZE 8 PEN ..... 1349.00  
DX-1200 ..... A/B SIZE ELECTROSTATIC ..... 1749.00  
DX-1300 ..... A/B SIZE 1M BUFF STD ..... 2295.00  
GRX-300 ..... D-SIZE ROLLERBED ..... 5995.00  
GRX-400 ..... E-SIZE ROLLERBED ..... 7995.00

## ROLAND PLOTTER PENS

VATER BASE ..... 417.50  
NL BASE ..... 419.50  
JERICAM BASE ..... 439.95  
MAGNETIC PLOTTER PENS FIBERTIP ..... 419.95  
ROLLER BALL ..... 417.50  
PLOTTER PAPER ALL  
UNINTERRUPTIBLE POWER SUPPLIES  
UPS-250 SUNDON ..... 499.00  
UPS-400 SUNDON ..... 599.00  
73-800 SUNDON ..... 1299.00  
POWER BAR WITH SURGE PROTECTOR ..... 17.50  
OD-100L HOLDS 100pc 5 1/4" WITH LOCK ..... 12.50  
OD-140L HOLDS 140pc 5 1/4" WITH LOCK ..... 14.95  
OD-80L HOLDS 80pc 3 1/2" WITH LOCK ..... 14.95

WE CARRY ONE OF THE LARGEST SELECTION OF  
RIBBONS FOR ALL TYPES OF PRINTERS, SOFTWARE  
FOR IBM, APPI E, COMMODORE, ATARI ETC.  
BOOKS FROM MCCOY PUBLISHERS. CALL FOR A FREE  
FLYER & PRICING. COMPUTER CABLES FOR PRINTERS,  
MODEM, DISK D. VES. CUSTOM MADE CABLES.  
CONNECTORS: DB SERIES, HEADERS, EDGE CARD,  
SEMICONDUCTORS, RAM, ROM, EPROM, TTL, CMOS,  
TUBES, CAPACITORS, RESISTORS, FUSES, CRYSTALS,  
TRANSISTORS, LAMPS, SWITCHES ETC. TEST  
INSTRUMENT, SCOPE, MULTI TESTERS, LOGIC PROBES  
ETC. ELECTRONIC KITS, EDUCATION / HOBBYIST.  
MOVING SIGN ANY SIZE.

CALL US FOR YOUR ELECTRONIC NEEDS!

MOST ORDERS SHIPPED  
WITHIN 24 HOURS.

SERVING YOU FOR OVER 15 YEARS

If you find a better price  
call us before you buy.

## TERMS

VISA/MC/COD/CHECK  
ALL ITEMS SHIPPED BY CANPAR OR UPS. ADD \$4.00  
FOR ALL COD ORDERS. ALLOW 10 BUSINESS DAYS  
FOR SHIPPING WHEN PAYING BY PERSONAL CHECK  
ALL ITEMS SUBJECT TO PRIOR SALE DELIVERY &  
HANDLING CHARGE 5%. MIN. \$5.00 ALL RETURNED  
MERCHANDISE MUST HAVE RNA NUMBER  
RESTOCKING CHARGE 20%. PRICE SUBJECT TO  
CHANGE WITHOUT ANY NOTICE

Credit card charges  
are not submitted  
until time of  
shipment



WHY WAIT? CALL ORION ELECTRONICS NOW!

ORDER TOLL FREE!

1-800-265-2658

40 LANCASTER ST., W., KITCHENER, ONT. N2H 4S9

PH: (519) 576-9902 FAX: (519) 576-9028

DEALER INQUIRIES INVITED

Order desk & technical support open:  
9:00 a.m. to 6:00 p.m. Monday-Friday  
9:00 a.m. to 5:00 p.m. Saturday

For Service  
CALL

1-519-576-9026

Immediate shipment on purchase  
orders from qualified institutions  
(schools and universities included).



# EXECUTIVE SOFTWARE SERIES

SOFTWARE FOR PC, XT AND AT COMPATIBLE COMPUTERS  
FROM THE CREATORS OF ALMOST FREE SOFTWARE

NEW

## V O L U M E T W O

The response to our first Executive Series Software disk has been so overwhelming that we would have created another one even if every disk drive in the place had died all on the same day. We hope you'll agree that this one is every bit as interesting as the last, crammed to the write protect notch with helpful programs to make your computer more powerful, easier to use and simply more productive.

Included in this collection are several file management programs, a disk formatter which actually makes your disks bigger, a virus check program that really protects your PC from infection and a double helping of other powerful slabs of code.

There are several programs on this disk which no serious user should even consider being without.

There are commercial programs which do some of the things that this collection does. They cost hundreds of dollars. This one costs just twenty bucks. If it saves you ten minutes the next time you're really in a panic it'll have been worth that and then some.

As always, if you order this disk and don't feel it's fair value after you've tried it out, we'll buy it back from you for every cent you paid for it... something else that commercial software doesn't offer you. Finally, if you have any questions you'll find our help desk is always just a phone call away.

**BCOPY** is a handy little replacement for the DOS COPY command which copies files as a background task. As soon as you let it go, it returns you to the DOS prompt so you can get back to whatever you were doing.

**BELL** makes the beep in your PC sound like an electronic phone. Not likely to affect the bottom line, this, but it's very small and kind of fun.

**NJFRERAM** will tell you how much free memory is left in your machine from minute to minute, even when you're inside an application. This is a great asset to spreadsheet users.

**CASE** will convert text into all lower case, all upper case, capitalized words and it'll even clean up WordStar files.

**MAXI** is a disk formatting program which will allow you to get four hundred kilobytes on a regular 360K disk, or almost a megabyte and a half on a quad density disk. Speeds up your hard drive backing up considerably.

**POPCALC** is a handy four

finger calculator which pops up in a window whenever you need it.

**TONTO** is a sort of SideKick clone which provides a number of useful functions in a window when you call it forth.

**VFILER** is a simple file manager which will help you move, copy, rename and delete lots of files without lots of typing.

**WHEREIS** locates files on your hard drive... no matter where they're lurking.

**MCOPY** is a DOS COPY replacement with lots of features. It will copy files over multiple floppies if you have too many files to copy onto one, prompting you to swap disks. It uses a sophisticated algorithm to make sure you use your floppy space as efficiently as possible. It's a civilized replacement for BACKUP and RESTORE in this case. It also does CRC checks of each file to make sure your important data isn't corrupted.

**ADDRESS** is a resident envelope addresser which works with most popular word processors. It allows you to roll an en-

velope into your printer, hit a key and have the envelope addressed automatically, copying the address from the screen of your PC. In addition, it will also print a text or specially designed graphic return address on every envelope if you like.

**VCHECK** protects your system against those computer viruses you've read so much about. It checks sensitive files in your computer to make sure they haven't been infested.

**SETALARM** is a simple memory resident reminder that will beep at you at a pre-arranged time.

**SILENCE** kills the speaker in your PC when you don't want to be beeped at.

**VTREE2** is an enhanced version of the VTREE program on our last disk... there's always one more version. It maps out the tree structure of your hard drive and tells you how much space each directory occupies.

**WORLDTIME** will tell you the correct time in any city in the world.

## EXECUTIVE SOFTWARE DISK OF THE MONTH CLUB

New Executive Software Series disks will be appearing roughly once a month. If your day is too full to allow you the time to order these disks, we offer you our disk of the month club service. Join the club, provide us with a credit card number and we'll automatically ship you each new disk, billing your account. If you don't want to keep a disk, simply return it and we'll credit your card account. This service places you under no obligation... you can cancel it whenever you no longer need it. All club members will receive disks at the rate of \$19.95, or \$29.95 for two disk sets, for twelve calendar months, regardless of any price increases which may occur within this period.

To get on line with the Executive Software Series disk club, contact us by letter, phone, or FAX, or simply use the coupon below.

☐ Charge my Credit Card  
☐ Visa ☐ MasterCard ☐ AmEx

Account# \_\_\_\_\_

Expiry Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Prov. \_\_\_\_\_ Postal Code \_\_\_\_\_

Signature \_\_\_\_\_

MOORSHEAD PUBLICATIONS

1300 Don Mills Road, North York,

Ontario M3B 3M8

(416)445-5600 FAX: 416-445-8149

FINE PRINT: This software has been collected from public access bulletin boards and/or has been placed directly in the public domain by its authors. It is all believed to be in the public domain, or offered as "shareware". As shareware, users of these programs are requested to pay registration fees to their authors, which may entitle you to additional updates, support and documentation. Note that the fee charged for this disk defers our cost in collecting and distributing the software only, it does not replace any requested shareware contributions. This will help to ensure a continuing supply of high quality shareware available at reasonable prices. If you try out this disk, and do not feel that it is fair value, you may return it for a refund or exchange it for a different disk with no questions asked. We do not sell software to people who cannot use it. If you have trouble with disk, you are welcome to call our free technical support service at (416) 445-5600 during normal business hours. Please be prepared to tell us the exact make and model of your computer and the disk and program you are having difficulty with. Please note that we cannot be responsible for any loss, damage or expense resulting from your use of this software, however caused. If you are unable to read your disk, it has probably been corrupted in the mail. You need not call us in this case. Simply return the disk to our software department with a note requesting a replacement. It will be shipped immediately. Please note that this disk does presuppose a reasonable familiarity with your computer. If you are very new to your system, we strongly recommend that you familiarize yourself with it before attempting to use almost free software.

THIS DISK IS ONLY \$19.95 (PLUS 8% O.S.T. & \$1.50 SHIPPING) FROM MOORSHEAD PUBLICATIONS  
1300 DON MILLS ROAD, TORONTO, ONTARIO M3B 3M8 PHONE: (416)445-5600 FAX: 416-445-8149  
PLEASE SPECIFY 5 1/4 INCH DISKETTES OR 3 1/2 INCH MICROFLOPPIES



# Zero Crossing Power Controller

Control AC power and eliminate RFI with integral cycles


ANDY FLIND

The idea for this project arose when a new soldering iron was purchased for the author's workshop. The old iron was a 15 watt model, perfectly adequate for light electronic work, but sadly unequal to the occasional heavier task. It was decided that the replacement should be a 25 watt iron, especially as a very popular version just happened to be on "special offer" at the time.

The extra power is sometimes useful, but for lighter day-to-day work it soon proved to be an embarrassment. The bit (an iron-coated type) continually oxidized and refused to tin properly; eventually it turned blue and started to warp. Joints made with it took ages to solidify and displayed the typical appearance of overheating. In short, something had to be done.
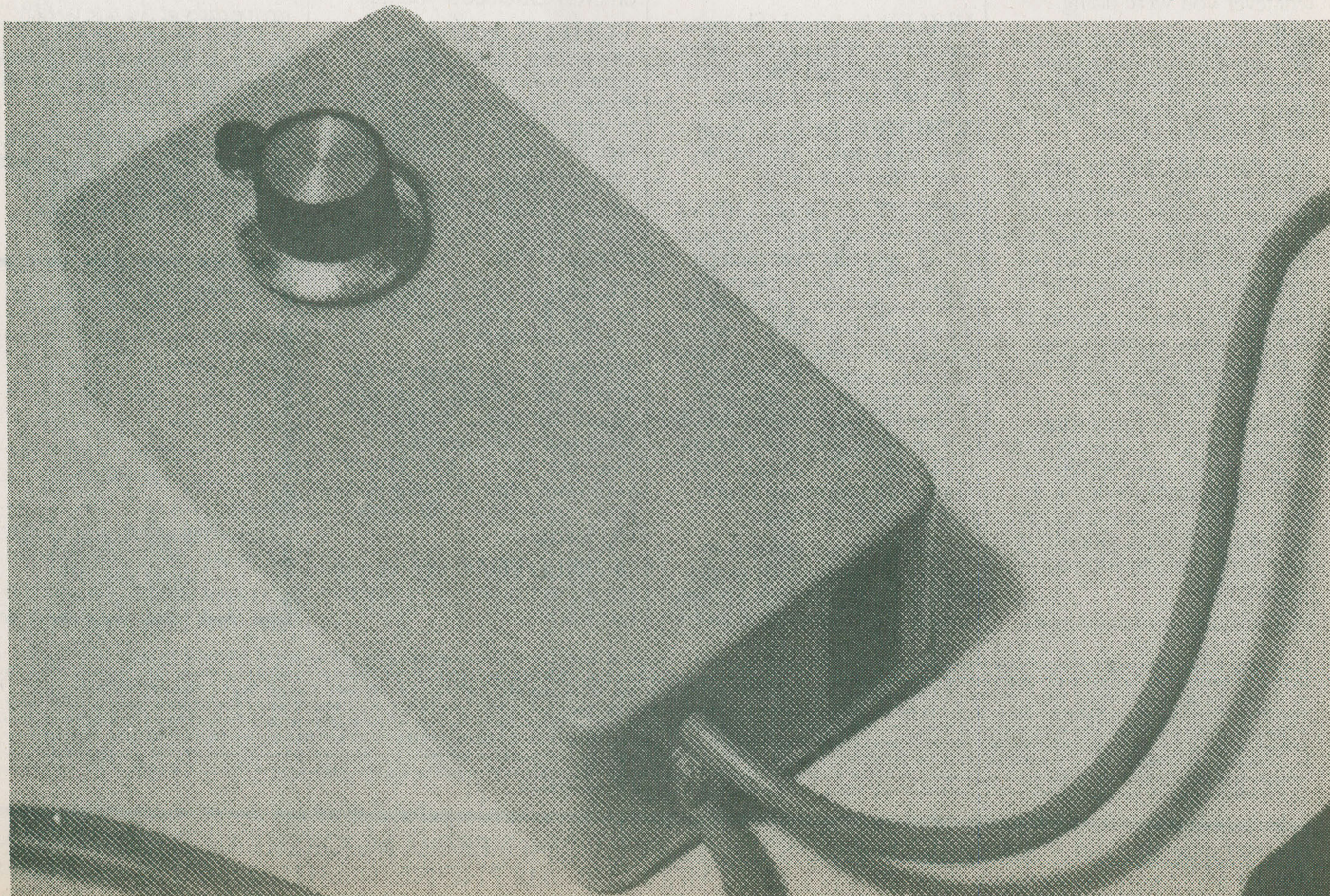
## Burst Fire

The usual method of controlling light loads is by variable phase control, as used in lamp dimmers. Even when well suppressed, though, these create a lot of radio frequency interference at close range, especially unwelcome where sensitive electronic equipment is being tested. As a soldering iron has a fair degree of thermal






inertia, some form of "burst fire" controller seemed the best solution, as these are inherently interference-free.

Since the mains supply alternates between positive and negative peak voltages at 60 hertz, it follows that it must pass through zero 120 times a second. If the load can be switched on and off at, or very close to, these zero points, the switching device will not make or break any heavy currents, so the interference generated will in consequence be negligible. Integral-cycle controllers using this method switch loads on and off at regular intervals, the switching taking place at zero crossings. The net power delivered depends on the ratio between the "on" and "off" times.

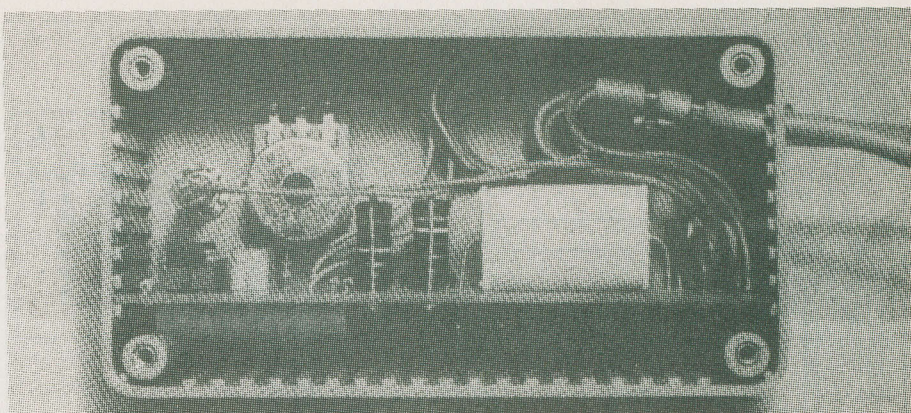Switching "off" at the right moment is easy. If the drive is removed from a triac gate it will continue to conduct until the current passing through it falls to a low level, which of course coincides with the low voltage point (for a resistive load). Thus the correct "off" point is selected automatically. Switching on is slightly more difficult; the right point has to be



sensed in some way and drive applied to the triac at that exact moment.

Custom chips are available for the job, but are not really suited to light loads. The reason for this is that they usually fire the triac with a very short pulse to the gate, then rely on the "on" condition being maintained by the load current. With a small load such as a 25W iron, this is likely to be insufficient at the point where the gate pulse ends; for such applications a

## PARTS LIST

### Resistors

All 0.5W types except R1 and R2

R1	.....180 1 watt
R2	.....100k 1 watt
R3,5	.....10k
R4	.....1M
R6	.....1k

### Potentiometer

VR1 470k lin. carbon with nylon or plastic spindle

### Capacitors

C1	.....0.47u 250V
C2	.....470u 25V electro.
C3	.....1u polyester layer

### Semiconductors

IC1 CMOS 4013B type D flip-flop

TR1	.....2N3904 or equiv.
D1, D2, D4, .....	1N4003 or equiv.
D3	.....12 volt 1W Zener
D5, D6	.....1N4148 or 1N914
CSR1	.....C206D triac

### Miscellaneous

VDR1 mains transient suppressor such as Int. Rectifier Z21L271 or Active Components #10441; PCB; box, 120 x 65 x 40mm; plastic control knob; 120VAC neon indicator (with integral resistor); 8-pin DIP socket; connecting wire, etc.

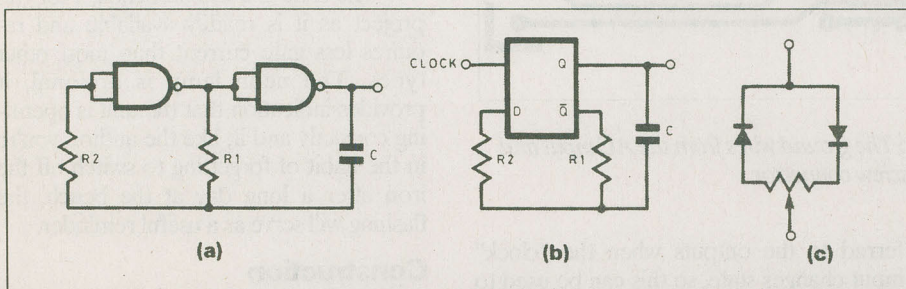


Fig. 1a. CMOS NAND gate oscillator. Fig. 1b Oscillator built with a "D" type flip-flop. Fig. 1c. Substitute for R1 to obtain variable mark to space output.

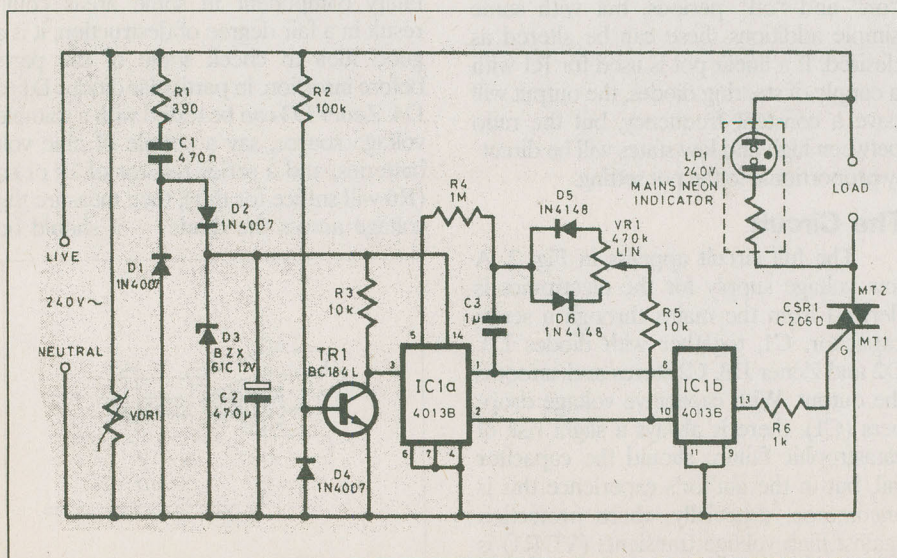


Fig 2. Complete circuit of the power controller.



# Zero Crossing Power Controller

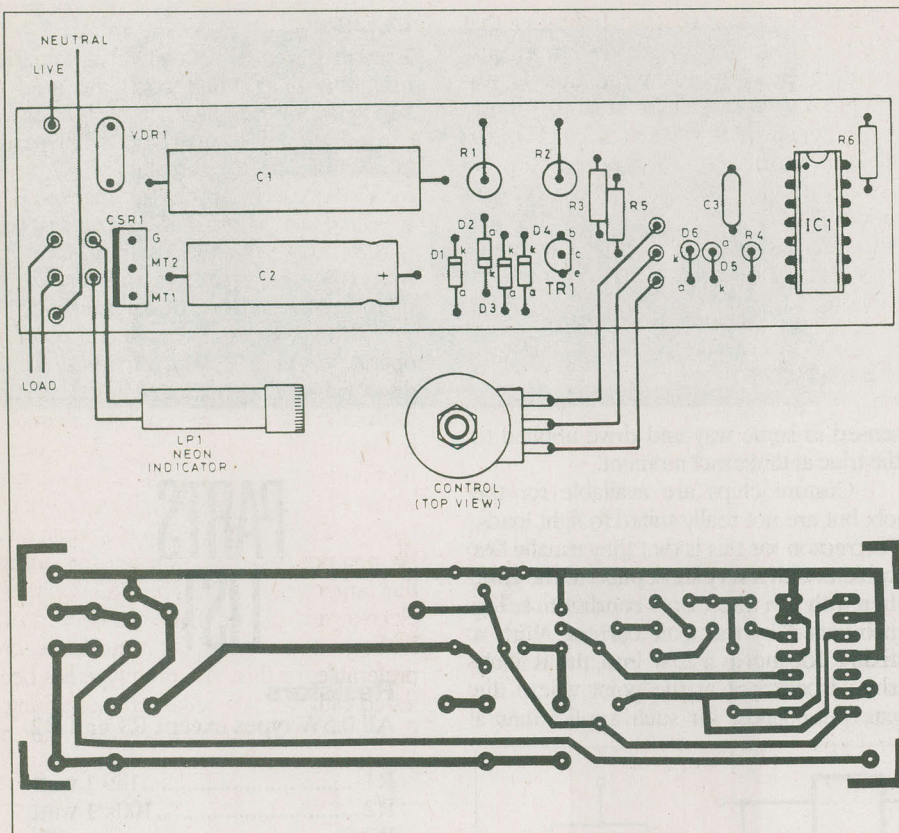


Fig. 3. Layout, wiring and PCB for the controller. The ground wires from the AC input and to the load should be connected together with a screw connector.

continuous gate drive is better. Fortunately it is possible to construct an extremely simple circuit around a "D" type flip-flop which will not only generate the required variable mark-space timing function, but can be synchronized to the zero crossings through its clock input.

A common oscillator circuit that can be built with the two inverting logic gates is shown in Fig. 1a. Positive feedback is applied right around the circuit via capacitor C and R2, ensuring clean and positive switching. However, after each switching action, negative feedback from R1 gradually pulls the input towards the opposite polarity until another change of state takes place. R2, by the way, prevents the gate's input protection from loading the timing circuit.

In Fig. 1b the same circuit is shown built, with a "D" type flip-flop. With this type of device, the "Q" output will assume the state present on the "D" input, whilst the "Q" output will take up the opposite state. We thus have an input and two opposing outputs, so an oscillator circuit can be constructed exactly as before. However, changes of input are only trans-

ferred to the outputs when the "clock" input changes state, so this can be used to synchronize output changes to another input signal.

As shown, the output will have equal "on" and "off" periods, but with some simple additions these can be altered as desired. If a linear pot is used for R1 with a couple of steering diodes, the output will have a constant frequency, but the ratio between high and low states will be directly proportional to the pot setting.

## The Circuit

The full circuit appears in Fig. 2. A low voltage supply for the electronics is derived from the mains through a series capacitor, C1, together with diodes D1, D2 and Zener D3. C2 stores and smooths the output. With capacitive voltage droppers (C1), there is always a slight risk of catastrophic failure should the capacitor fail, but in the author's experience this is uncommon, especially where protection against high voltage transients (VDR1) is provided. Capacitors are much cheaper and easier to mount on PCBs than trans-

formers. To generate the clock signal, current flowing through R2 is passed through the transistor's base-emitter junction during positive half-cycles, turning it on. During the negative periods it flows through D4, and the transistor turns off. A logic signal synchronized to the mains can thus be taken from its collector. The IC used, a CMOS 4013B, actually contains two "D" type flip-flops. The first of these is used as described, the output switching at about 1Hz, with the on-off ratio being adjustable through VR1.

The flip-flops in the 4013 are also provided with "set" and "reset" inputs, which can be used to drive the outputs directly regardless of the "D" and the "clock" inputs. In the first stage these are not used so they are connected to ground. The second flip-flop is used simply as a follower to buffer the output before it drives the triac. Its "set" and "reset" inputs are driven from the "Q" and "Q" outputs of the first stage, and the unused "D" and "clock" inputs are grounded.

The triac is a C206D, chosen for this project as it is readily available and requires less gate current than most other types. The neon lamp is optional; it provides indication that the unit is operating correctly and if, like the author, you're in the habit of forgetting to switch off the iron after a long day at the bench, the flashing will serve as a useful reminder.

## Construction

Construction of this project is quite straightforward, so little needs to be said about it. Since live testing is difficult and a faulty component in some areas could result in a fair degree of destruction, it is a good idea to check some of the parts before insertion, in particular diodes D1 to D4. Zener D3 can be tested with a suitable voltage source, say a couple of nine volt batteries, and a series resistor of 1k or so (R6 will suffice for this), then measure the voltage across the diode — it should be

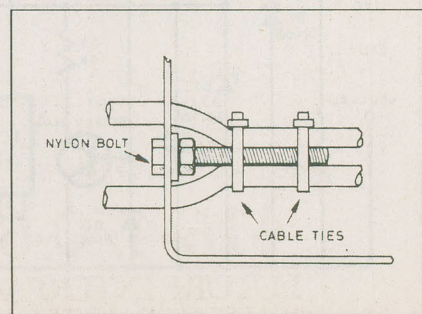


Fig. 4. Method of securing the AC power leads.



12V. Fig. 3 shows the positions of all the components; take care to ensure that the diodes are fitted the correct way round.

### Testing

Testing, of course, must be carried out with due regard for the fact that all of the circuit will be connected directly to the mains and MUST therefore be treated as "live". It is suggested that a socket is used for IC1, and initially the unit should be plugged in without this IC. It is a good idea to connect the meter probes to the points indicated before plugging in, to eliminate the risk of making contact with live parts. Begin with the meter connected across the 47u capacitor C2, set to a range covering up to 250 volts DC. This will protect your meter if a fault is present.

Plug in, and if there is scarcely any reading, reduce the meter range until you can see the voltage on C2, which should be around 11.5 to 12 volts. If this seems correct, unplug and reconnect the meter between negative and the bottom end of R3 (collector of TR1), which should read around five volts when plugged in again.

This is an average reading, indicating that TR1 is switching properly. Ignore any reading present when the unit is unplugged, which will be due to charge stored in C2. If all appears well, it remains only to insert IC1 and plug in again; the neon indicator should begin to flash at about 1Hz, and adjustment of VR1 should vary the flashes from so brief they're just visible to so long they're very nearly continuous.

### Final Assembly

The layout of the unit in its case is shown in Fig. 4. the "cord-grip" arrangement is a little unusual; since the unit is rather compact, there isn't space for most of the available types of cable clamp. The solution is to place a nylon screw between the two cable entry holes and tie the cables firmly to it with a couple of nylon cable-ties. This provides a compact, cheap and effective fixing for both leads. No metal parts should be exposed on the outside of the case. A potentiometer with a nylon shaft and a plastic knob must be used.


### In Use

Though designed to control a soldering iron, this simple unit could be used or adopted for a host of other applications. It can be employed anywhere a low-power interference-free controller is required, for instance with an electric blanket. The specified triac is rated at three amps, permitting safe use with loads up to about 250 watts (though a small heatsink may be required above a couple of hundred watts).

Alternatively it could be used to operate flashing displays of various kinds, disco lights, Christmas tree lights, and so forth. The flash rate can easily be altered or made variable just by changing the pot connections and the value of C3. Two pots would allow independent adjustment of the "on" and "off" periods. C3 of course must be non-polarized: in practice this means that larger values should be made from two electrolytics placed back-to-back. Low-leakage types such as tantalums are preferable for this. The prototype has been tested with two 10u tantalum beads giving a flash rate of around five seconds, with no problems at all. ■

## FUTURE INTERFACE INC.

### YOUR HARD DRIVE REPAIR SPECIALISTS

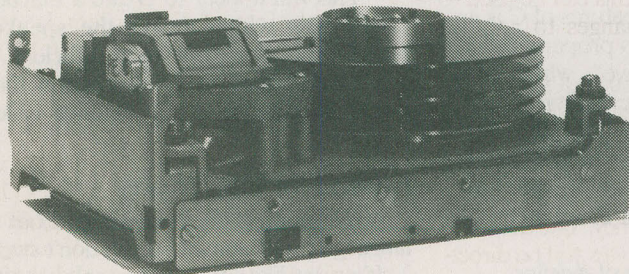


CMI FUJI SEAGATE TANDON MAXTOR  
QUANTUM SHUGART MINISCRIBE C.D.C.  
I.M.I. NEC RODIME PRIAM OLIVETTI  
MICROSCIENCE

- Class 100 Clean Room • Servo and Wedge Writing Capabilities • 5 to 10 Day Turnaround • Full 24 Hour Burn-in on all Repaired Drives • 180 Day Warranty on all Work • Competitive Pricing • In-House Servo-Writing on Seagate 4000 Series • Free Estimates Available
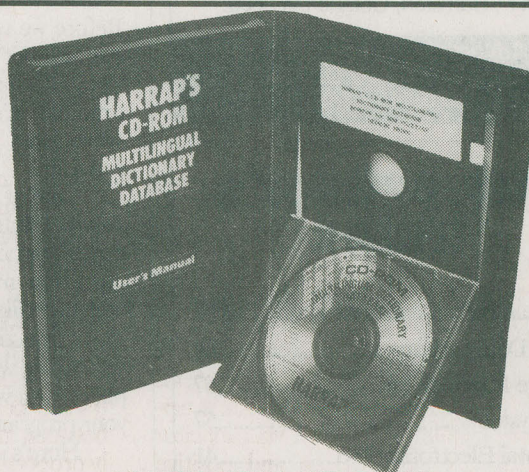
# 416-470-6280

FUTURE INTERFACE INC.  
401 ALDEN RD., UNIT 8, MARKHAM,  
ONTARIO L3R 4N4



## HARRAP'S CD-ROM MULTILINGUAL DICTIONARY

At the touch of a key, Harrap's CD-ROM Multilingual Dictionary Database gives instant access to 5 million words in 8 languages: English, French, German, Spanish, Italian, Dutch, Japanese and Chinese. For this project, publishing companies from seven countries have contributed 13 highly reliable and renowned dictionaries. The total amount of stored data is almost 500 megabytes, including address information used for quick retrieval. This corresponds to an amazing 500 million characters. Works with most popular word processing programs.

### INLY SYSTEMS INTERNATIONAL LTD.

1090 Cummings Avenue, Gloucester, Ontario K1J 7S2  
(613) 744-8307 FAX (613) 744-8320



# CLASSIFIEDS

## Where Buyers Find Sellers

ORIGINALTRI-MODE parts \$89.95,  
SB3 Parts \$69.95, Notch Filters \$39.95,  
Catalogues \$1.00, GENIE, Box 522,  
Montreal, PQ, H3S 2V3

Electronic Design/Computer program-  
ming. Call Bob (416) 665-4288.

Modems for PC/XT/AT Halfcard 2400B  
—\$230., 1200B — \$110. 2 year warranty  
with cable software, C.O.D., Plus \$8.00  
S&H, H.E.S. P.O. Box 2752, Station B,  
Kitchener, ON N2H 6N3.

FREEZING SPRAYS 16 oz. \$4.20  
TV Booster made Canada \$65.00 both  
units. Coax RG59 \$84/1.000ft.; Antennas  
from \$39.00, Rotors \$69.00, and more  
37c for catalogue postage  
ANTECO Ltd. POB 3014 Willowdale "D"  
ONT. M2R 3G0.

PRINTED CIRCUIT BOARDS  
for ETI, Radio Electronics, and Ham  
Radio projects. Full list \$1.00,  
refunded with first order.  
B-C-D ELECTRONICS, P.O. Box 6326  
Station F, Hamilton, Ontario L9C 6L9.

For Advertising Information Call:  
(416) 445-5600 Or Fax:  
416-445-8149

## Advertiser's Index

Duncan Instruments of Canada Ltd.	62
EMJ Data Systems .....	64
Future Interface Inc. ....	57
Inly Systems .....	57
Kaientai Electronics Ltd .....	41
KB Electronics Ltd. ....	7
McGraw Hill .....	insert
National Technical Schools .....	5
Orion Electronics .....	52
The Hunter Group.....	6
Toshiba of Canada Ltd. ....	63
Trebas Institute of Recording Arts....	2

### For Advertising Information

Call (416) 445-5600  
Fax: 416-445-8149

## The Techie's Guide to C Continued from page 18

list when it finishes with the current one. This is actually useful sometimes.

You'll probably note that, strictly speaking, there is no *break* needed after the *default* case, as it's the last case in the list, and there's no where for C to fall through to if the *break* had been left off. This is true enough. In this case, C actually ignores the existence of the last *break* when it compiles the program. However, if we were to tack another case onto this *switch* some time in the future, we might forget to go back and add the necessary *break* to the *default* case. As such, it's a good rule to always end cases with *breaks*, whether they're really needed or not, unless there's a good reason to omit them.

The contents of the three cases should be pretty easy to work out. The case for eight, the backspace, prints a backspace, a space and another backspace, so it moves to the previous character, blows it away and then moves back into the now vacant position. The case for nine, the tab, just prints five spaces. You'll recall this use of *printf* from last month. Finally, the case for thirteen, the carriage return, should be pretty obvious.

### Definition of Terms

Before we vanish into the swirling mists of eternity, let's consider a bit of compiler lore. This has nothing to do with the above example; it's just a useful thing to have your head around when you're writing programs.

One of the slickest features of C is its *#define* statement. This is properly called a "pre-processor directive", which is a term that means that the authors of the language liked big words. Like the *#include* directive we saw last month, this is something which happens before the compiler starts worrying about the contents of your program.

Here's a common use of *#define*

```
#define pi 3.1415926

main( )
{
    printf("The value of pi is %f",pi);
}
```

The syntax for the *printf* statement is a little weird; don't sweat it right now. The important point is that the *#define* statement has associated the number 3.1415926 with the label *pi*.

This may seem like just another sort of variable. It's not. What actually happens here is that before it compiles the program

the compiler goes through it and finds every occurrence of the label *pi*. It then mechanically replaces each one with the number 3.1415926. This results in a lot faster code than would have come to pass if we'd used a variable for *pi*.

If you had a program with lots of occurrences of *pi* in it, you would use a *#define* to initially establish what *pi* actually is. You might want to experiment and see what effect changing the precision of *pi*, the number of digits after the decimal point, has on the working of your program. In this case, all you need do is to change the number in the *#define*.

You can assign anything to a label in a *define*. For example,

```
#define name "Wombat Mc-  
Angleiron"
```

tells C that *name* should be replaced with the string *Wombat McAngleiron*. Now, if you attempt to use *name* in your program in some place where a string would not be appropriate, C will most certainly complain.

Finally, you can even use this facility to meddle with function names. For example, if you print character seven to the screen, the speaker on your PC will beep. Thus, we might

```
#define beep( ) putch(7)
```

This will appear to create a function called *beep* which makes the speaker sound. This is slightly more efficient of space and speed in your program than would be creating a real function called *beep*.

### Beam Me Up, Scotty

If you're not exactly illuminated about C language programming as yet, don't sweat it. It's a bit like listening to rock 'n roll... you have to let it wash over you for a while until the lyrics start to make sense. Unfortunately, depending on the rock 'n roll you check out, when they finally do make sense, the lyrics might turn out to be telling you to go eat live sheep. At least C language, when it finally does become clear to you in a flash of blinding insight, won't involve mutilating livestock.

Next month, we'll have a look at some specific PC compatible C language compilers. If you're just itching to be able to actually write some code, you'll want to get the next edition of ET&T to find out what's best to write it in.

Bye... ■



# The Small-fry Mini-Amp

Not too hi and not too fi — but small, hot and not a lot of money.

KEITH BRINDLEY

**W**e certainly can't call this project the ultimate in super-powered, high-fidelity amplifiers, but we can assure you that it's simple to build and it really couldn't be cheaper. A single chip design means that as few as eight components give an amplifier with 46dB of gain from a 9V power source. A single pot controls gain from zero to maximum.

The output power into an 8 ohm loudspeaker with a 9V power supply is up to around half a watt which, although it isn't eardrum-shattering volume, is more than enough for a simple guitar practice amplifier, or a personal stereo extension amp. Power op amps are useful as servo drivers or simple intercoms too.

## Construction

The circuit of the Mini-amp is given in

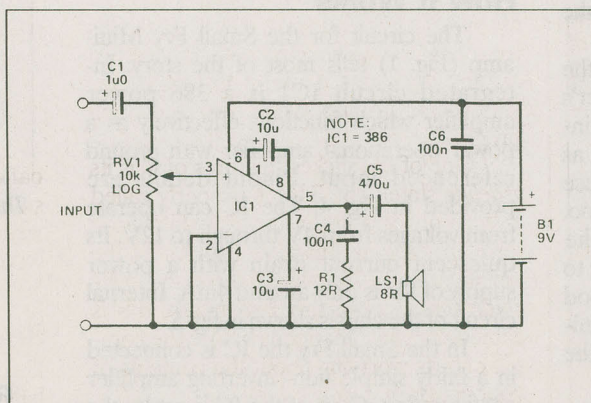


Fig. 1. The circuit diagram of the Mini-amp.

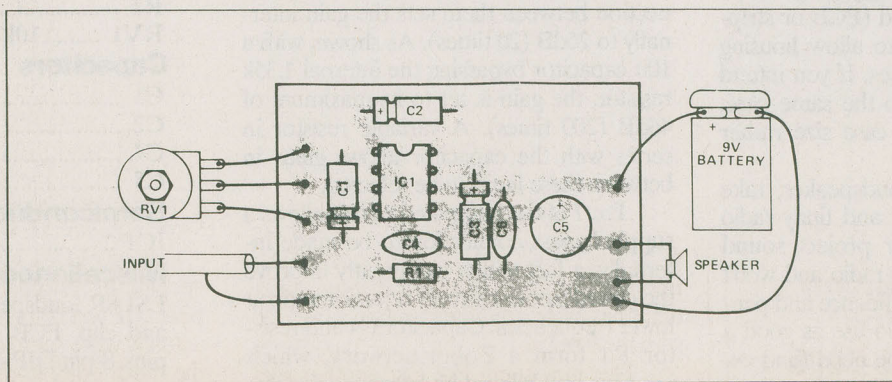


Fig. 2. The component overlay of the PCB.

Fig. 1. You can choose between PCB and stripboard construction. Neither method involves any hazards; the usual precautions and procedures will let you build it safely. The PCB layout, component overlay and wiring diagrams are combined in Fig. 2, while those for stripboard are shown in Fig. 3.

If PCB construction is your choice, the only point to note is to leave insertion of the integrated circuit until last. This way there is less likelihood of damage from a slap-happy soldering iron. Preferably use an IC socket (although this isn't essential) and check that the chip is in the right way around. PCB pins for all input, output and power supply connections make life easy but again aren't essential. Watch for electrolytic capacitor polarization — make sure you get them facing the right way.

Stripboard construction is just as easy.



# The Small-fry Mini-Amp

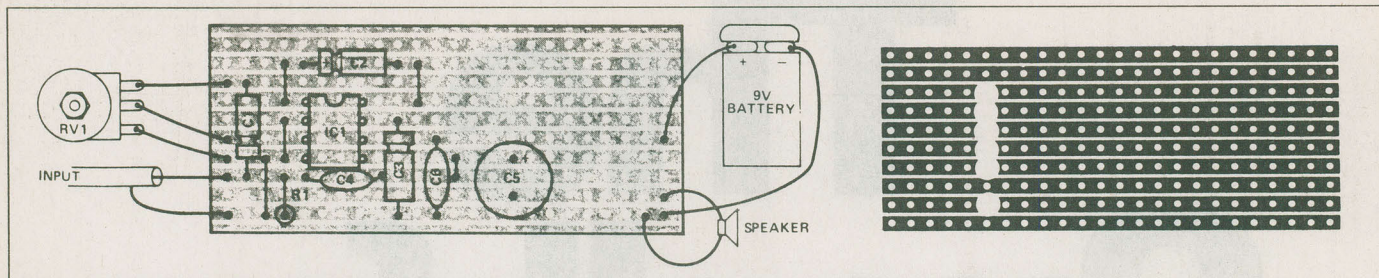


Fig. 3. The component overlay for the stripboard and the track cuts required.

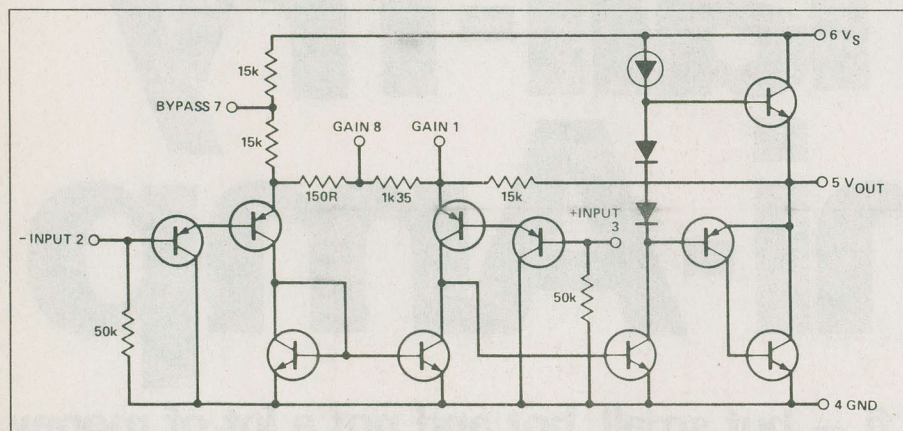


Fig. 4. The internal circuit of the 386 amplifier IC.

Before components are inserted make all track breaks, shown in the underside view of the stripboard in Fig. 3. Then follow the same rules as for PCB construction.

Shielded cable must be used for the input connection; otherwise the amplifier's high gain will ensure heaps of hum and interference. Mount the potentiometer as close to the board as possible, or use shielded cable for these connections too. You'll see the potentiometer in the prototype amplifier is mounted directly to the PCB pins on the PCB. This is a good idea, as it keeps interference to a minimum and allows a method of fixing the board to the front panel of your choice.

Talking of housing, the vast numbers of possible uses makes suggesting a case fairly pointless. The board (PCB or stripboard) is small enough to allow housing inside the smallest of cases. If you intend fitting a loudspeaker into the same case, it'll be this that decides case size rather than the board.

Moving onto the loudspeaker, take care in your choice. Tiny and tinny radio speakers will make your project sound similar to a tiny and tinny radio and won't do your valuable time, confidence and pennies much justice either. So use as good a loudspeaker as you feel the need (and expense) for. There is an argument for not using an internal loudspeaker at all but rather

one of your hi-fi system's loudspeakers.

## How It Works

The circuit for the Small Fry Mini-amp (Fig. 1) tells most of the story. Integrated circuit IC1 is a 386 power amplifier which functions effectively as a power operational amplifier with ground referenced input. Pinout details are provided in Fig. 4. The IC can operate from voltages from 4V through to 12V. Its quiescent current drain with a power supply of 9V is only around 4mA. Internal circuit of the chip is shown in fig. 5.

In the Small Fry the IC is connected in a fairly simple non-inverting amplifier configuration. Gain of the IC is set by the connection between pins 1 and 8. No connection between them sets the gain internally to 26dB (20 times). As shown, with a 10u capacitor bypassing the internal 1.35k resistor, the gain is set to its maximum of 46dB (200 times). A variable resistor in series with the capacitor allows gains in between these limits to be selected.

Pin 7 of the integrated circuit allows a supply bypass connection to be made internally, a fact which can greatly improve the circuit's power supply rejection ratio at lower frequencies. Capacitor C4 and resistor R1 form a Zobel network, which prevents instability at high frequencies due to reactance in certain types of load. ■


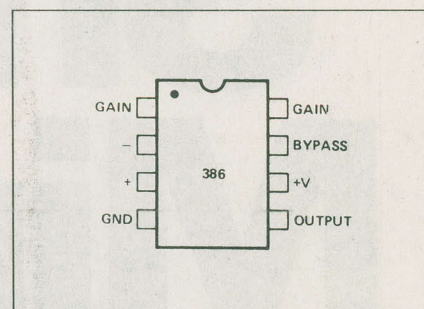


Fig. 4. Pinout of the 386.

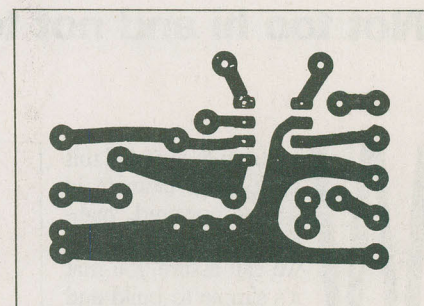

The PCB for the Mini-amp.

## PARTS LIST

### Resistors

All .25W 5%

R1 ..... 12R

RV1 ..... 10k log potentiometer

### Capacitors

C1 ..... 1u 10V electro.

C2, ..... 3 10u 10V electro.

C4, ..... 6 100n

C5 ..... 470u 10V electro.

### Semiconductors

IC1 ..... LM386

### Miscellaneous

LS1 8R loudspeaker, B1 9V battery and clip, PCB or stripboard PCB pins, 8-pin DIP socket.



# Are you a key player, or just a spectator?

If you use microcomputers...either in your business or for your personal applications... you're a member of an elite group of people who exploit the leading edge of technology. If you have invested your time into learning how to make computers work for you, you cannot afford to get anything less than maximum performance out of your equipment.

There are countless sources of microcomputer news available, and while keeping up with the state of the art is important, knowing about the twelve most recent wordprocessing packages to be released won't get you any closer to deciding which one is suitable for your uses.

Computing Now! gets into computers. Its editorial staff uses the latest microcomputer technology every day, and they've forgotten more about computers than most people ever find out. They're your pipeline to using this essential technology.


Every month, the articles in Computing Now! will tell you how to use your microcomputer to its fullest.

In detail.

In depth.

Inside.

SEE  
SPECIAL  
SUBSCRIPTION  
OFFER ON PAGE 32



**Computing Now!**

TWO NEW ALMOST FREE SOFTWARE DISKS

CANADA'S PERSONAL COMPUTER MAGAZINE

THE HOFF

PC HARDWARE TOPS: BACK: HARDWARE

MM70247 \$3.50 JAN 1989

**I need to stay on top of microcomputers**

Please set me up with a ☐ 1 year subscription (\$22.95) ☐ 2 year subscription (\$37.95)

Please ☐ Bill me ☐ Charge my ☐ Visa ☐ Master Card ☐ American Express

Card Number \_\_\_\_\_ Expiry Date \_\_\_\_\_

Name \_\_\_\_\_ Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Province \_\_\_\_\_ Postal Code \_\_\_\_\_

Send to Computing Now!, 1300 Don Mills Road, North York, Ontario M3B 3M8  
or, to expedite delivery, call (416)445-5600 or FAX 416-445-8149.






# THE QUALITY LINE
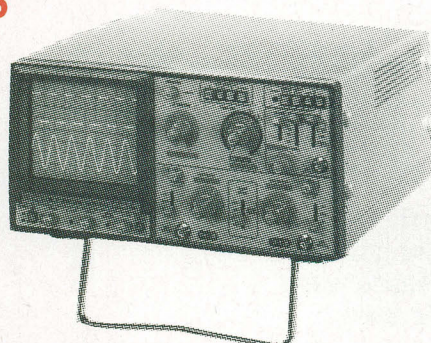
## DUAL TRACE OSCILLOSCOPES — GOS SERIES

For performance and reliability.

- Select from five models.
- Dual or single trace.
- Band width: 40, 20 MHz.
- Triggered/Delayed sweep operation.
- Sensitivity to 1 mV.



## COUNTERS — GFC/GUC SERIES

Full featured, dependable and value priced.

- Choose from four models:

Universal

5 Hz-100 MHz  
GUC2010

Intelligent

DC-1.3 GHz  
GFC8130

Frequency

1 Hz-550 MHz  
GFC8055

Frequency

1 Hz-120 MHz  
GFC8010

- Easy to read LED display.



## DIGITAL MULTIMETERS — GDM SERIES

Rugged and reliable—for the lab, field or production line.

- Select from four models:

3 1/2 or 4 1/2

Digit Display.

LED or LCD

Digital Display

- Standard Functions

(AC/DC

Volts/Amps

& Resistance) plus:

Diode check


Continuity Test

Capacitance

1.99 nF to

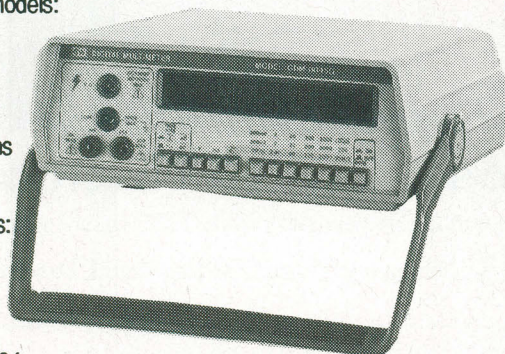19.99  $\mu$ F GDM8034


- Accuracy: to 0.03% (TRMS) GDM8045; to 0.1% DCV GDM8035.


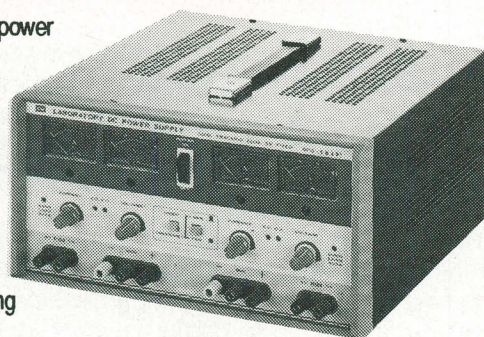
## DC POWER SUPPLIES — GP SERIES

Over twenty quality power supplies for the lab, classroom or production line.

- Single, Dual or Quad output
- Dual-tracking Volts/Amps. (GPD/GPQ) 0-60V./0-10A
- Analogue metering or Digital display
- Regulation 0.01% typical



## WAVEFORM GENERATORS GFG/GPG SERIES

An exceptional combination of Functions and Features.

- Select from these models:

2 MHz

Function

GFG8015/  
8016/8020-

2 MHz

Sweep/


Function

GFG8017/8019

13 MHz Function GFG813

5 MHz Pulse GPG8018

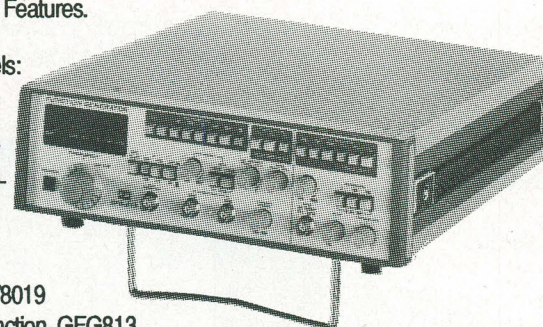- Waveform Output: Sine, Square, Triangle, TTL Pulse & Ramp



## DIGITAL IC TESTERS — GTC/GUT SERIES

- Test up to 1800 popular ICs.

- Choose between two models:

GUT6000

(1800 types)

GTC3000

(1700 types)

- Test:


54/74 Series TTL

55/75 Series TTL

High Speed CMOS

- Repetitive Test Cycle for Production Usage.

- Auto-Search identifies unknown ICs.

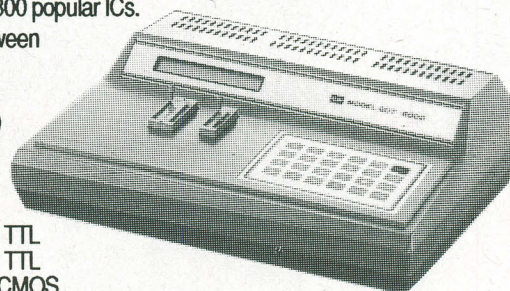

CSA Approved where applicable — One Year Warranty. Available through your local electronic distributor.

# DUNCAN INSTRUMENTS CANADA LTD.

## ELECTRONIC INSTRUMENT SPECIALISTS

121 MILVAN DRIVE, WESTON (TORONTO), ONTARIO M9L 1Z8

TELEPHONE: (416) 742-4448 FAX: (416) 749-5053



**We can count the number of portables  
we make on one hand.**




It's just that we need several extra fingers to do it. Because our "first family" of portable computers is almost three times larger than anyone else's.

Which means that we offer you the portable computer which fits *your* needs like a glove. Whatever your needs. From the complete battery powered laptops to incredibly powerful desktops, intelligent terminals and LAN nodes and servers. All in truly portable packages.

It's our impressive and

comprehensive quality family, coupled with state-of-the-art technology and a commitment to stay number one, which has made Toshiba the best selling portable computers in Canada. Thanks to you, over 50% of Canada's portables proudly bear the name Toshiba.

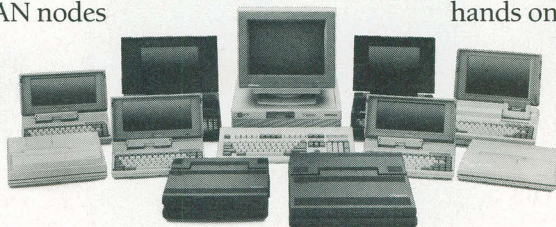**The best do keep getting better.** To get your hands on the best portable for you, call your nearest Toshiba reseller. Or call Toshiba direct at 1-800-387-5645.



**TOSHIBA**

**WE MEAN BUSINESS**

INFORMATION SYSTEMS DIVISION

Circle No. 12 on Reader Service Card



# Tecmar Set the Standard for Excellence in Tape Backup.

## Now We've Topped It.

### Introducing QT-125™

Nobody has to tell you that Tecmar is the leader in tape backup systems. After all, *more than 70,000 users* have chosen Tecmar's popular QIC-60™ 60MByte products to protect their data.


**The New Standard.** And now, Tecmar has set the new tape backup standard for massive data storage applications—with a 125MByte tape system for IBM PC/XT/AT, Compaq 286, 386 and compatibles. It's called the QT-125, the first in Tecmar's new QualityTape™ family of products.

**The Performance Leader.** The QT-125 internal and external drives incorporate industry-standard SYTOS™ tape drive software, are QIC-120 hardware compatible, and employ the high-reliability Wangtek drive. Performance features include:

- Network compatibility with Novell, 3COM and IBM Token Ring.
- Automatic and unattended backup.
- IBM 6157 streaming cartridge tape compatibility.

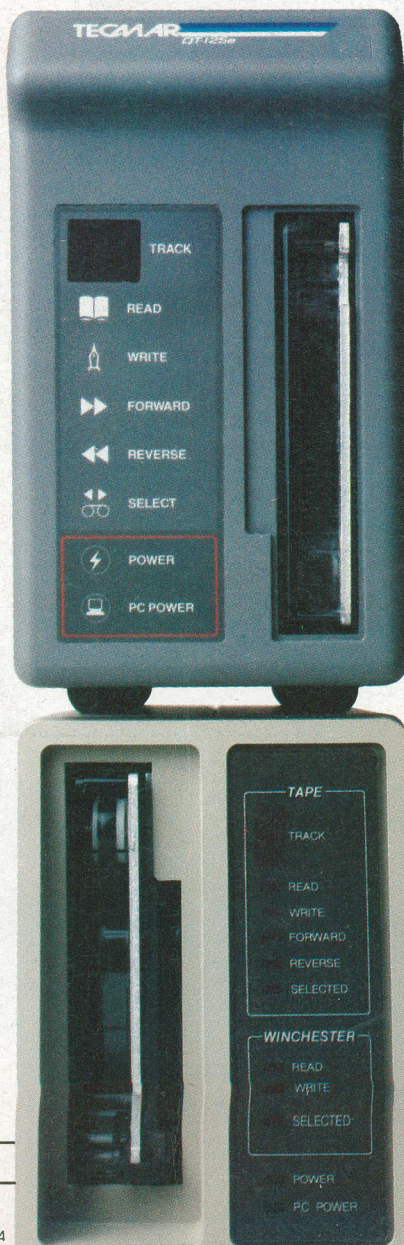**EMJ Data Systems Ltd.**

HEAD OFFICE:  
GUELPH  
(519) 837-2444 FAX (519) 836-1914



- On-line backup speed of 5MBytes per minute.
- File-by-file or mirror-image backup and restore.
- And much more.

**Two-Year Warranty Plus.** Best of all, with the QT-125 you get Tecmar quality backed by the industry's only two-year warranty including the new QuickTurn™ Quality Service program. If you have any trouble with your Tecmar QT-125 in the first six months of operation, we'll send you a replacement within 48 hours.



**Stay with the Leader.** So, when you need tape backup, go for the top in quality, reliability and performance. It's Tecmar—again.

QIC-60 is a trademark of Colorado Memory Systems; SYTOS is a trademark of Sytron Corp.; IBM PC/XT/AT are registered trademarks of International Business Machines Corp.; ComputerLand is a registered trademark of ComputerLand Corporation; BusinessLand is a registered trademark of BusinessLand Corporation.

Circle Number 06 on Reader Service Card

**TECMAR**  
a subsidiary of Rexon, Inc.

**The Power Behind Your PC**

BRANCHES:  
Vancouver (604) 875-9344 FAX (604) 875-6393  
Calgary (403) 228-1535 FAX (403) 244-4469  
Winnipeg (204) 452-4411 FAX (204) 452-8594

Toronto (416) 454-2940  
Montreal (514) 849-4171 FAX (514) 288-6062  
Halifax (902) 423-6152 FAX (902) 423-3628  
(B.C., Alta.): 1-800-663-9048

\*TOLL FREE  
(Man., Ont., Que., N.B., N.S., P.E.I.): 1-800-265-72

Circle No. 13 on Reader Service Card